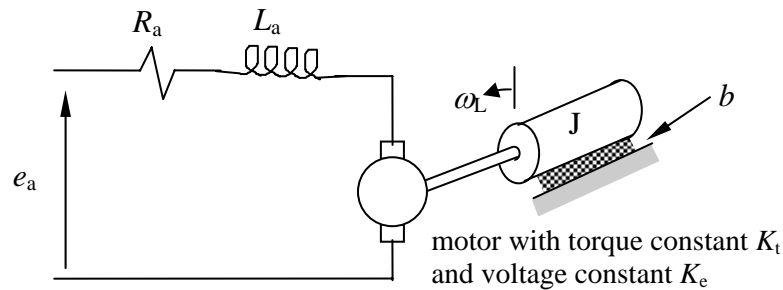


Lesson 08

Problem 8.1

For the armature-controlled DC motor shown below,

- Determine the necessary algebraic and differential equations to relate the known input voltage, e_a , to the angular velocity of the load, ω_L . Your solution should consist of a numbered list of equations, a list of unknowns, and a list of known or computed parameters.
- Determine the transfer function relating the armature current to the input voltage, $I_a(s)/V_a(s)$, and the transfer function relating the angular velocity to the input voltage, $\Omega(s)/V_a(s)$.
- For each of these two transfer functions, determine the static gain, the natural frequency, and the damping ratio.




Problem 8.2

A two pole Butterworth low-pass active filter is shown.

- Determine the transfer function between the output e_o and the input e_s .
- Determine an expression for the natural frequency and the damping ratio of this circuit.
- From the given list of commonly-available resistors and capacitors, select values for R , C_1 , and C_2 such that the following design criteria are met:

$$9000 \leq \omega_n \leq 10,000 \text{ rad/s}$$
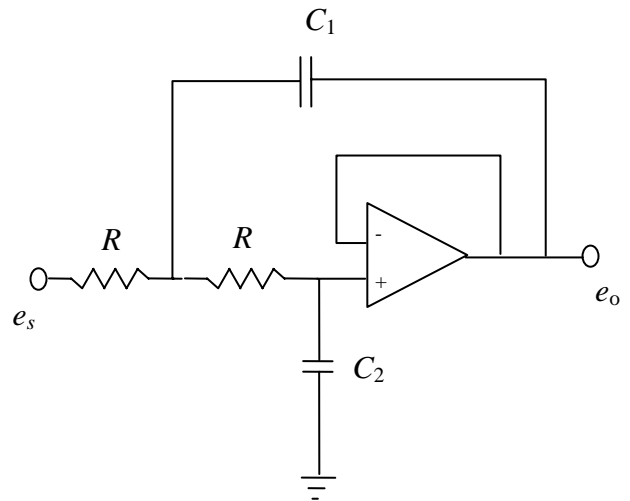
$$0.7 \leq \zeta \leq 1.0$$
- Substitute your design values into the transfer function and create a Simulink simulation (using the transfer-function block) for this system. Plot the output for a unit step input.



Resistors				Capacitors		Inductors
ohms		kohms	kohms	microF	picoF	microH
1	56	1	27	1000	5000	330
1.5	62	1.1	30	680	4700	3300
2.7	68	1.2	33	470	4560	
4.3	75	1.3	36	220	2200	milliH
4.7	82	1.5	39	100	1500	33
5.1	91	1.6	43	47	1000	
5.6	100	1.8	47	33	470	
6.2	110	2	51	22	330	
6.8	120	2.2	56	10	220	
7.5	130	2.4	62	4.7	100	
8.2	150	2.7	68	3.3	68	
9.1	160	3	75	2.2	47	
10	180	3.3	82	1	33	
11	200	3.6	91	0.47	27	
12	220	3.9	Mohms	0.33	22	
13	240	4.3	1	0.22	18	
15	270	4.7	1.1	0.1	12	
16	300	5.1	1.2	0.047	10	
18	330	5.6	1.3	0.033	7.5	
20	360	6.2	1.5	0.022	5	
22	390	6.8	1.6	0.01	2.2	
24	430	7.5	1.8		1.8	
27	470	8.2	2			
30	510	9.1	2.1			
33	560	10	2.4			
36	620	11	2.7			
39	680	12	3			
43	750	13	3.3			
47	820	15	3.9			
51	910	16	4.7			
		18	5.6			
		20	6.8			
		22	8.2			
		24	10			

