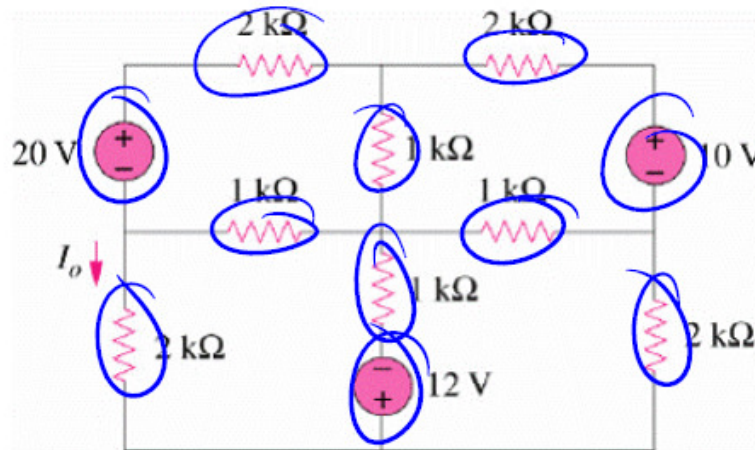


**Homework Set #10**  
**DUE Friday, March 31, 2017**


1. In the circuit:
  - a. how many circuit elements are there?
  - b. how many nodes are in the circuit?
  - c. how many essential nodes are in the circuit?
  - d. how many branches are there?
  - e. how many loops are in the circuit?
  - f. how many meshes are in the circuit?




B Nodes circled = 7

C essential nodes squared = 5

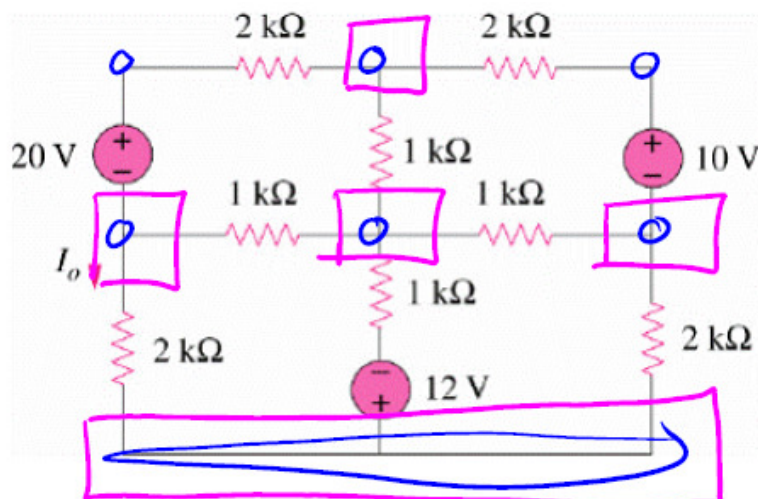
essential nodes are those connecting 3 or more elements



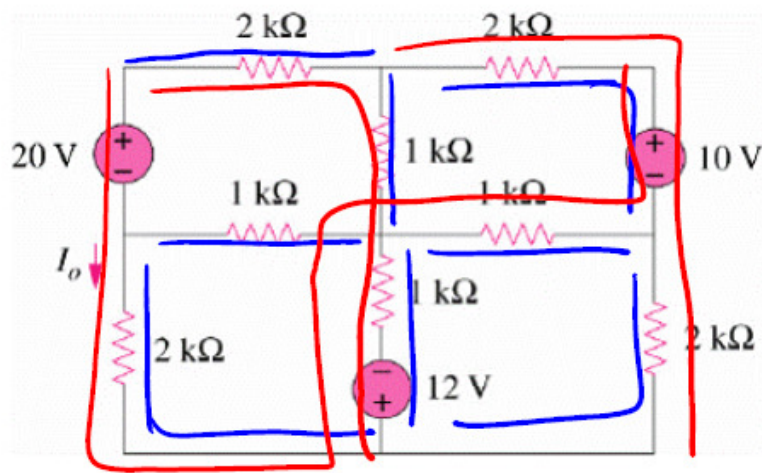
D Branches are traced - too many to count..




E Loops circled =  $4 + 3 + 4 = 11$

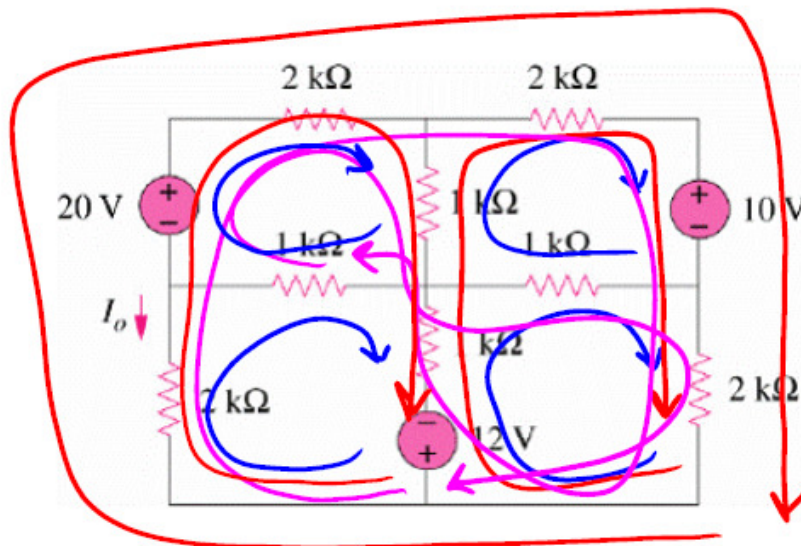

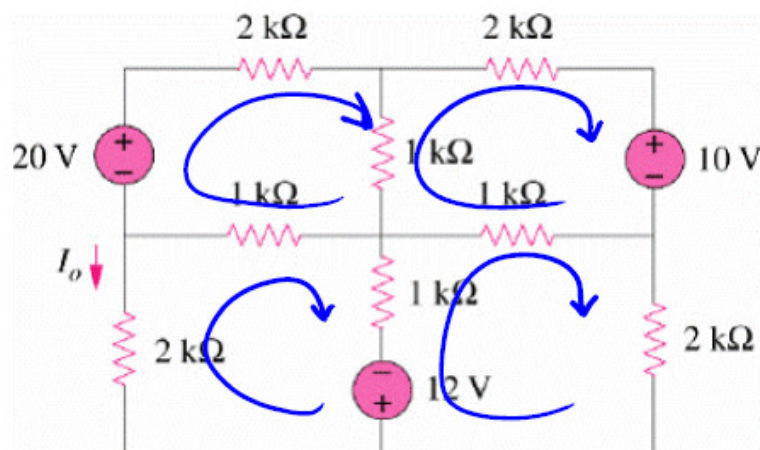F meshes are loops that don't enclose other loops = 4



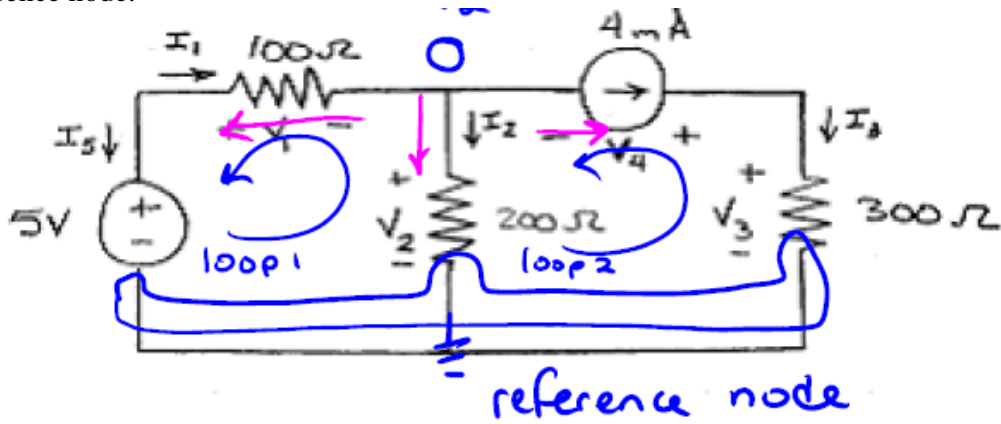2. For the following circuit, identify the node voltages and solve for the values using the node voltage method to solve for the values of  $V_1-V_4$ ,  $I_1-I_5$ . . Make it clear which node you are using as the reference node.



Node-voltage method

$$\text{KCL)} \quad \frac{V_2 - 5}{100} + \frac{V_2}{200} + 4\text{m} = 0$$

$$\boxed{V_2 = 3.067 \text{ V}}$$

$$\text{KVL)} \quad -V_2 - V_1 + 5 = 0$$

$$\boxed{V_1 = 1.933 \text{ V}}$$

$$\text{Ohms Law)} \quad V_3 = (4\text{mA})(300)$$

$$\boxed{V_3 = 1.2 \text{ V}}$$

$$\text{KVL)} \quad -V_3 + V_4 + V_2 = 0$$

$$\boxed{V_4 = -1.867 \text{ V}}$$

Solve for currents!


$$I_1 = \frac{5 - V_2}{100} \Rightarrow I_1 = 19.33 \text{ mA}$$

$$I_2 = \frac{V_2}{200} \Rightarrow I_2 = 15.34 \text{ mA}$$

$$I_3 = 4 \text{ mA}$$

$$I_5 = -I_1 = -19.33 \text{ mA}$$

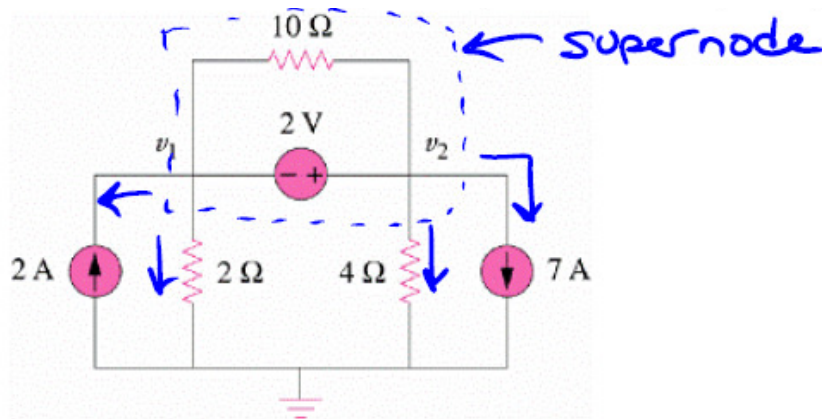3. Use nodal-voltage analysis to find  $v_1$  and  $v_2$  in the following circuit  
 (Note: the 2V source between nodes makes a supernode.)



KCL  
 $v_1 + v_2$ ) 
$$-2 + \frac{v_1}{2} + \frac{v_2}{4} + 7 = 0$$

super  
 node) 
$$-v_1 - 2 + v_2 = 0$$

$$v_1 = -7.33V$$

$$v_2 = -5.33V$$