

## Homework Set #11

DUE Monday, April 3, 2017

For the circuit in Figure E4.11 determine the power supplied by each source using:

- Nodal Analysis
- Mesh Analysis

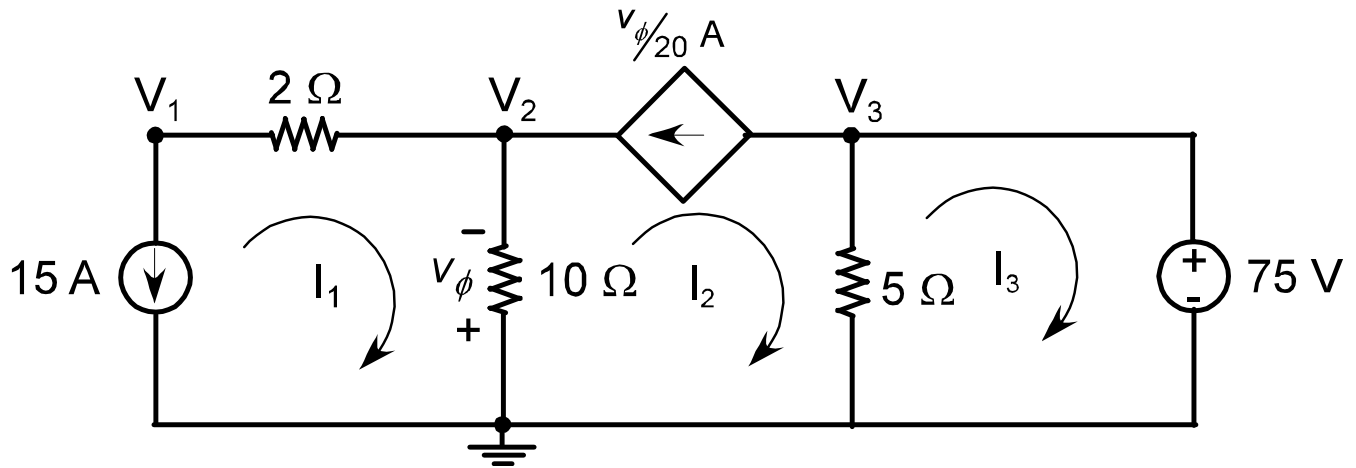


Figure E4.11

a)

By observation:  $v_\phi = -V_2$ 

$$\text{Node 1: } \frac{V_1 - V_2}{2} + 15 = 0$$

$$\text{Node 2: } \frac{V_2 - V_1}{2} + \frac{V_2}{10} - \frac{V_\phi}{20} = 0 \quad \text{gives} \quad \frac{V_2 - V_1}{2} + \frac{V_2}{10} + \frac{V_2}{20} = 0$$

$$\text{Node 3: } V_3 = 75 \text{ V}$$

The foregoing equations can be re-arranged as follows:

$$\begin{aligned} 0.5V_1 - 0.5V_2 &= -15 \\ -0.5V_1 + 0.65V_2 &= 0 \end{aligned}$$

In matrix form:

$$\begin{bmatrix} 0.5 & -0.5 \\ -0.5 & 0.65 \end{bmatrix} \times \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} -15 \\ 0 \end{bmatrix}$$

When *inverted*:

$$\begin{bmatrix} 8.667 & 6.667 \\ 6.667 & 6.667 \end{bmatrix} \times \begin{bmatrix} -15 \\ 0 \end{bmatrix} = \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

These solve to:  $V_1 = -130 \text{ V}$ , and  $V_2 = -100 \text{ V}$ Which leads to:  $P_{15A} = +V_1 \times 15 = -130 \times 15 = -1950 \text{ W}$ ,

$$P_{75V} = -V_3 \times (-V_2/20 + V_3/5) = -75 \times (5 + 15) = -1500 \text{ W}$$

$$P_{DEP} = +(V_3 - V_2) \times (-V_2/20) = +(75 + 100) \times (+100/20) = +875 \text{ W}$$


b)

By observation:  $I_2 = -V_\phi/20$ ,  $v_\phi = 10(I_2 - I_1)$  and  $I_1 = -15 \text{ A}$  gives:  $I_2 = -0.5(I_2 + 15)$ Solves to:  $I_2 = -5 \text{ A}$ Mesh 3:  $75 + 5(I_3 - I_2) = 0$  gives:  $5(I_3 + 5) = -75$  Solves to:  $I_3 = -20 \text{ A}$

2. And just when you thought it was safe!!

For the circuit in Figure E4.12 determine the power supplied by each source using:

- Nodal Analysis
- Mesh Analysis

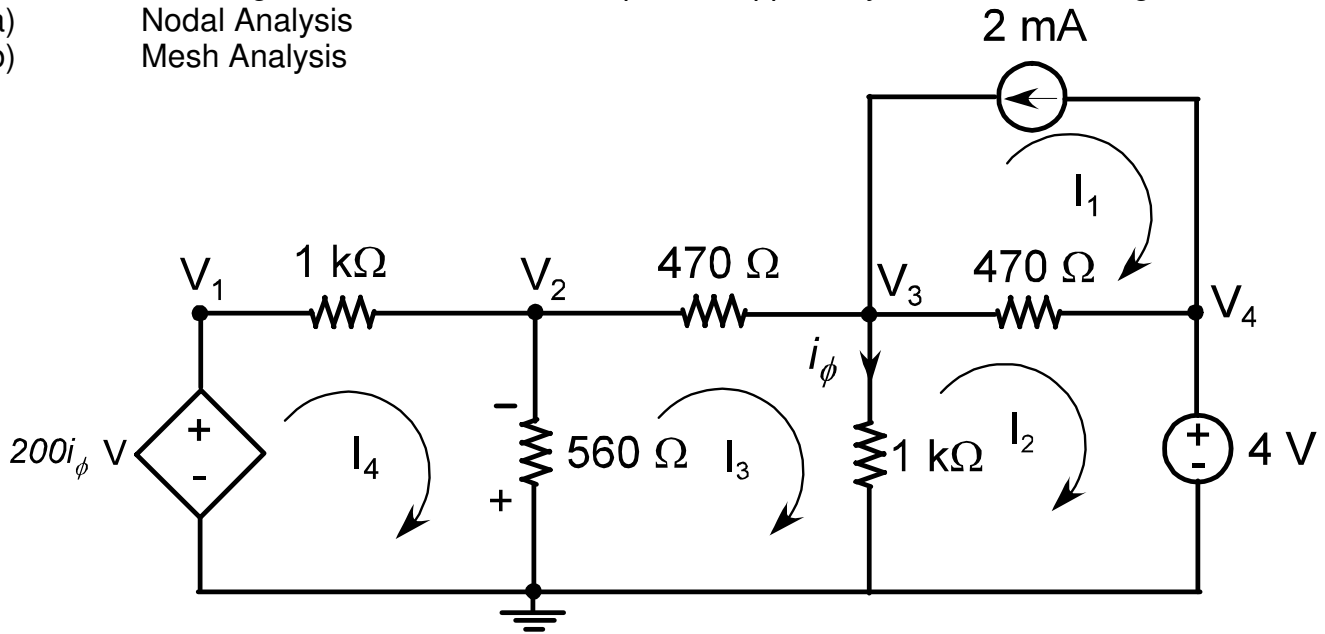

a)  
By observation:  $i_\phi = 0.001V_3$  and  $V_1 = 200 \times 0.001V_3 = 0.2V_3$  and  $V_4 = 4 \text{ V}$

Node 2:  $\frac{V_2 - 0.2V_3}{1000} + \frac{V_2}{560} + \frac{V_2 - V_3}{470} = 0$  gives  $4.913V_2 - 2.328V_3 = 0$

Node 3:  $0.002 + \frac{V_3}{1000} + \frac{V_3 - V_2}{470} + \frac{V_3 - 4}{470} = 0$  gives  $-2.128V_2 + 5.255V_3 = 10.511$

These solve to:  $V_2 = 1.173 \text{ V}$ , and  $V_3 = 2.475 \text{ V}$

b)  
Observation:  $i_\phi = (I_3 - I_2)$  and  $I_1 = -0.002 \text{ A}$

Mesh 2:  $4 + 1000(I_2 - I_3) + 470(I_2 + 0.002) = 0$  gives:  $1470I_2 - 1000I_3 = -4.94$

Mesh 3:  $1000(I_3 - I_2) + 560(I_3 - I_4) + 470 I_3 = 0$  gives:  $-1000I_2 + 2030I_3 - 560I_4 = 0$

Mesh 4:  $-200(I_3 - I_2) + 1000I_4 + 560(I_4 - I_3) = 0$  gives:  $200I_2 - 760I_3 + 1560I_4 = 0$


Solves to:  $I_1 = -2 \text{ mA}$ ,  $I_2 = -5.25 \text{ mA}$ ,  $I_3 = -2.77 \text{ mA}$  and  $I_4 = -0.677 \text{ mA}$

Which leads to:  $P_{2\text{mA}} = +(V_4 - V_3) \times 0.002 = 1.525 \times 2 = 3.05 \text{ mW}$ ,

$P_{4\text{V}} = +V_4 \times I_2 = 4 \times -5.25 = -21 \text{ mW}$

$P_{\text{DEP}} = -0.2(I_3 - I_2) \times I_4 = -0.2(-2.77 + 5.25) \times (-0.677) = 0.336 \text{ mW}$

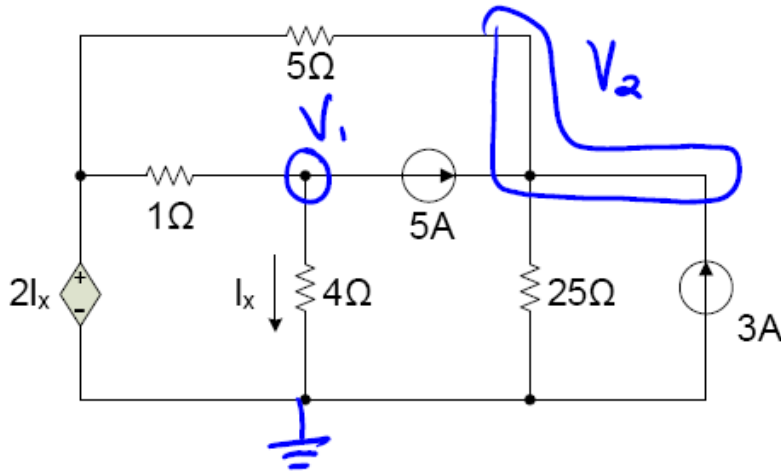3. Given the following circuit (Note: this is an old exam problem)  
 Label the circuit with all the node voltages including the reference node  
 a. Use the node-voltage method to solve for the unknown node-voltages  
 b. Compute the value of  $I_x$ .



$$\text{KCL } \left. \begin{array}{l} \\ V_1 \end{array} \right) \quad \frac{V_1 - 2I_x}{1} + \frac{V_1}{4} + 5 = 0$$

$$\text{KCL } \left. \begin{array}{l} \\ V_2 \end{array} \right) \quad \frac{V_2 - 2I_x}{5} - 5 + \frac{V_2}{25} - 3 = 0$$

$$\text{constraint) } \quad I_x = \frac{V_1}{4}$$

$V_1 = -6.667 \text{ V}$ $V_2 = 30.56 \text{ V}$ $I_x = -1.667 \text{ A}$
---