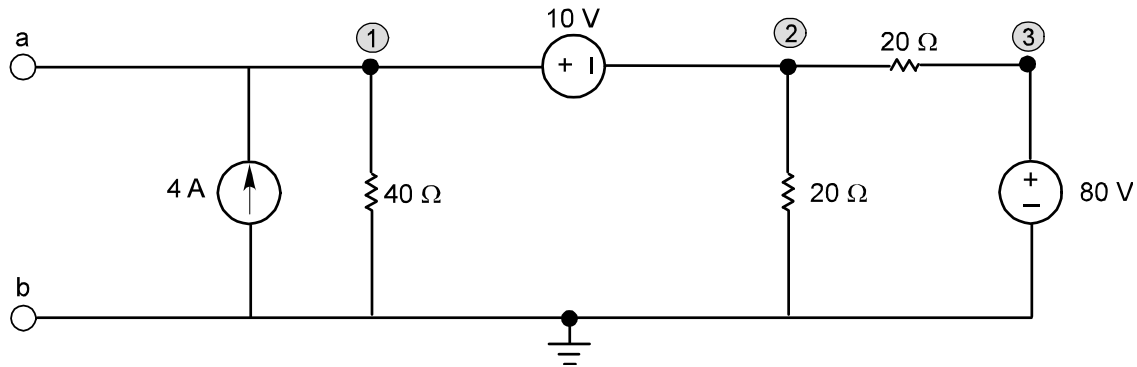


Homework Set #13
DUE Friday, April 3, 2017

1. For the circuit shown below:



a)

- Write and solve the nodal equation needed to determine V_1 .
- b) De-activate the sources and determine the resistance seen by terminals a—b, when they are open-circuited.
- c) Draw the Thevenin Equivalent at terminals a—b.
(NOTE: you can use source transforms to check this result.)

$$V_2 = V_1 - 10 \quad \text{and} \quad V_3 = 80$$

$$-4 + \frac{V_1}{40} + \frac{V_2}{20} + \frac{V_2 - 80}{20} = 0$$


$$-4 + \frac{V_1}{40} + \frac{V_1 - 10}{20} + \frac{V_1 - 90}{20} = 0$$

$$0.125V_1 = 9$$

$$\text{This solves to:} \quad V_1 = 72 \text{ V} = V_{Th}$$

$$R_{Th} = 40 // 20 // 20 = 8 \text{ } \Omega$$

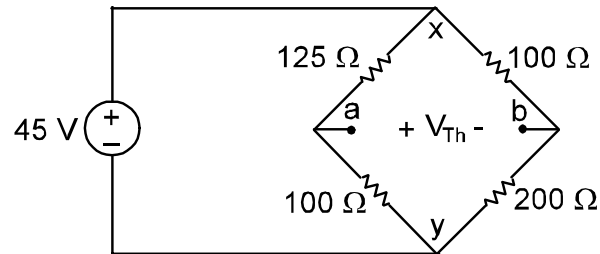2. Determine the Thevenin equivalent circuit across terminals a—b for the Wheatstone Bridge shown below:



(NOTE: When you de-activate the 45 V source x & y become the same node, so some resistors are in parallel when you look into a-b.)


With a—b on O/C, V_{Th} is the difference of two voltage dividers.

$$V_a = 45 \times \frac{100}{125 + 100} = 20 \text{ V} \quad \text{and} \quad V_b = 45 \times \frac{200}{200 + 100} = 30 \text{ V}$$


$$V_{Th} = V_a - V_b = \boxed{-10 \text{ V}}$$

With the 45V source de-activated $R_{Th} = (125//100) + (200//100) = \boxed{122.2 \Omega}$

3. For the circuit shown below:

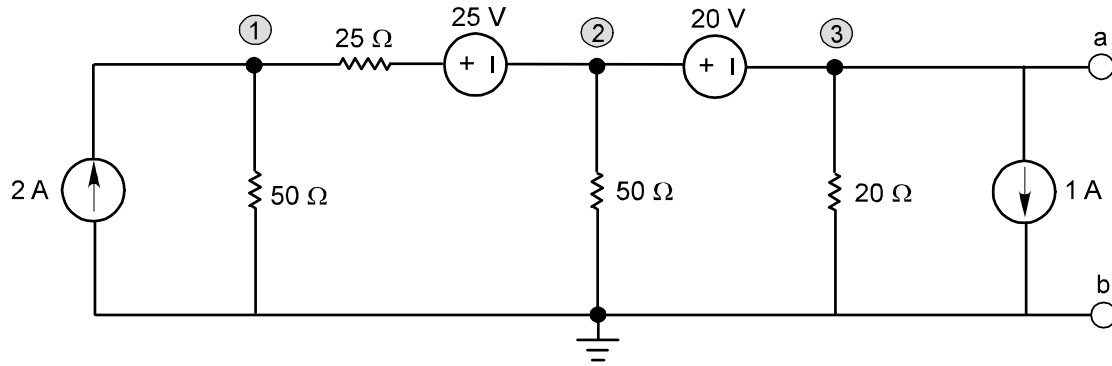

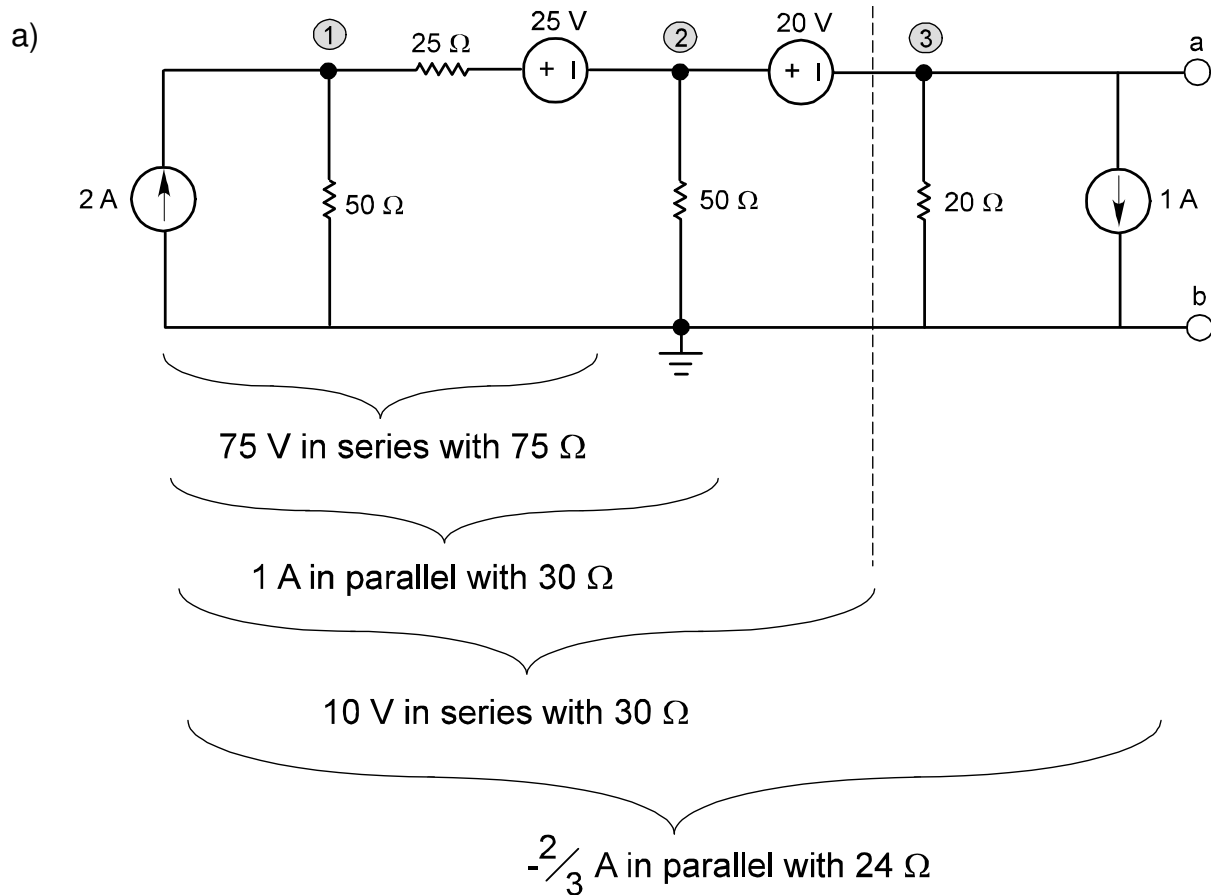- a) Use source transforms to determine the Thevenin Equivalent at terminals a—b. (i.e. Draw the Thevenin Equivalent looking into terminals a—b.)
 b) Assume the answer to part (a) is $V_{Th} = 12\text{ V}$ and $R_{Th} = 8\ \Omega$ (NOTE: this is **not** the answer to part (a)) and determine the power dissipated in a $127.5\ \Omega$ load resistor connected across a—b.



$$I_L = \frac{12}{127.5 + 8} = 88.6\text{ mA} \quad \text{and} \quad P_L = 0.0886^2 \times 127.5 = 1\text{ W}$$