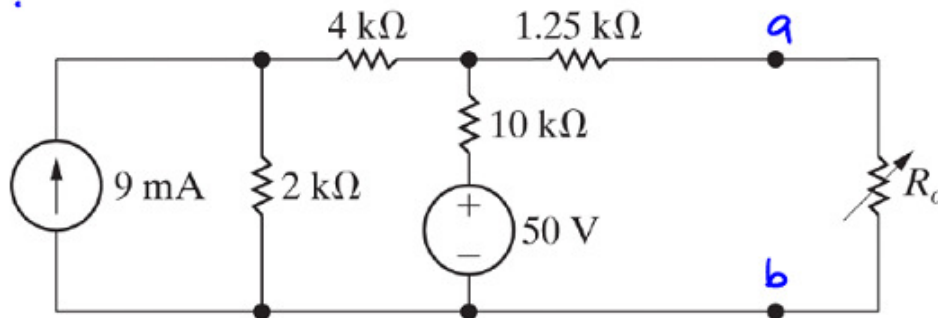



**Homework Set #16**  
**DUE Monday, April 24, 2017**

1. Recall that maximum power transfer occurs when  $R_L = R_{Th}$ . The rheostat ( $R_o$ ) is adjusted to give maximum power transfer.

- Find the value of  $R_o$ .
- Find the maximum power that can be delivered to  $R_o$ .



Find Thev eq. ckt

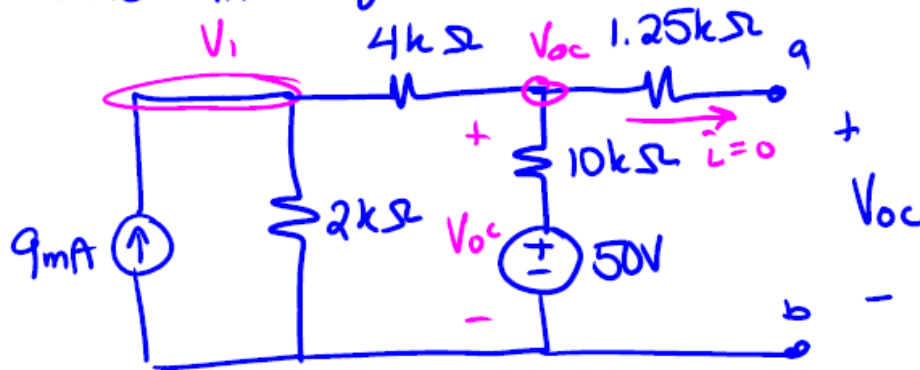


$$\text{KCL } \left. \begin{array}{l} V_1 \\ V_1 \end{array} \right) \quad -9\text{m} + \frac{V_1}{2\text{k}} + \frac{V_1 - V_{oc}}{4\text{k}} = 0$$

$$\text{KCL } \left. \begin{array}{l} V_2 \\ V_2 \end{array} \right) \quad \frac{V_{oc} - V_1}{4\text{k}} + \frac{V_{oc} - 50}{10\text{k}} = 0$$

$$V_1 = 22 \text{ V}$$

$$V_{oc} = 30 \text{ V} \Rightarrow \boxed{V_{TH} = 30 \text{ V}}$$

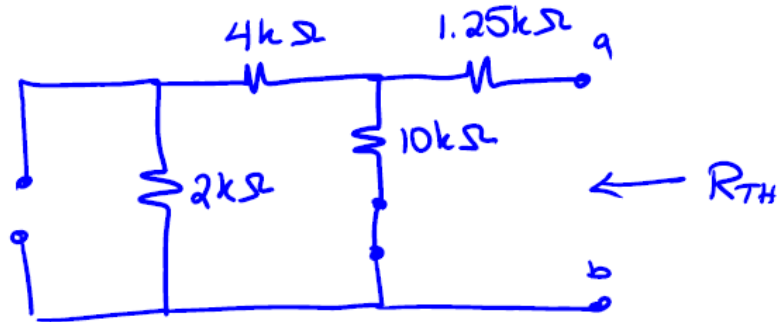
Find  $R_{TH}$  direct method  
(zero sources)



$$R_{TH} = (4 \text{ k} + 2 \text{ k}) // 10 \text{ k} + 1.25 \text{ k}$$

$$\boxed{R_{TH} = 5 \text{ k}\Omega}$$

Then eq.

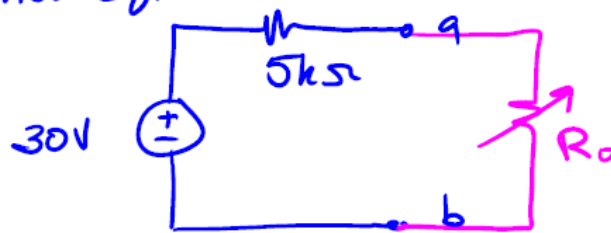

set  $R_0 = R_{TH}$  for max power



$$\boxed{R_0 = 5 \text{ k}\Omega}$$

$$b) \quad V_L = 30 \frac{1}{2}$$

$$P_L = V_L^2 / R_0$$

$$\boxed{P_L = 45 \text{ mW}}$$

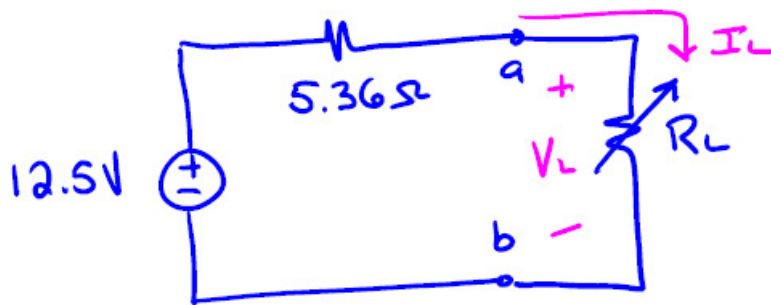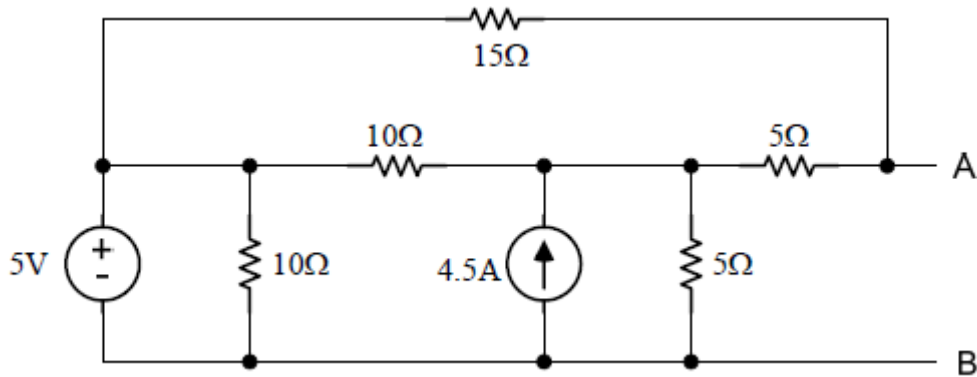2. In order to provide a graphical verification of the Maximum Power Transfer Theorem, plot (EXCEL, MATLAB or MAPLE) the power  $P_L$  extracted from this circuit (in other words, the power absorbed by a load resistor,  $R_L$ , connected across terminals A-B) as a function of the load resistance  $R_L$  as  $R_L$  is varied between  $0.25 R_{Lmax}$  and  $4R_{Lmax}$ . Your plot should reveal that  $P_L$  is at a maximum when  $R_L = R_{Lmax}$ . *Hint: you found the Thevenin equivalent of this circuit in homework 14.*



$$V_L = 12.5 \frac{R_L}{5.36 + R_L} \quad I_L = \frac{12.5}{5.36 + R_L}$$

$$P_L = \frac{V_L^2}{R_L} = \left( \frac{12.5}{5.36 + R_L} \right)^2 R_L$$

or

$$P_L = I_L^2 R_L = \left( \frac{12.5}{5.36 + R_L} \right)^2 R_L$$

Plot of Power delivered to the load

