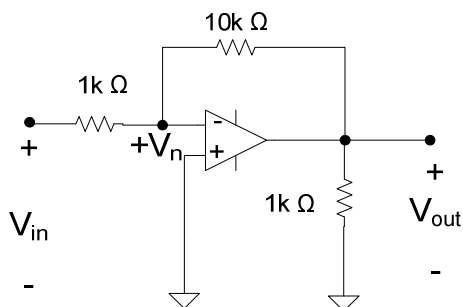


Homework Set #20
DUE Tuesday, May 2, 2017

1. For the circuit below, assume the op-amp is ideal.
 - a. What is the main function of the op-amp circuit below?
 - b. Find the value of V_n in the circuit if $V_{in} = 1V$
 - c. Find the value of V_{out} in the circuit if $V_{in} = 1V$
 - d. Find the Voltage Gain of the circuit, V_{out}/V_{in}
 - e. Assume that the op-amp supply voltages are $V_{cc} = \pm 20V$, and the op-amp saturates at the supply voltages, find the maximum range of the input voltage (V_{in}) that will allow the op-amp to operate in its linear range.



a) Inverting amplifier

b) $V_p = 0$ (tied to ground)

$V_n = V_p$ (ideal op amp assumption)

$$\boxed{V_n = 0}$$

c) KCL at V_n) $\frac{0 - 1}{1k} + \frac{0 - V_{out}}{10k} = 0$

$$V_{out} = 10k \left(\frac{-1}{1k} \right)$$

$$\boxed{V_{out} = -10V}$$

d) KCL at V_n) $\frac{0 - V_{in}}{1k} + \frac{0 - V_{out}}{10k} = 0$

$$\frac{V_{out}}{V_{in}} = -\frac{10k}{1k}$$

$$\boxed{\text{Gain} = -10}$$


e) $V_{out} = -10 V_{in}$

$$-20 \leq V_{out} \leq 20$$

$$-20 \leq -10 V_{in} \leq 20$$

$$\boxed{2 \geq V_{in} \geq -2}$$

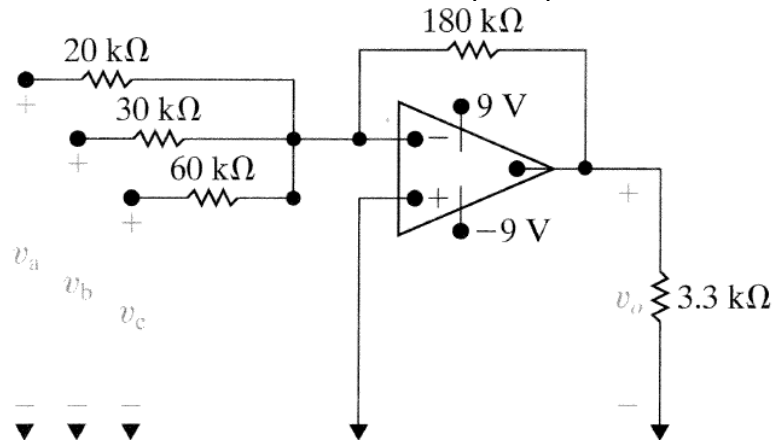2. For the circuit below, assume the op-amp is ideal.



- What circuit configuration is shown in this figure?
- Find v_o if $v_a = 0.5$ V, $v_b = 1.5$ V, and $v_c = -2.5$ V.
- The voltages v_a and v_b remain at 0.5 V and 1.5 V, respectively. What are the limits on v_c if the op amp operates within its linear region?

[a] This circuit is an example of an inverting summing amplifier.

$$[b] v_o = -\frac{180}{20}v_a - \frac{180}{30}v_b - \frac{180}{60}v_c = -4.5 - 9 + 7.5 = -6 \text{ V}$$


$$[c] v_o = -13.5 - 3v_c = \pm 9$$

$$\therefore v_c = -7.5 \text{ V when } v_o = 9 \text{ V};$$


$$v_c = 1.5 \text{ V when } v_o = -9 \text{ V}$$

$$\therefore -7.5 \text{ V} \leq v_c \leq 1.5 \text{ V}$$

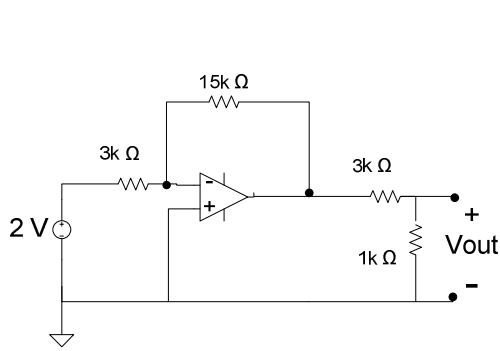
3. For each circuit below, assume the op-amp is ideal. Find the value of V_{out} and describe what the circuit does.




(a)

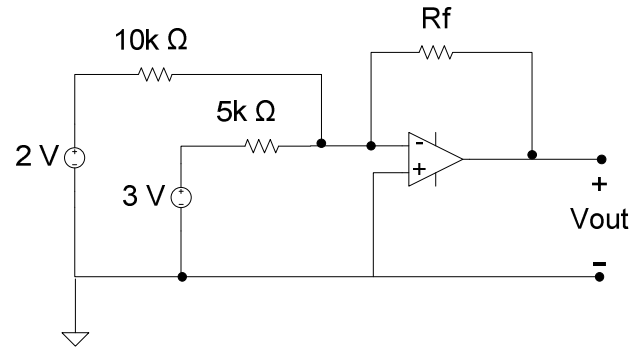

(b)

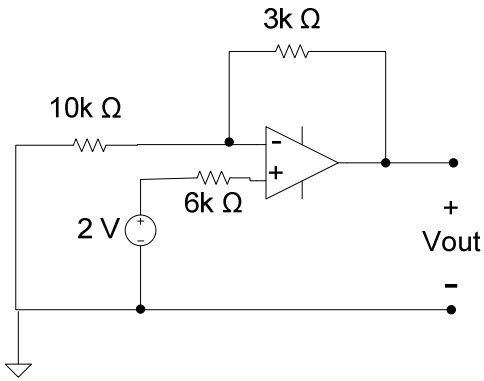


(c)

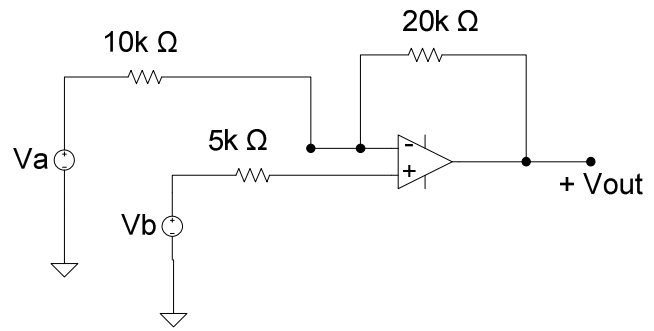

(d)

a) Inverting Amplifier

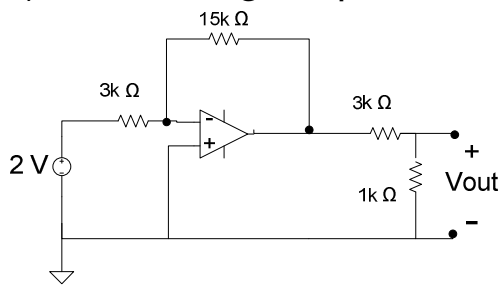


$$\frac{V_x}{2} = -\frac{15k}{3k}$$

$$V_{out} = V_x \frac{1k}{3k+1k}$$

$$V_{out} = -10 \left(\frac{1}{4} \right)$$


$$V_{out} = -2.5V$$

b) Summing Amplifier

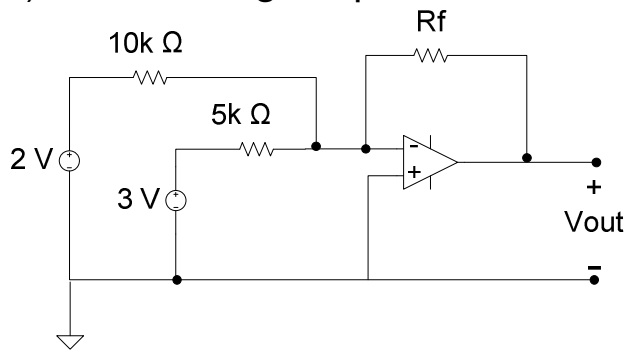

$$\begin{aligned}
 V_{out} &= -\frac{R_F}{10k} 2 - \frac{R_F}{5k} 3 \\
 &= -\frac{R_F}{1000} (0.2 + 0.6) \\
 &= -\frac{R_F(0.8)}{1000}
 \end{aligned}$$


c) Non-Inverting Amplifier

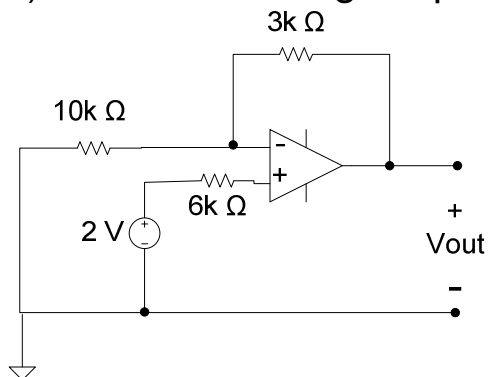

$$\underbrace{V_o}_2 = \left(1 + \frac{3k}{10k}\right)$$

$$\boxed{V_o = 2.6V}$$

d) Difference Amplifier

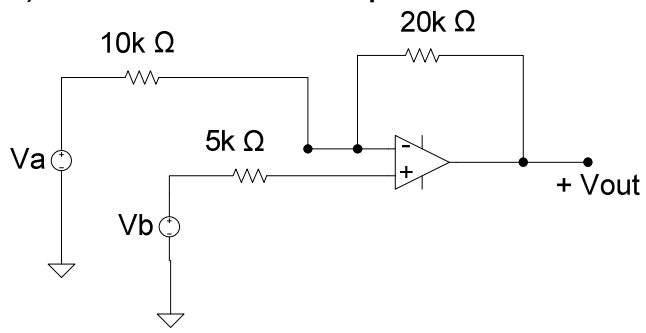

using super position

$$V_o = V_a \left(-\frac{20k}{10k} \right) + V_b \left(1 + \frac{20k}{10k} \right)$$