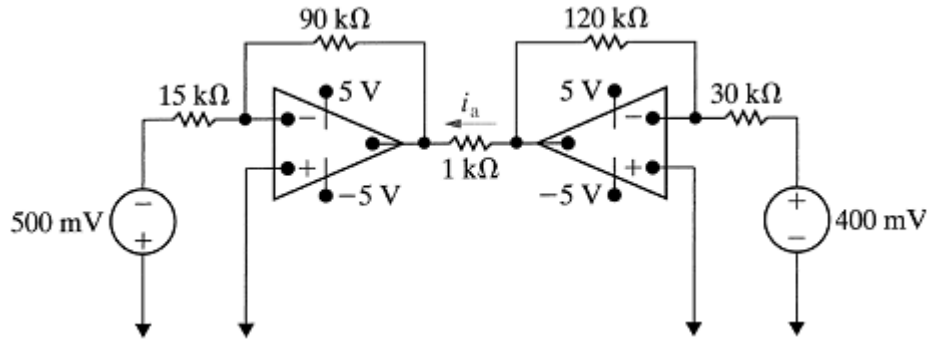


**Homework Set #22**  
**DUE Monday, May 8, 2017**

1. The op-amps in the following circuit are ideal.



Let  $v_{o1}$  = output voltage of the amplifier on the left. Let  $v_{o2}$  = output voltage of the amplifier on the right. Then

- a) Find  $i_a$ .
- b) Find the value of the right source voltage for which  $i_a = 0$ .

[a] Let  $v_{o1}$  = output voltage of the amplifier on the left. Let  $v_{o2}$  = output voltage of the amplifier on the right. Then

$$v_{o1} = \frac{-90}{15}(-0.5) = 3 \text{ V}; \quad v_{o2} = \frac{-120}{30}(0.4) = -1.6 \text{ V}$$

$$i_a = \frac{v_{o2} - v_{o1}}{1000} = -4.6 \text{ mA}$$

[b]  $i_a = 0$  when  $v_{o1} = v_{o2}$  so from (a)  $v_{o2} = 3 \text{ V}$

Thus


$$\frac{-120}{30}(v_L) = 3$$

$$v_L = -\frac{90}{120} = -750 \text{ mV}$$

2.

The op amp in the noninverting amplifier circuit of Fig. P5.43 has an input resistance of  $440 \text{ k}\Omega$ , an output resistance of  $5 \text{ k}\Omega$ , and an open-loop gain of  $100,000$ . Assume that the op amp is operating in its linear region.

Figure P5.43

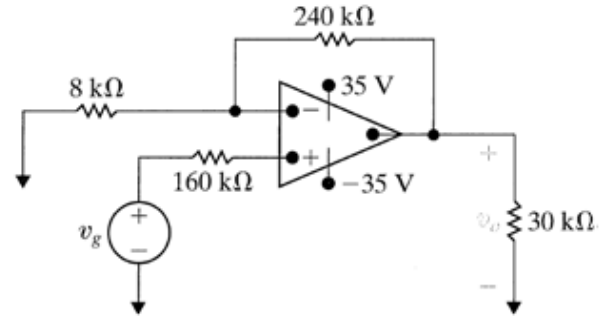

- Calculate the voltage gain ( $v_o/v_g$ ).
- Find the inverting and noninverting input voltages  $v_n$  and  $v_p$  (in millivolts) if  $v_g = 1 \text{ V}$ .
- Calculate the difference ( $v_p - v_n$ ) in microvolts when  $v_g = 1 \text{ V}$ .
- Find the current drain in picoamperes on the signal source  $v_g$  when  $v_g = 1 \text{ V}$ .
- Repeat (a)–(d) assuming an ideal op amp.

$$[a] \frac{v_n}{8000} + \frac{v_n - v_g}{600,000} + \frac{v_n - v_o}{240,000} = 0 \quad \text{or} \quad 78.5v_n - 2.5v_o = v_g$$

$$\frac{v_o}{30,000} + \frac{v_o - v_n}{240,000} + \frac{v_o - 100,000(v_p - v_n)}{5000} = 0$$

$$57v_o - v_n - 48 \times 10^5(v_p - v_n) = 0$$

$$v_p = v_g + \frac{(v_n - v_g)(160)}{600} = (11/15)v_g + (4/15)v_n$$

$$57v_o - v_n - 48 \times 10^5[(11/15)v_g - (11/15)v_n] = 0$$

$$57v_o + 3,520,000v_n = 3,520,000v_g$$

$$\Delta = \begin{vmatrix} 78.5 & -2.5 \\ 3.52 \times 10^6 & 57 \end{vmatrix} = 8,804,474.5$$

$$N_o = \begin{vmatrix} 78.5 & v_g \\ 3.52 \times 10^6 & 3.52 \times 10^6 v_g \end{vmatrix} = 272.8 \times 10^6 v_g$$

$$v_o = \frac{N_o}{\Delta} = 30.98v_g; \quad \frac{v_o}{v_g} = 30.98$$

$$[b] N_1 = \begin{vmatrix} v_g & -2.5 \\ 3.52 \times 10^6 v_g & 57 \end{vmatrix} = 8,800,057v_g$$

$$v_n = \frac{N_1}{\Delta} = 0.9995v_g; \quad v_n = 999.5 \text{ mV}$$

$$v_p = (11/15)(1000) + (4/15)(999.5) = 999.87 \text{ mV}$$

$$[c] v_p - v_n = 367.94 \mu\text{V}$$


$$[d] i_g = \frac{(1000 - 999.87)10^{-3}}{160 \times 10^3} = 836.22 \text{ pA}$$

$$[e] \frac{v_g}{8} + \frac{v_g - v_o}{240} = 0, \quad \text{since } v_n = v_p = v_g$$

$$\therefore v_o = 31v_g, \quad \frac{v_o}{v_g} = 31$$

$$v_n = v_p = 1 \text{ V}; \quad v_p - v_n = 0 \text{ V}; \quad i_g = 0 \text{ A}$$

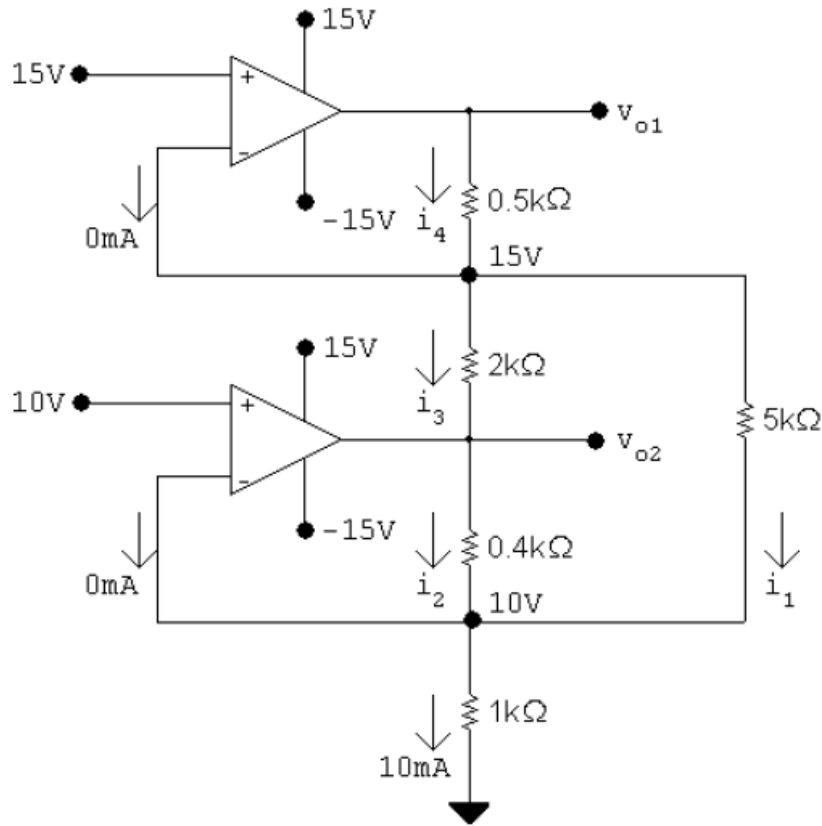3. Problem 5.39 in Nilsson. ( $v_{o1}$  is slightly under 16 V)



$$i_1 = \frac{15 - 10}{5000} = 1 \text{ mA}$$

$$i_2 + i_1 + 0 = 10 \text{ mA}; \quad i_2 = 9 \text{ mA}$$

$$v_{o2} = 10 + (400)(9) \times 10^{-3} = 13.6 \text{ V}$$

$$i_3 = \frac{15 - 13.6}{2000} = 0.7 \text{ mA}$$

$$i_4 = i_3 + i_1 = 1.7 \text{ mA}$$

$$v_{o1} = 15 + 1.7(0.5) = 15.85 \text{ V}$$