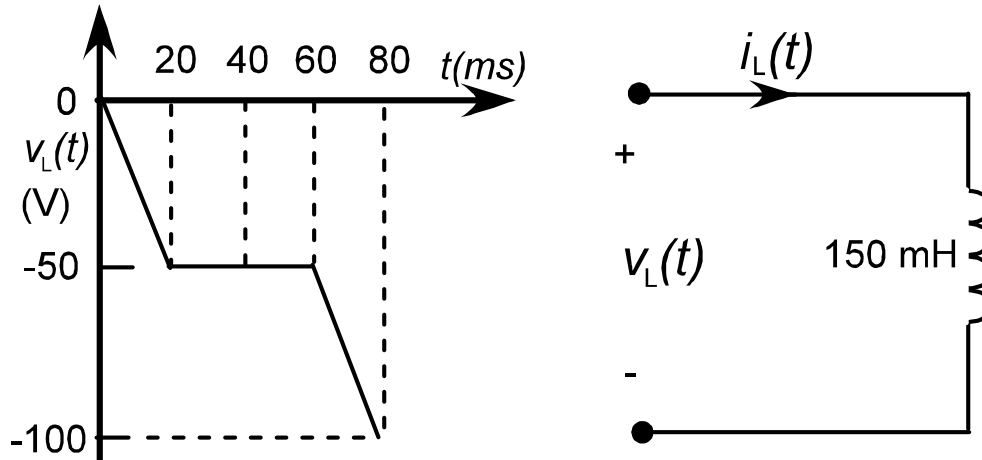


Homework Set #25
DUE Monday, May 15, 2017

1. Consider the voltage waveform shown in the graph below left:



Suppose the voltage is applied across the 150 mH inductor, find the instantaneous current through the inductor and total energy stored at $t = 40$ ms ($i_L(40$ ms) & $w_L(40$ ms)) if the initial current is zero.

$$v_L(t) = L_{eq} \frac{di_L}{dt} \quad \text{and} \quad i_L(t) = \frac{1}{L_{eq}} \int v_L dt$$



$$\int v(t) dt = 0.5 \times 20 \times 10^{-3} \times (-50) + 20 \times 10^{-3} \times (-50) = -1.5 \text{ Vs} \quad @ t = 40 \text{ ms}$$

$$\boxed{i_L(40 \text{ ms}) = -10 \text{ A}}$$

$$w_L(t) = 0.5 \times L_{eq} \times i^2 = 0.5 \times 0.15 \times (-10)^2$$

$$\boxed{w_L(40 \text{ ms}) = 7.5 \text{ J}}$$

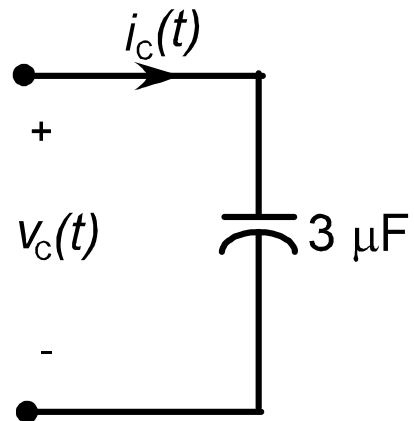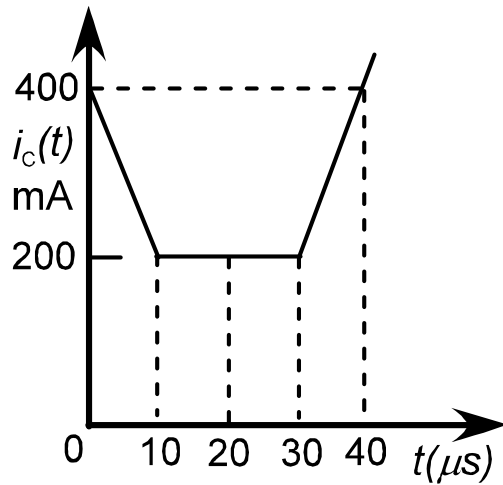2. Consider the current waveform shown in the graph below left:



Suppose the current is applied to the $3 \mu\text{F}$ capacitor, find the instantaneous voltage across the capacitor and total energy stored at $t = 25 \mu\text{s}$ ($v_c(25\mu\text{s})$ & $w_c(25\mu\text{s})$) if the initial voltage is zero.

$$i_c(t) = C_{eq} \frac{dv_c}{dt} \quad \text{and} \quad v_c(t) = \frac{1}{C_{eq}} \int i_c dt$$

$$\int i(t) dt = 0.5 \times 10 \times 10^{-6} \times 200 \times 10^{-3} + 200 \times 10^{-3} \times 25 \times 10^{-6} = 6 \mu\text{As} \quad @ t = 25 \mu\text{s}$$

$$\boxed{v_c(25\mu\text{s}) = 2 \text{ V}}$$

$$w(t) = 0.5 \times C_{eq} \times v^2 = 0.5 \times 3 \times 10^{-6} \times 2^2$$

$$\boxed{w_c(50\mu\text{s}) = 6 \mu\text{J}}$$