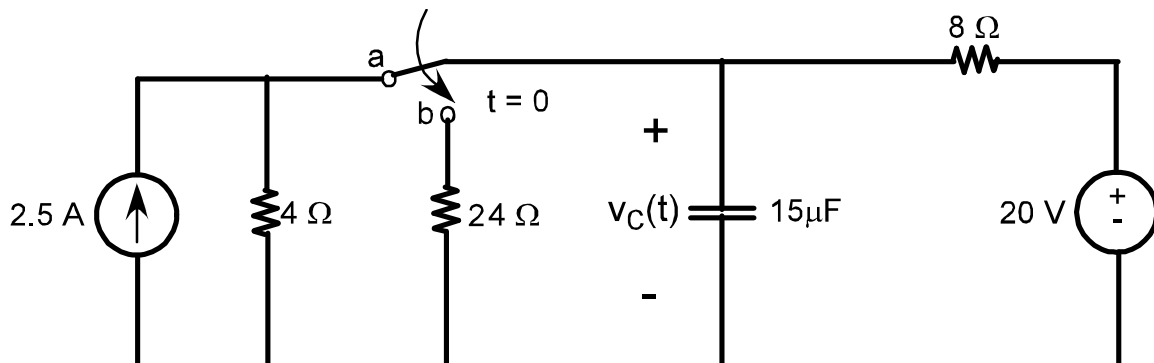


Homework Set #26
DUE Tuesday, May 16, 2017

1. In the circuit below, the switch is moved instantaneously from a to b at $t = 0$. Determine:
- Initial and final voltages across the capacitor.
 - The time-constant, τ
 - $v_C(t)$ and $i_C(t)$.



Since the switch has been closed for a long time, the capacitor has become fully charged before the switch is opened and is an open-circuit. Convert the current source to a Thevenin 10 V in series with 4 Ω to give a circulating current of:

$$I_{\text{cir}} = \frac{20 - 10}{8 + 4} = 0.8333 \text{ A}$$

$$\therefore v_C(0^+) = v_C(0^-) = 20 - 8 \times 0.8333 = 13\frac{1}{3} \text{ V}$$

i.e. the initial voltage, $V_0 = 13\frac{1}{3} \text{ V}$

For $t > 0$, the capacitor becomes an open-circuit in steady-state and V_f is given by the voltage divider relationship:

$$V_f = 20 \frac{24}{8 + 24} = 15 \text{ V}$$

The Thevenin resistance seen by C is 6 Ω , so the time constant is:

$$\tau = RC = 15 \times 10^{-6} \times 6 = 90 \mu\text{s}$$


Since: $v_C(t) = (V_0 - V_f)e^{-t/\tau} + V_f = (13.33 - 15)e^{-11111t} + 15 = 15 - 1.667e^{-11111t}$

Then: $v_C(t) = 15 - 1.667e^{-11111t}$

$$i_C(t) = C_{\text{eq}} \frac{dv_C}{dt} = 15 \times 10^{-6} \times (-1.667) \times (-11111)e^{-11111t}$$

And: $i_C(t) = 277.8e^{-11111t} \text{ mA}$

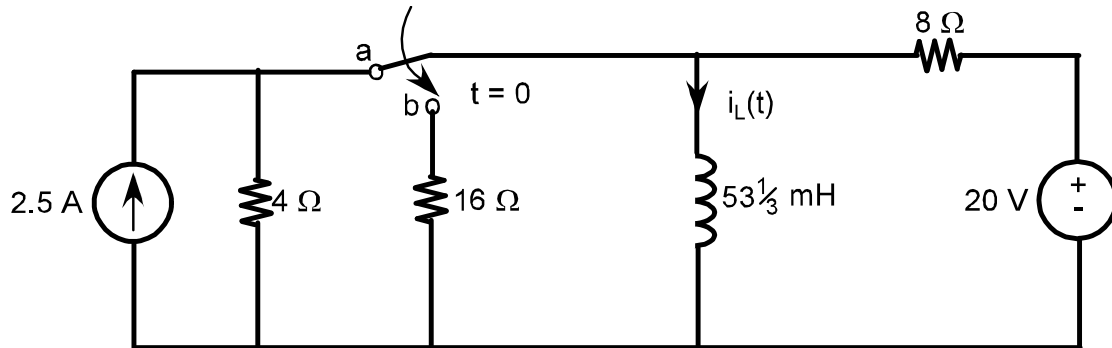2. In the circuit below, the switch is moved instantaneously from a to b at $t = 0$. Determine:
- Initial and final currents through the inductor.
 - The time-constant, τ
 - $i_L(t)$ and $v_L(t)$.



Since the switch has been closed for a long time, the inductor has become fully energized before the switch is opened and is a short-circuit.

$$\therefore i_L(0^+) = i_L(0^-) = 2.5 + 2.5 = 5 \text{ A}$$

i.e. the initial current, $i_0 = 5 \text{ A}$

For $t > 0$, the inductor becomes a short-circuit in steady-state and $I_f = 2.5 \text{ A}$.

The Thevenin resistance seen by L is $5\frac{1}{3} \Omega$, so the time constant is:

$$\tau = \frac{53.33 \times 10^{-3}}{5.333} = 10 \text{ ms}$$

Since: $i_L(t) = (I_0 - I_f)e^{-t/\tau} + I_f = (5 - 2.5)e^{-100t} + 2.5 = 2.5 + 2.5e^{-100t}$

Then: $i_L(t) = 2.5(1 + e^{-100t}) \text{ A}$

$$v_L(t) = L_{eq} \frac{di_L}{dt} = 0.05333 \times (-2.5 \times 100e^{-100t})$$

And: $v_L(t) = -13.33e^{-100t} \text{ V}$