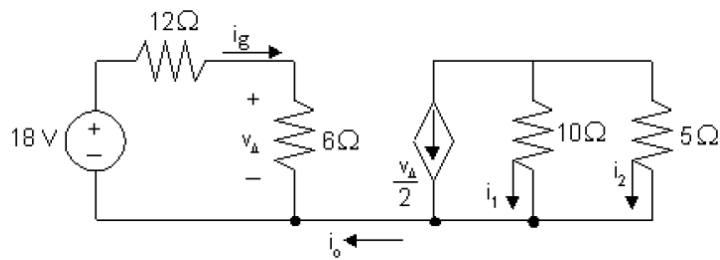


**Homework Set #5**  
**DUE Monday, March 20, 2017**

1. Problem 2.35 (answer:  $i_2 = -2$  A)

[a]  $i_o = 0$  because no current can exist in a single conductor connecting two parts of a circuit.

[b]





$$18 = (12 + 6)i_g \quad i_g = 1 \text{ A}$$

$$v_{\Delta} = 6i_g = 6\text{V} \quad v_{\Delta}/2 = 3 \text{ A}$$

$$10i_1 = 5i_2, \text{ so } i_1 + 2i_1 = -3 \text{ A; therefore, } i_1 = -1 \text{ A}$$


[c]  $i_2 = 2i_1 = -2$  A.

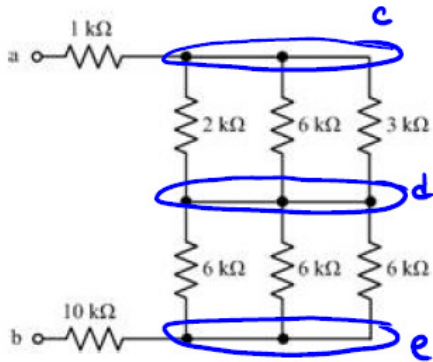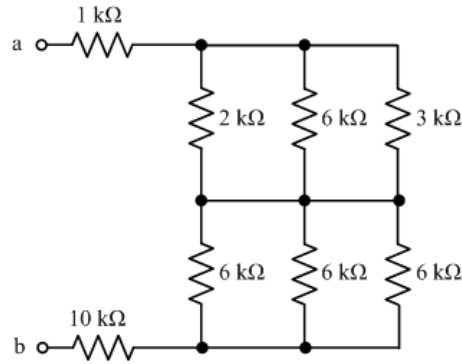2. For both circuits shown below, reduce to a single resistor at terminals a and b.  
a)



$$2k \parallel 6k \parallel 3k = 1k \Omega$$

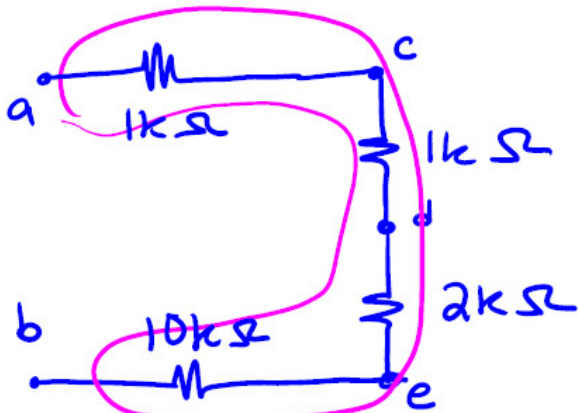
$$6k \parallel 6k \parallel 6k = 2k \Omega$$



in series
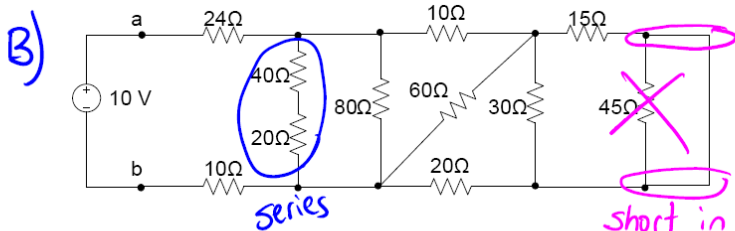
$$R_{eq} = (1 + 1 + 2 + 10)k = 14k \Omega$$






Series  
 $40 + 20 = 60$


short in || w/  
 a resistor  
 shorts out the  
 resistor
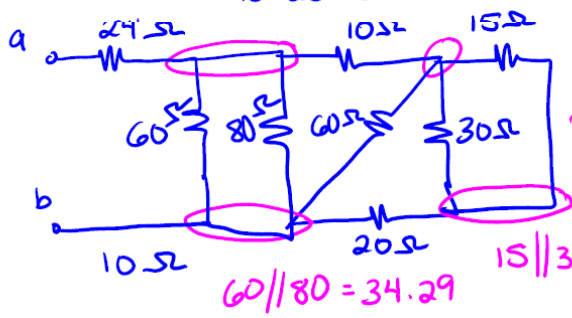
$$R_{eq} = \left( \frac{1}{45} + \frac{1}{0} \right)^{-1} = 0$$




$$60 \parallel 80 = 34.29$$


$$15 \parallel 30 = 10 \Omega$$

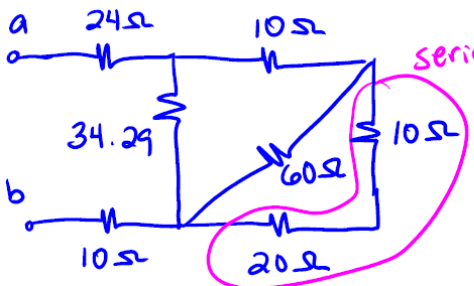


Series  $10 + 20 = 30$

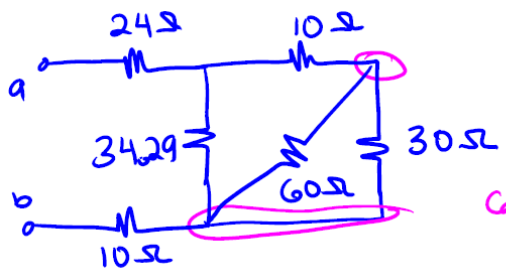


$$60 \parallel 30 = 20 \Omega$$

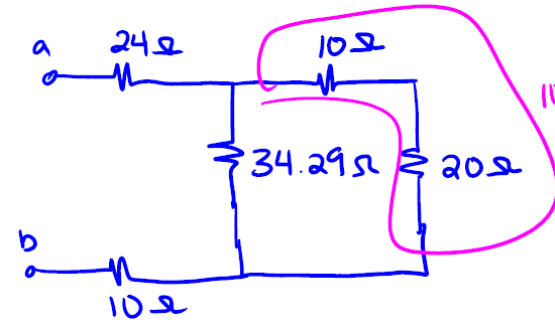

$$10 + 20 = 30$$

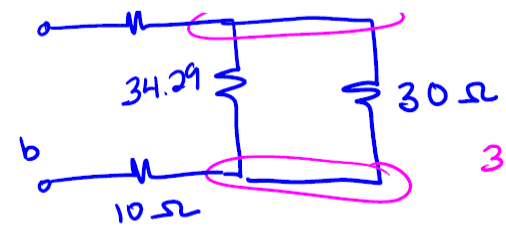


$$34.29 \parallel 30 = 16$$

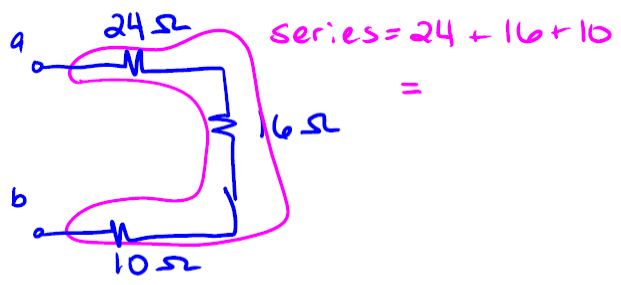

Series =  $24 + 16 + 10$   
 =

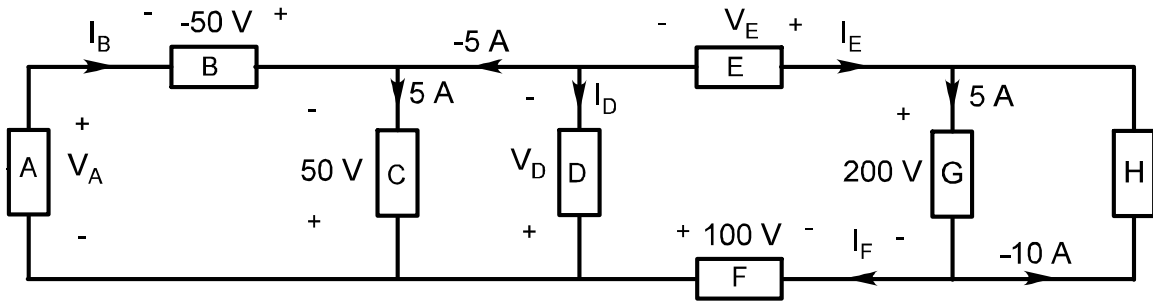3. Complete the table below. Observe the Passive Sign Convention.



Element	Voltage	Current	Power	Consumed/Produced?
A	0	+10	0	-
B	-50	+10	+500	C
C	+50	+5	-250	P
D	+50	-10	+500	C
E	-150	+15	-2250	P
F	+100	+15	-1500	P
G	+200	+5	+1000	C
H	+200	-10	+2000	C