
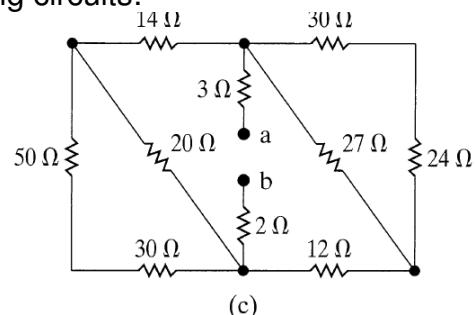
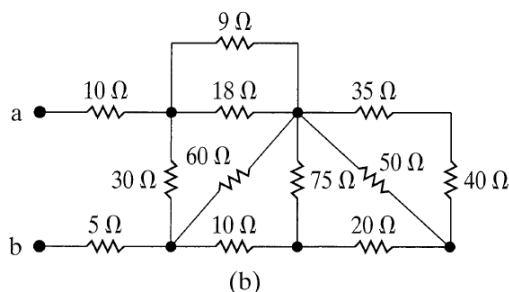


Homework Set #6
DUE Tuesday, March 21, 2017 – COB

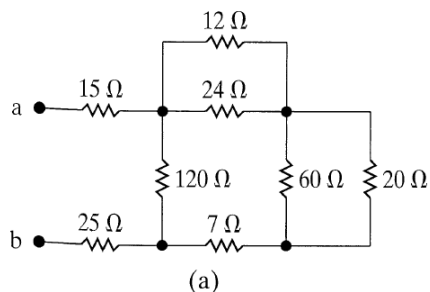1. Find the equivalent resistance (R_{ab}) for each of the following circuits:




$$\begin{aligned}
 \text{[a]} \quad 60 \parallel 20 &= 1200/80 = 15 \Omega & 12 \parallel 24 &= 288/36 = 8 \Omega \\
 15 + 8 + 7 &= 30 \Omega & 30 \parallel 120 &= 3600/150 = 24 \Omega \\
 R_{ab} &= 15 + 24 + 25 = 64 \Omega
 \end{aligned}$$


$$\begin{aligned}
 \text{[b]} \quad 35 + 40 &= 75 \Omega & 75 \parallel 50 &= 3750/125 = 30 \Omega \\
 30 + 20 &= 50 \Omega & 50 \parallel 75 &= 3750/125 = 30 \Omega \\
 30 + 10 &= 40 \Omega & 40 \parallel 60 + 9 \parallel 18 &= 24 + 6 = 30 \Omega \\
 30 \parallel 30 &= 15 \Omega & R_{ab} &= 10 + 15 + 5 = 30 \Omega
 \end{aligned}$$

$$\begin{aligned}
 \text{[c]} \quad 50 + 30 &= 80 \Omega & 80 \parallel 20 &= 16 \Omega \\
 16 + 14 &= 30 \Omega & 30 + 24 &= 54 \Omega \\
 54 \parallel 27 &= 18 \Omega & 18 + 12 &= 30 \Omega \\
 30 \parallel 30 &= 15 \Omega & R_{ab} &= 3 + 15 + 2 = 20 \Omega
 \end{aligned}$$

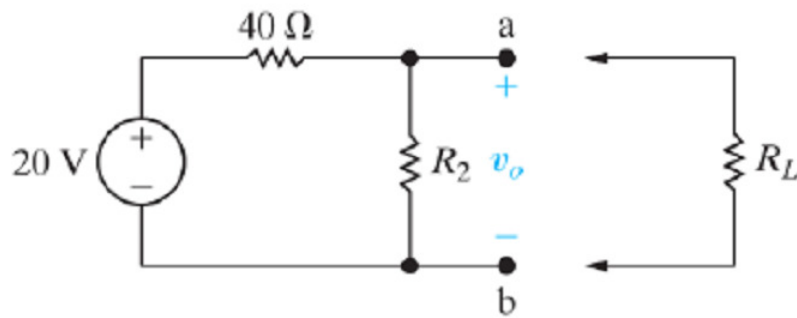2. The output of the voltage divider is 4 V when R_L is not connected. When R_L is connected it drops to 3 V. Find R_L .




No-load circuit

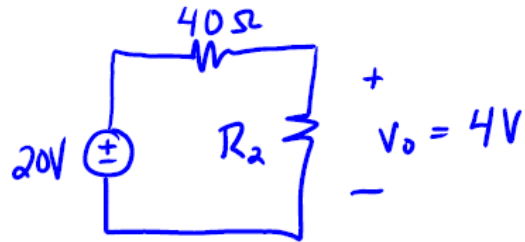

$$\text{voltage div) } 4 = 20 \left(\frac{R_2}{40 + R_2} \right)$$

$$\Rightarrow R_2 = 10$$

loaded circuit

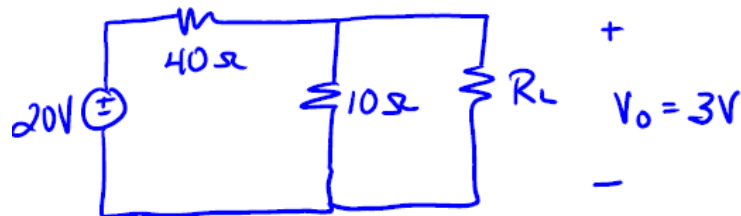


$$3 = 20 \frac{10 \parallel R_L}{40 + 10 \parallel R_L}$$

$$\frac{3}{20} = \frac{10 R_L}{(10 + R_L)} \cdot \frac{1}{\left(40 + \frac{10 R_L}{10 + R_L}\right)}$$

$$\Rightarrow \boxed{R_L = 24 \Omega}$$

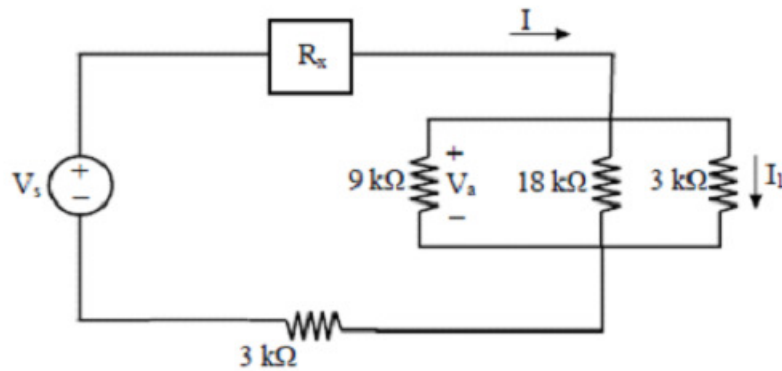
3.

- Find the equivalent resistance (R_{eq}) for the three resistors in parallel.
- Calculate the voltage V_a if $V_s = 10$ Volts and $R_x = 5$ k Ω .
- Parameters in the circuit are changed such that V_s and R_x are not known and $I_1 = 3$ mA. Calculate the current I .



a) $R_{eq} = 9k \parallel 18k \parallel 3k = 2k\Omega$

b) equivalent ckt

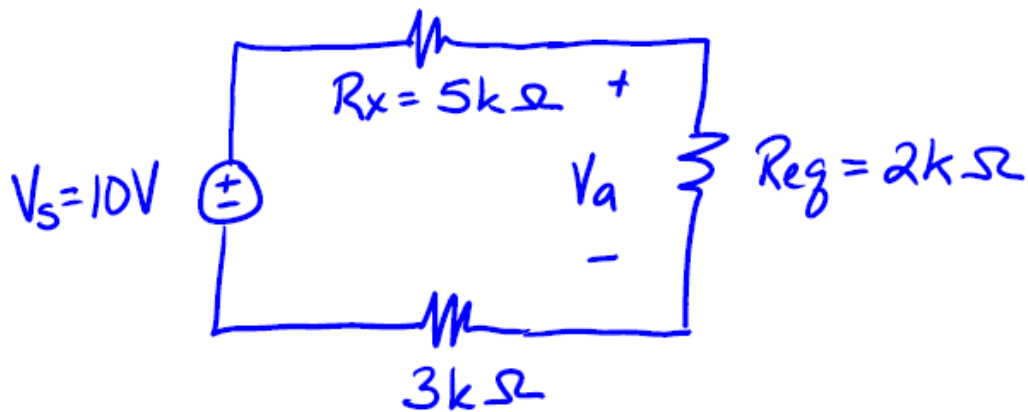


using voltage divider:

$$V_a = \frac{V_s \cdot R_{eq}}{R_x + R_{eq} + 3k}$$

$$= \frac{(10)(2k)}{5k + 2k + 5k} = 1\frac{2}{3}$$

$$V_a = 1\frac{2}{3} \text{ V}$$

c) Find I and I_1 ,

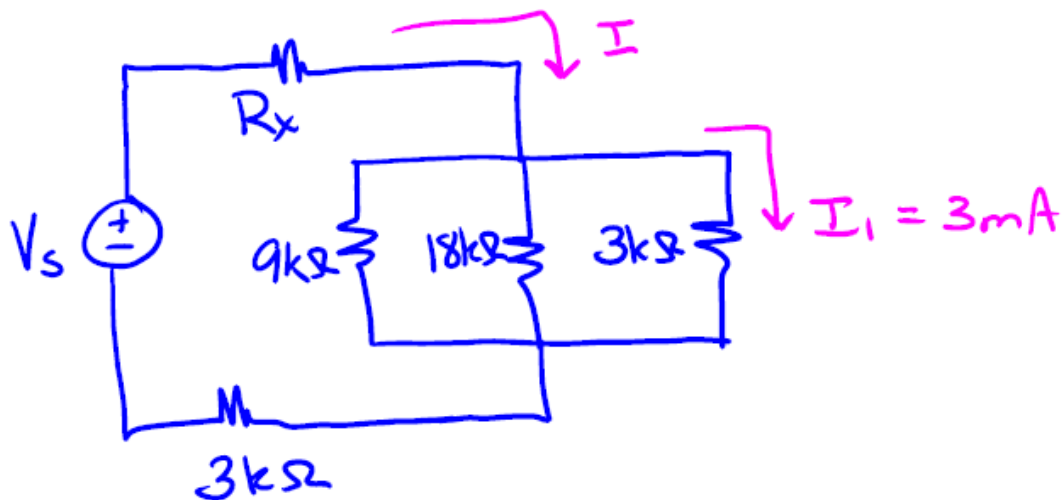

use current divider

$$I_1 = \frac{I (9k // 18k // 3k)}{3k}$$

$$I = \frac{(3m)(3k)}{(2k)}$$

$$I = 4.5mA$$