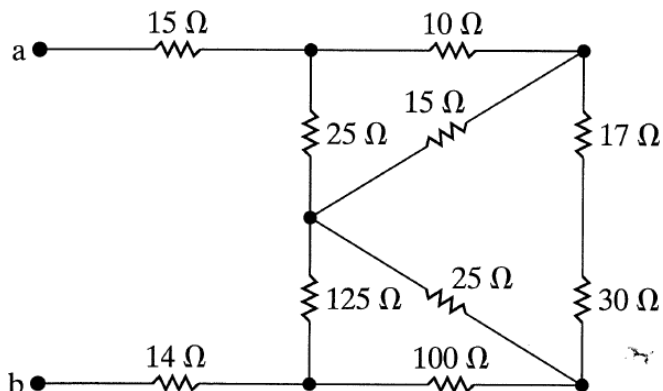


**Homework Set #9**  
**DUE Tuesday, March 28, 2017**

1. Determine the resistance  $R_{ab}$  in the following circuit:




Replace the upper and lower deltas with the equivalent wyes:

$$R_{1U} = \frac{(25)(10)}{50} = 5 \Omega; R_{2U} = \frac{(10)(15)}{50} = 3 \Omega; R_{3U} = \frac{(25)(15)}{50} = 7.5 \Omega$$

$$R_{1L} = \frac{(125)(25)}{250} = 12.5 \Omega; R_{2L} = \frac{(25)(100)}{250} = 10 \Omega; R_{3L} = \frac{(125)(100)}{250} = 50 \Omega$$

The resulting circuit is shown below:

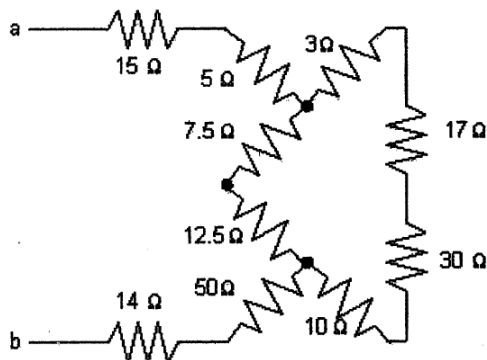


Now make series and parallel combinations of the resistors:

$$(7.5 + 12.5) \parallel (3 + 17 + 30 + 10) = 20 \parallel 60 = 15 \Omega$$

$$R_{ab} = 15 + 5 + 15 + 50 + 14 = 99 \Omega$$

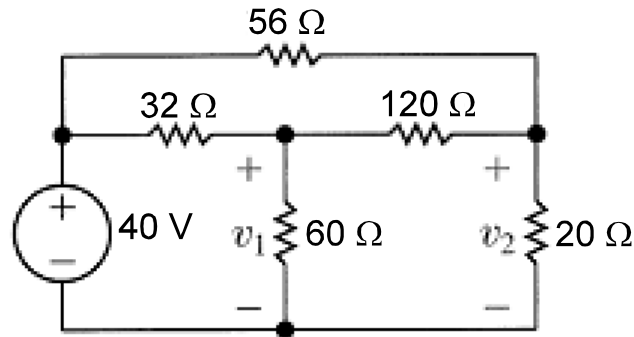2. a) Use Y – Δ Transformations (or Δ – Y) to obtain  $v_1$  &  $v_2$  in the following circuit.  
 b) Check your result using Nodal Analysis.




(HINT: Begin by transforming the Δ-connected 60Ω – 120Ω – 20Ω resistors into Y and then reduce the circuit to a single resistor and get the source current.)

Take the delta made-up of  $R_c = 120\ \Omega$ ,  $R_b = 60\ \Omega$ , and  $R_a = 20\ \Omega$  and convert to wye as follows:

$$R_1 = \frac{(60)(120)}{20 + 60 + 120} = 36\ \Omega, \quad R_2 = \frac{(120)(20)}{20 + 60 + 120} = 12\ \Omega, \quad R_3 = \frac{(60)(20)}{20 + 60 + 120} = 6\ \Omega$$

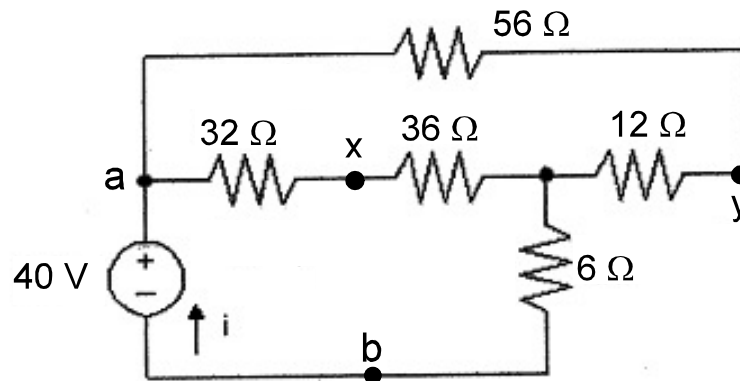This conversion leads to the following circuit:



The 56 Ω and 12 Ω are in series to give 68 Ω, while the 32 Ω and 36 Ω are also in series to give 68 Ω. Both 68 Ω resistors are in parallel to give 34 Ω, which is in series with the 6 Ω, so  $R_{ab} = 40\ \Omega$ .


The current drawn from the source is: 
$$i = \frac{40}{40} = 1\ A$$

Use current division to obtain the currents flowing in the 56 Ω and the 32 Ω resistors:


$$i_{56} = 0.5\ A, \quad i_{32} = 0.5\ A \quad (\text{This is coincidence})$$

$$v_1 = v_{xb} = 40 - 32 \times 0.5 = 24\ V \quad v_2 = v_{yb} = 40 - 56 \times 0.5 = 12\ V$$

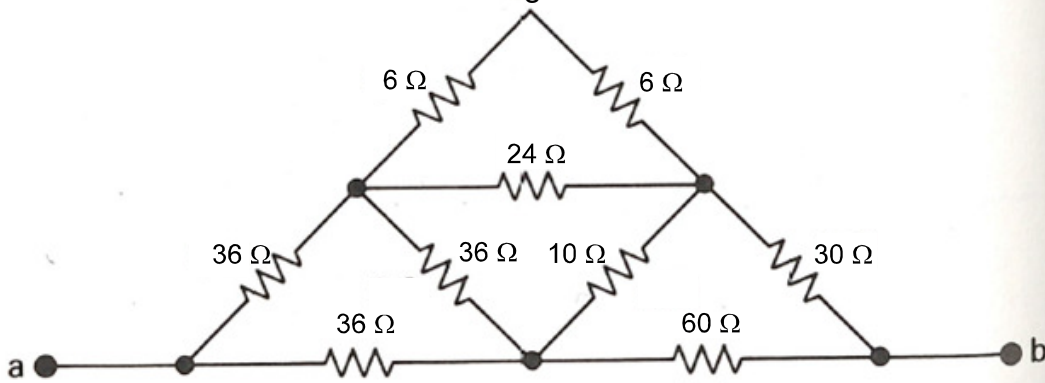3. Determine the resistance  $R_{ab}$  in the following circuit:




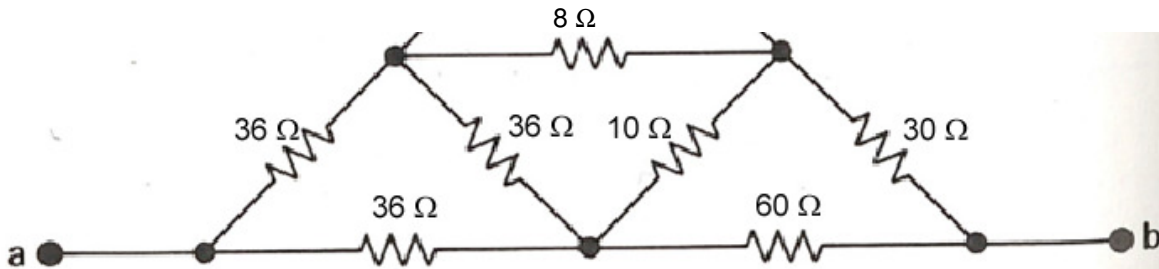The top two 6Ω resistors are in series and the resulting 12Ω is in parallel with the 24Ω below. This means the top three resistors can be replaced by a single 8Ω resistor to give:




The lower triangles are deltas (upside-down) they can be replaced by upside-down wyes.
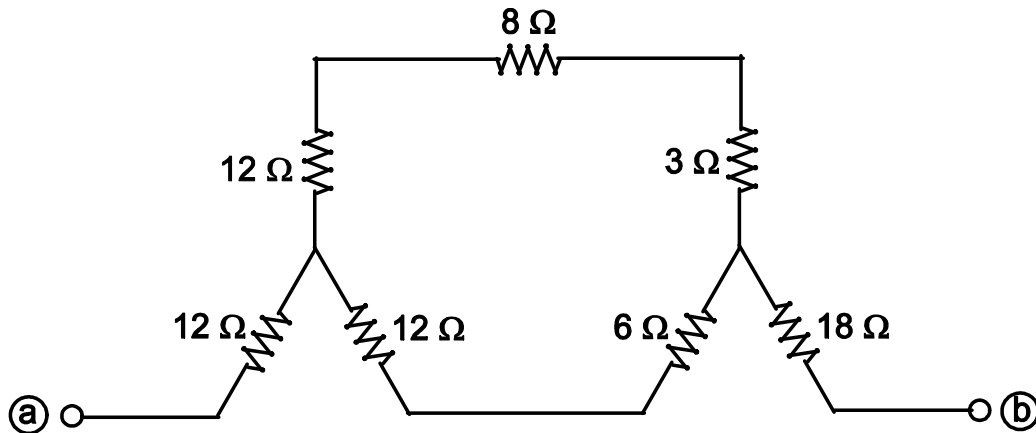
$$R_1 = \frac{(30)(60)}{10 + 30 + 60} = 18\Omega; \quad R_2 = \frac{(60)(10)}{10 + 30 + 60} = 6\Omega; \quad R_3 = \frac{(30)(10)}{10 + 30 + 60} = 3\Omega$$



Combining resistors gives:

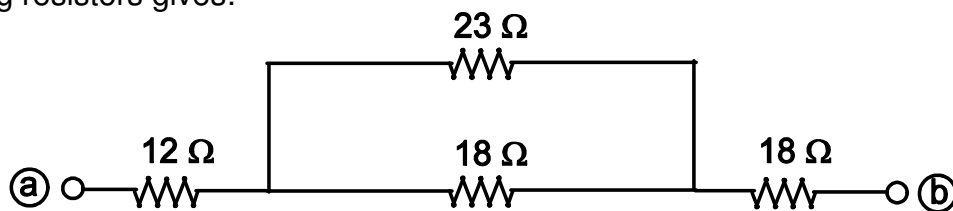

The 23Ω and 18Ω are in parallel to give 10.1Ω, which is in series with the 12Ω and the 18Ω resulting in:

$$R_{ab} = 40.1\Omega$$