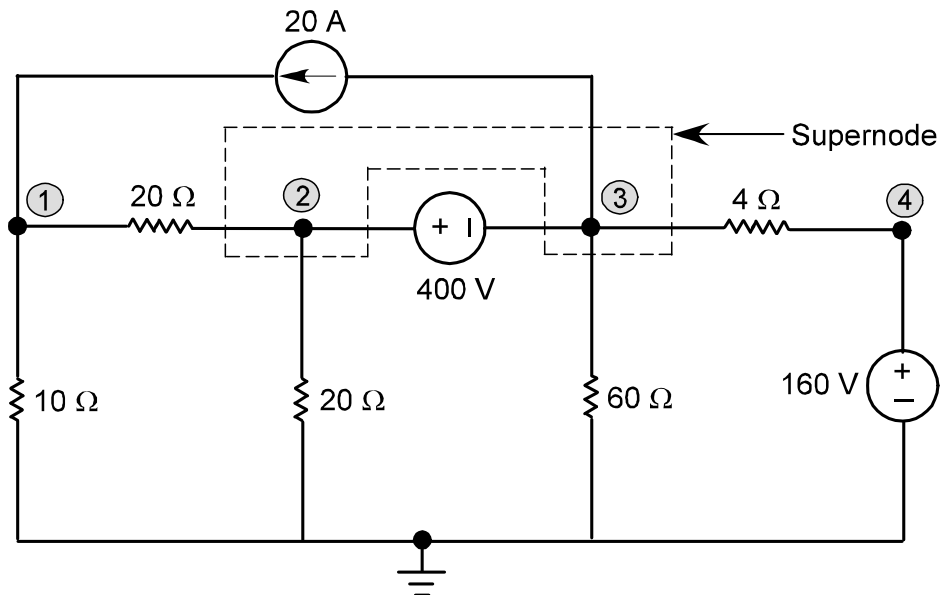


**Homework Set #12**  
**DUE Tuesday, April 4, 2017**

1.  
 a) Write the nodal equations needed to solve for all nodal voltages in the following circuit. **Do not attempt to solve these equations.**



- b) Assume the answer to part (a) is the following set of equations (NOTE: this is **not** the answer to part (a)). Solve them for all nodal voltages.


$$V_2 = V_3 + 600 \quad \text{and} \quad V_4 = 240$$

$$\frac{V_1}{10} + \frac{V_1 - V_2}{20} - 15 = 0$$

$$\frac{V_2 - V_1}{20} + \frac{V_2}{20} + 15 + \frac{V_3}{60} + \frac{V_3 - V_4}{4} = 0$$

2.

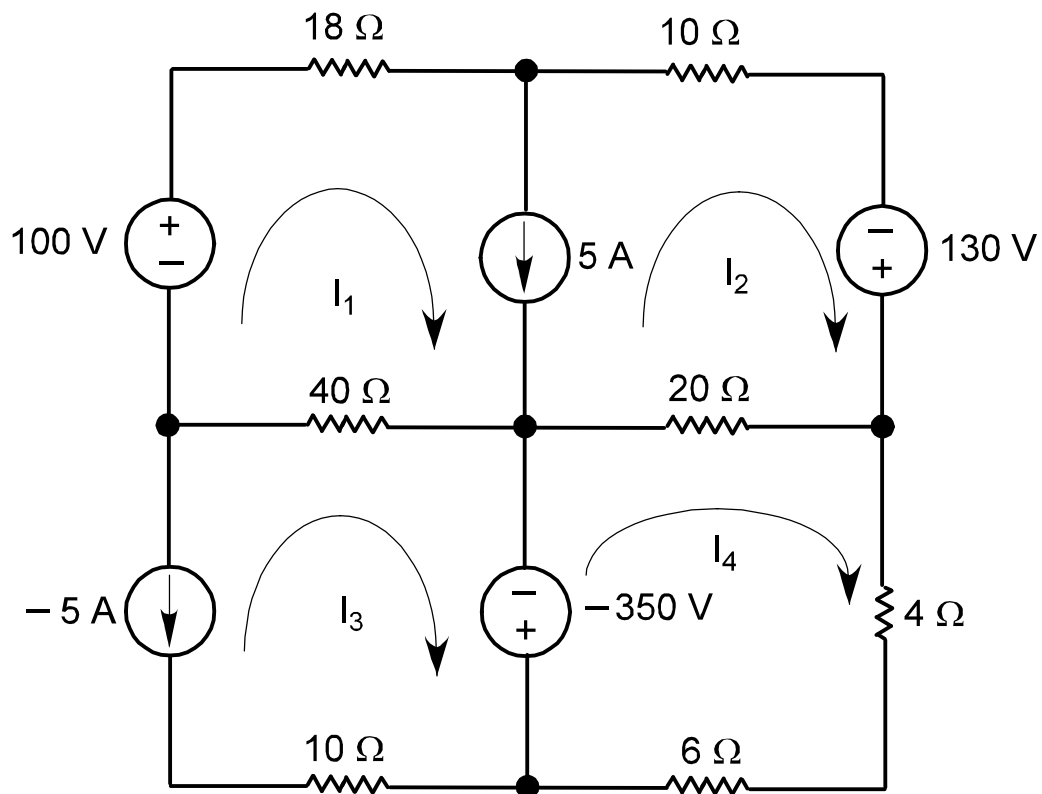- a) Write the mesh equations needed to solve for all mesh currents in the following circuit. **Do not attempt to solve these equations.**



- b) Assume part of the answer to part (a) is  $I_4 = 10$  A (NOTE: this is **not** the answer to part (a)). Determine the power **produced** by the -350 V source.

3. For the following circuit:
- determine all nodal voltages using nodal analysis, and
  - determine all mesh currents using mesh analysis.

