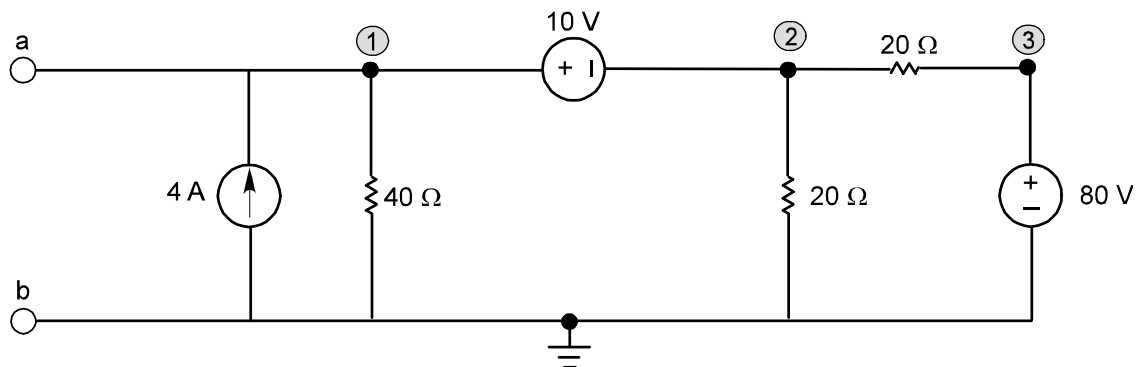



Homework Set #13
DUE Friday, April 3, 2017

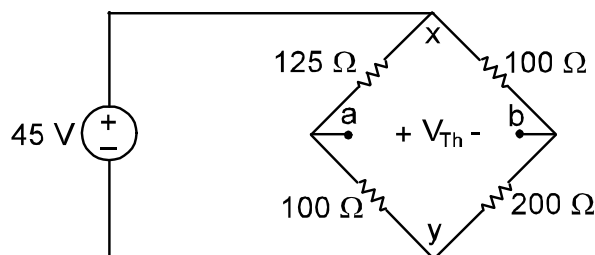1. For the circuit shown below:




a)

- Write and solve the nodal equation needed to determine V_1 .
- b) De-activate the sources and determine the resistance seen by terminals a—b, when they are open-circuited.
- c) Draw the Thevenin Equivalent at terminals a—b.
 (NOTE: you can use source transforms to check this result.)
2. Determine the Thevenin equivalent circuit across terminals a—b for the Wheatstone Bridge shown below:



(NOTE: When you de-activate the 45 V source x & y become the same node, so some resistors are in parallel when you look into a-b.)

3. For the circuit shown below:

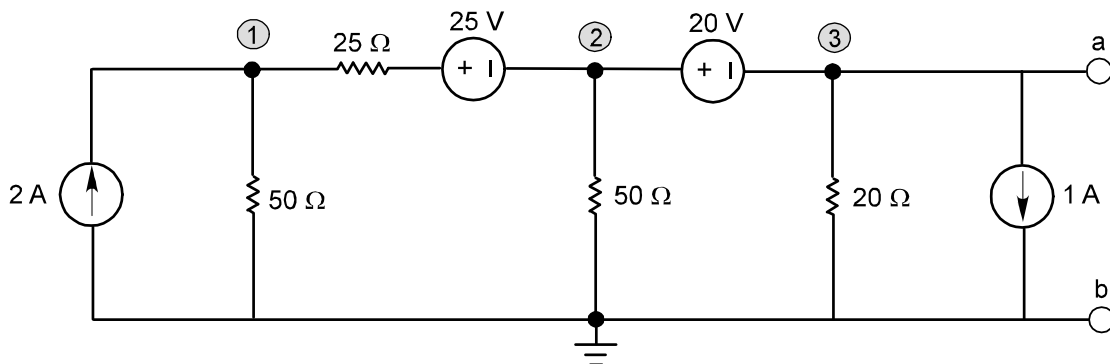

a)

- Use source transforms to determine the Thevenin Equivalent at terminals a—b.
 (i.e. Draw the Thevenin Equivalent looking into terminals a—b.)
- b) Assume the answer to part (a) is $V_{Th} = 12 \text{ V}$ and $R_{Th} = 8 \text{ } \Omega$ (NOTE: this is *not* the answer to part (a)) and determine the power dissipated in a $127.5 \text{ } \Omega$ load resistor connected across a—b.