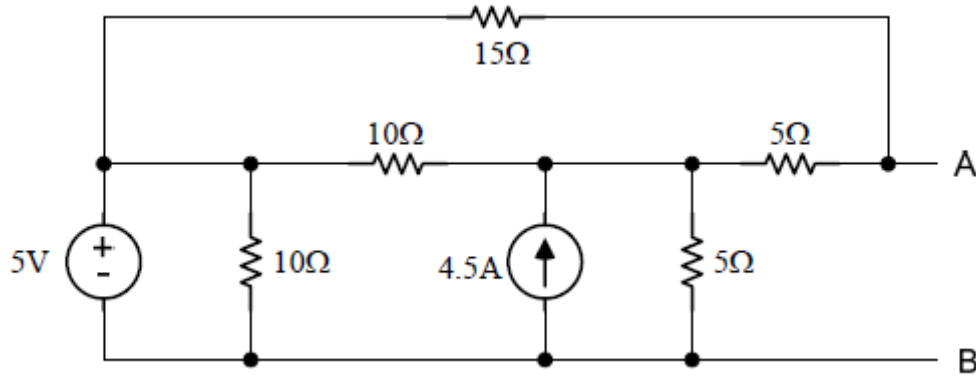


Homework Set #14
DUE Tuesday, April 18, 2017

1. Complete the following analysis for the circuit shown below:




- Find the Thevenin equivalent circuit looking into terminals A-B using the “open-circuit voltage, short-circuit current” technique.
- Repeat part A using the “open circuit voltage, equivalent resistance” technique.

2. A voltmeter with a resistance of $100\text{ k}\Omega$ is used to measure the voltage v_{ab} in the circuit in Fig. P4.67.


- What is the voltmeter reading?
- What is the percentage of error in the voltmeter reading if the percentage of error is defined as $[(\text{measured} - \text{actual})/\text{actual}] \times 100$?

Figure P4.67

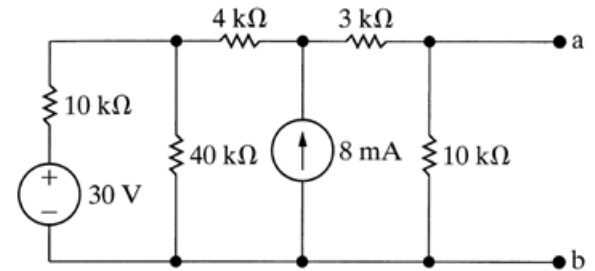

Do this by finding the Thevenin Equivalent at a – b and attaching the voltmeter to make a voltage divider.

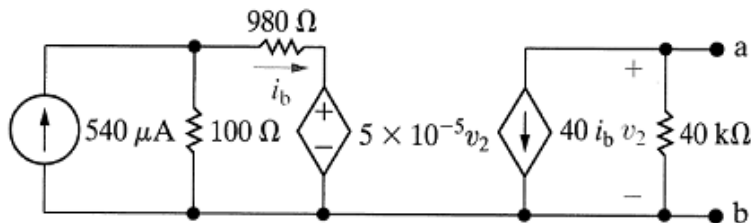3. Determine the Thevenin Equivalent at a – b for the following circuit.



Do this by finding the open-circuit voltage and short-circuit current and use them to get the Thevenin Resistance.