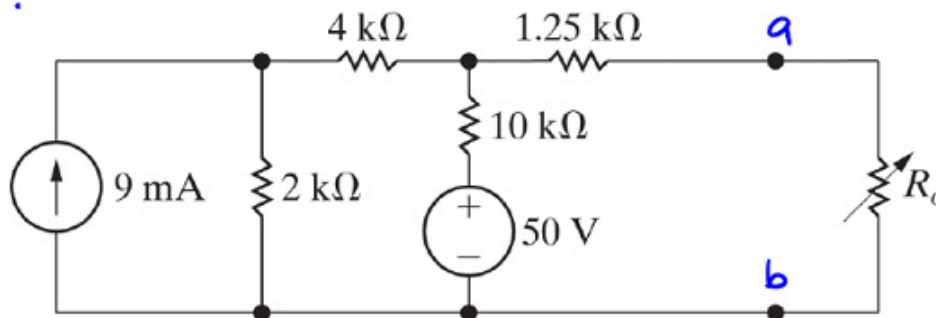


Homework Set #16
DUE Monday, April 24, 2017

1. Recall that maximum power transfer occurs when $R_L = R_{Th}$. The rheostat (R_o) is adjusted to give maximum power transfer.
- Find the value of R_o .
 - Find the maximum power that can be delivered to R_o .



2. In order to provide a graphical verification of the Maximum Power Transfer Theorem, plot (EXCEL, MATLAB or MAPLE) the power P_L extracted from this circuit (in other words, the power absorbed by a load resistor, R_L , connected across terminals A-B) as a function of the load resistance R_L as R_L is varied between $0.25 R_{Lmax}$ and $4R_{Lmax}$. Your plot should reveal that P_L is at a maximum when $R_L = R_{Lmax}$. *Hint: you found the Thevenin equivalent of this circuit in homework 14.*

