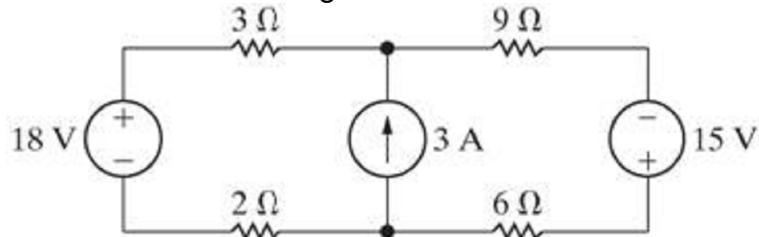


**Homework Set #17**  
**DUE Tuesday, April 25, 2017**

1. For the following circuit:



- Use the principle of linear superposition to find the current through the  $9\Omega$  resistor (positive from left to right) for each source acting alone.
  - Now compute the current in the  $9\Omega$  resistor when the three sources are activated together. Demonstrate that this result is equal to the sum of the individual current responses.
  - Compute the power in the  $9\Omega$  resistor due to each source acting alone and when the three sources are activated together. Does superposition hold for power calculations?
2. For the following circuit:
- Use the principle of superposition to find the voltage  $v$
  - Find the power dissipated in the  $20\Omega$  resistor.

