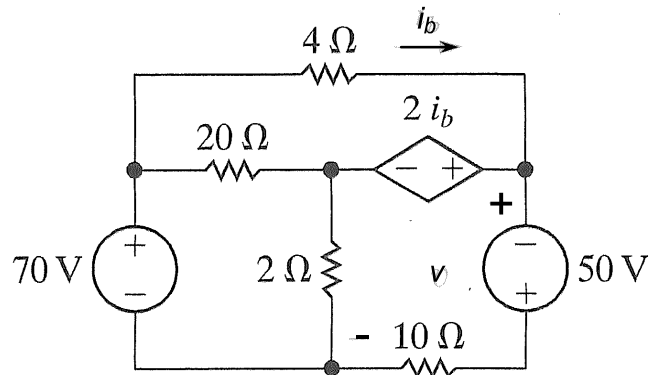


Homework Set #18
DUE Friday, April 28, 2017

1. Use superposition to find the voltage v in the following circuit. Note that it's the voltage across the 50 V source in series with the $10\ \Omega$ resistor.



2. Problem 5.1 in Nilsson.
3. Problem 5.3 in Nilsson.