

**Homework Set #21**  
**DUE Friday, May 5, 2017**

1. Design an inverting summing amplifier so that


$$v_o = -(3v_a + 5v_b + 4v_c + 2v_d).$$

If the feedback resistor ( $R_f$ ) is chosen to be  $60\text{ k}\Omega$ , draw a circuit diagram of the amplifier and specify the values of  $R_a$ ,  $R_b$ ,  $R_c$ , and  $R_d$ .

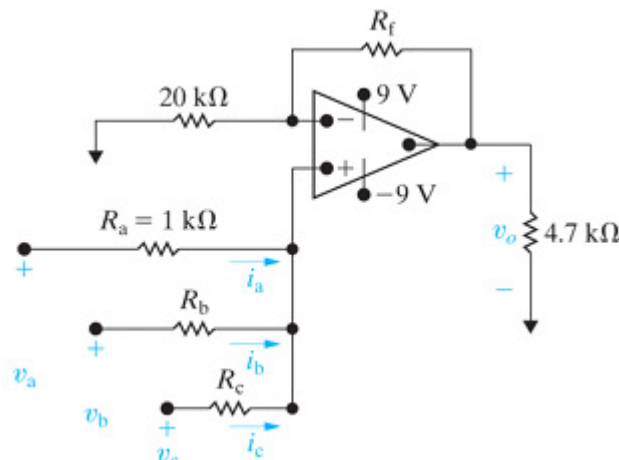2. The following circuit has to have an output voltage given by:

$$V_o = 4v_a + v_b + 2v_c$$

- Specify the numerical values of  $R_b$ ,  $R_c$ , and  $R_f$ .
- Using the values found in part (a) for  $R_f$ ,  $R_b$ , and  $R_c$ , calculate (in microamperes)  $i_a$ ,  $i_b$ , and  $i_c$  when  $v_a = 0.75\text{ V}$ ,  $v_b = 1.0\text{ V}$ , and  $v_c = 1.5\text{ V}$ .



(HINT: Use superposition to get an expression for  $V_o$  in terms of the unknown resistors. This gives you the ratios and  $R_a$  is known.)