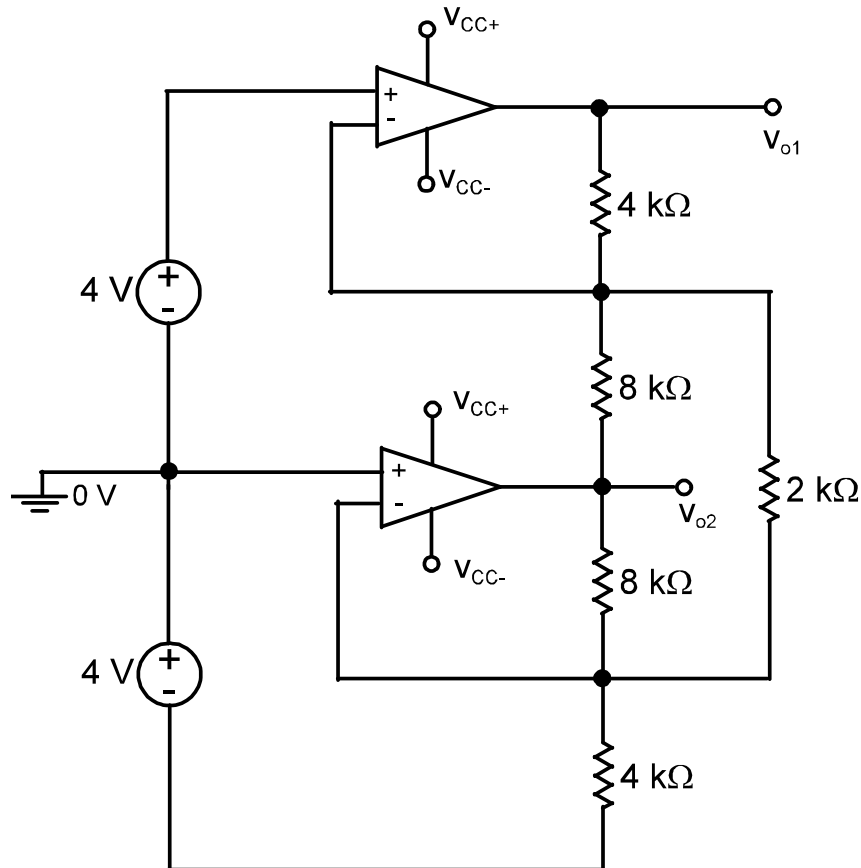



Homework Set #23
DUE Tuesday, May 9, 2017

1. Determine :
- V_{o1} & V_{o2} .
 - The minimum absolute values of V_{CC+} and V_{CC-} .



2. Design (i.e. draw the diagram and insert all parameter values) a constant current amplifier that will output 2.5 mA over its operating range and is driven from a signal that has a Thevenin equivalent of 5 V and 25 k Ω . Assume the op amp is ideal and operates in its linear range. Specify the smallest value of $\pm V_{CC}$ if the largest load resistance is 5 k Ω .

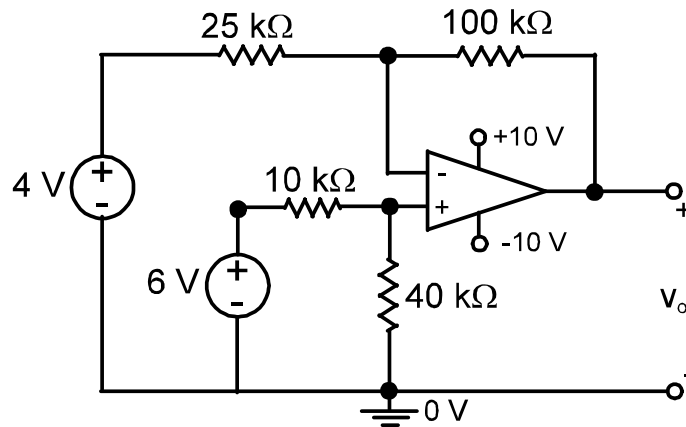3. a) Determine v_o for the following circuit. Assume the op amp and power supplies are ideal.



- b) Determine CMRR if the worst-case values of the resistors are: 22.5 k Ω for 25 k Ω , 90 k Ω for 100 k Ω , 11 k Ω for 10 k Ω , 36 k Ω for 40 k Ω .