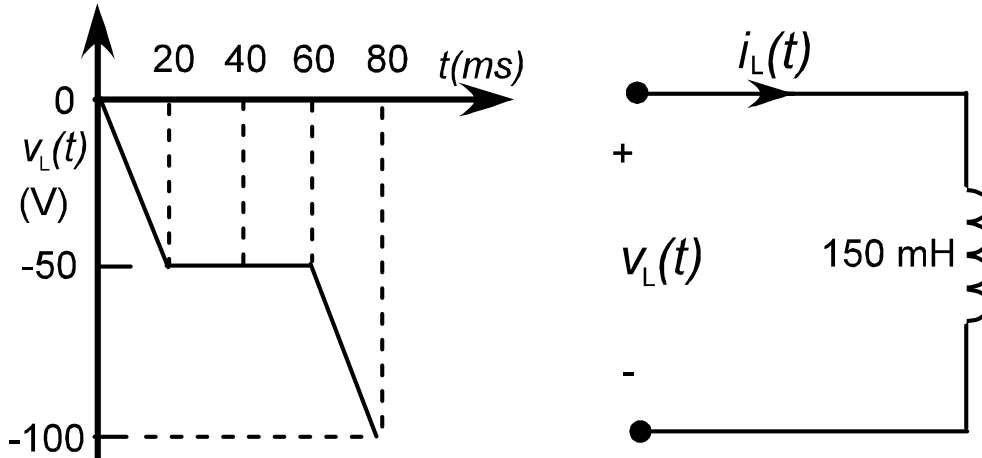



**Homework Set #25**  
**DUE Monday, May 15, 2017**

1. Consider the voltage waveform shown in the graph below left:



Suppose the voltage is applied across the 150 mH inductor, find the instantaneous current through the inductor and total energy stored at  $t = 40$  ms ( $i_L(40 \text{ ms})$  &  $w_L(40 \text{ ms})$ ) if the initial current is zero.

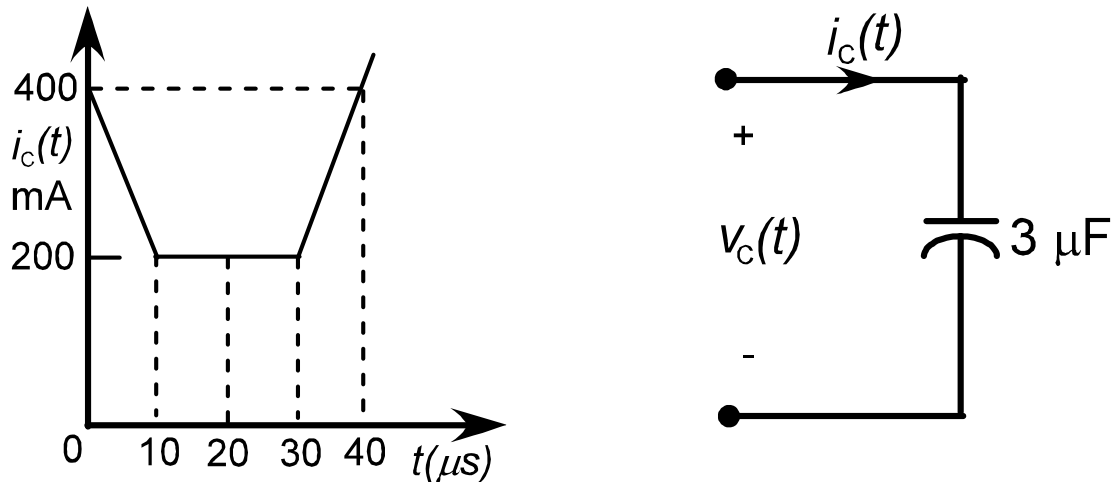2. Consider the current waveform shown in the graph below left:



Suppose the current is applied to the 3  $\mu\text{F}$  capacitor, find the instantaneous voltage across the capacitor and total energy stored at  $t = 25$   $\mu\text{s}$  ( $v_C(25 \mu\text{s})$  &  $w_C(25 \mu\text{s})$ ) if the initial voltage is zero.