
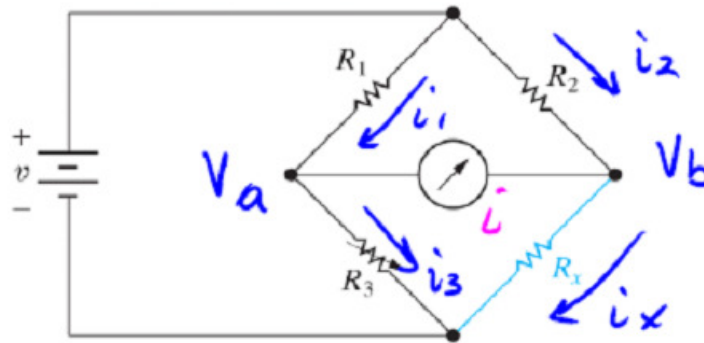


Homework Set #8
DUE Monday, March 27, 2017

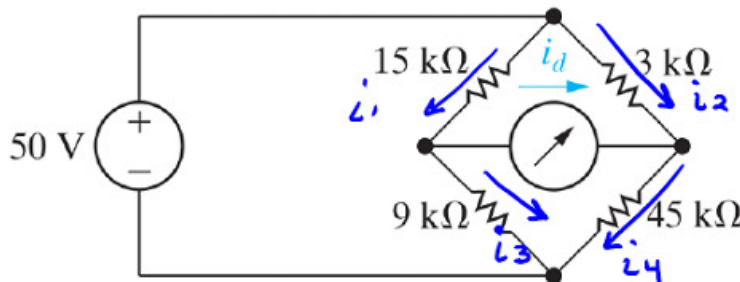1. The Wheatstone Bridge circuit shown below is energized from a 21 V source and is balanced when $R_1 = 800 \Omega$, $R_2 = 1200 \Omega$, and $R_3 = 600 \Omega$.
 - a) What is the value of R_x ?
 - b) What is the source current?
 - c) Which resistor absorbs the most power? How much power does it absorb?
 - d) Which resistor absorbs the least power? How much power does it absorb?



2. Find the detector current (i_d) if the voltage drop across the detector is zero (this means you can put resistors in parallel)



(Ans. $-3\frac{1}{3} \text{ mA}$)

3. Find the power dissipated in the 18Ω resistor.
 (HINT: $6/10=18/30$ means the bridge is balanced and the 50Ω resistor is shorted-out.)

