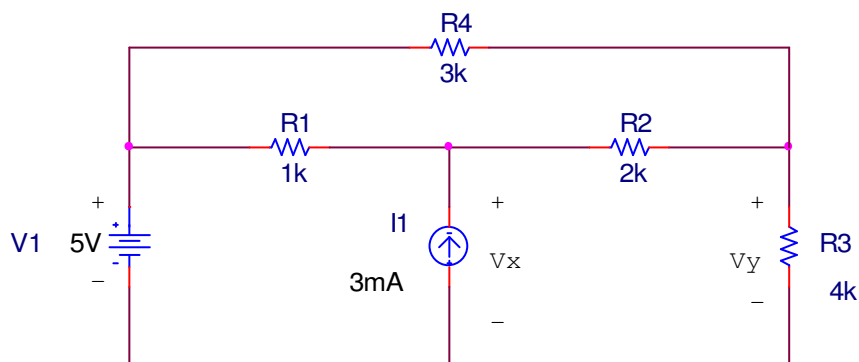



ECE203—DC Circuits Review for Test 2

Figure 1. Resistive circuit with two independent sources




1. Use the node voltage method to find V_x and V_y in the circuit of Figure 1. (Answers: $V_x = 6.91\text{V}$, $V_y = 4.73\text{ V}$)
2. Use the mesh current method to find V_x and V_y in the circuit of Figure 1. (Your results should agree with the results obtained in Problem 1.) (Answers: $V_x = 6.91\text{V}$, $V_y = 4.73\text{ V}$)
3. In the circuit of Figure 1, remove R_3 , and (a) find the Thevenin Equivalent circuit that is seen looking into the terminals where R_3 had been connected. (b) find the Norton Equivalent circuit that is seen looking into these terminals (c) Connect R_3 across the terminals each of these equivalent representations, and show that in both cases, that you still get the same value of V_y that was determined in Problems 1, 2, and 3! (Answers: $V_{th} = 6.5\text{ V}$, $R_{th} = 1.5\text{ k}$, $I_n = 4.333\text{ mA}$, $R_n = 1.5\text{ k}$, $V_y = 4.73\text{ V}$.)
4. Referring to the circuit of Figure 2, (a) use either node or mesh method (whichever is easier) to find V_y . (b) find the power absorbed by the 3 mA source and the 5 V source. (Answers: $P_{3\text{mA}} = -34\text{ mW}$, $P_{5\text{V}} = -21.25\text{ mW}$)

Figure 2. Resistive circuit with three independent sources

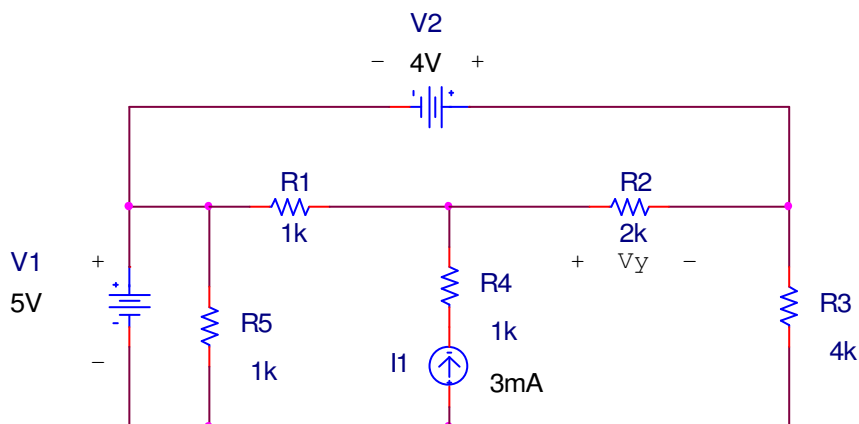


5. Referring to Fig. 3, (a) use either node or mesh method (whichever is easier) to find V_y and V_x . (b) find the power absorbed in the voltage-controlled current source.
 (Answers: $V_x = 4.364$ V, $V_y = -2.909$ V, $P_{vccs} = -34.51$ mW)

Figure 3. Resistive circuit containing a voltage-controlled current source

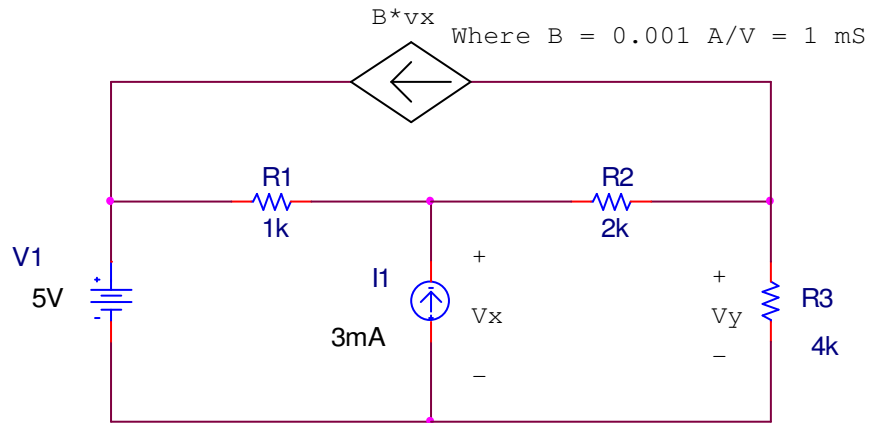

6. Referring to Fig. 3, (a) remove R_3 and, looking into the terminals where R_3 had been connected, find the Thevenin Equivalent. (b) Now connect R_3 across the terminals of this Thevenin Equivalent and find V_y . (This value of V_y must agree with the value of V_y obtained in Problem 5.) (Answers: $V_{th} = -4$ V, $R_{th} = 1.5$ k, $V_y = -2.909$ V)
7. Referring to Fig. 4, find the Thevenin Equivalent looking into terminals “a-b”. (Answers: $V_{th} = 0$ (since there are NO independent sources present), $R_{th} = 3.5$ ohms)

Figure 4. Resistive 1-port containing a current-controlled current source

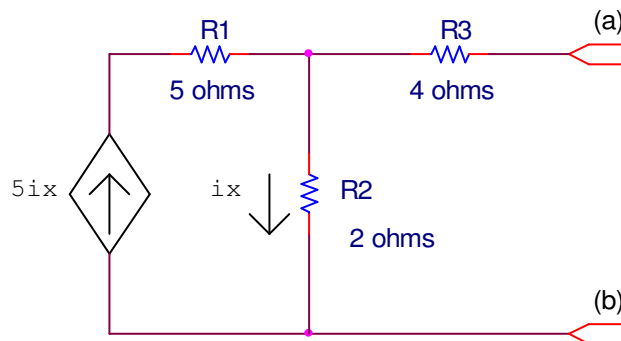

8. Referring to Fig. 5, (a) find the Thevenin Equivalent looking into terminals “a-b”. (b) find the value of load resistance R_L which, when placed across terminals “a-b”, extract maximum power from the circuit of Fig. 5. (c) What is the value of this maximum power that can be extracted? (d) What value of R_L will extract maximum current from this circuit? (e) What is this value of maximum current? (f) What value of R_L will extract maximum voltage from this circuit? (g) What is this value of maximum voltage?
 (Answers: (a) $V_{th} = 6\text{ V}$, $R_{th} = 4.4\text{ ohm}$, (b) $R_{Lmax} = 4.4\text{ ohm}$, (c) $P_{Lmax} = 2.045\text{ W}$, (d) $R_L = 0$, (e) $I_{max} = 1.363\text{ A}$, (f) $R_L = \text{infinity}$ (g) $V_{max} = 6\text{ V}$.)

Figure 5. Simple resistive 1-port circuit

