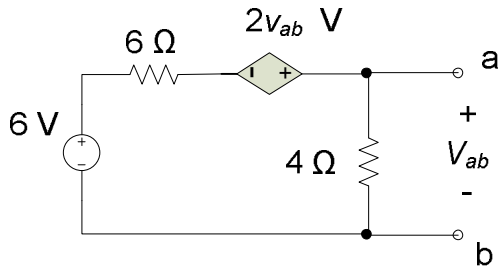


ECE203—DC Circuits


Review for Test 3

1. For the following circuit:




- Use the test source method to find R_{th} . ($12\ \Omega$)
- What is the value of a load resistor placed across terminals a-b for maximum power transfer to the load? ($12\ \Omega$)
- Compute the maximum power transferred to the load. ($3W$)

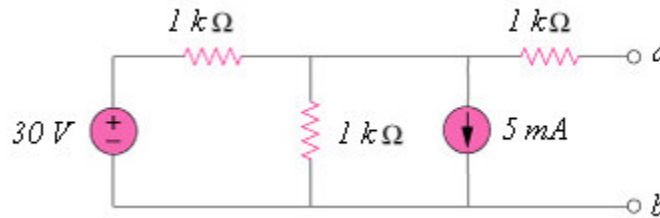2. For the following circuit, find the maximum power possible delivered to the load.




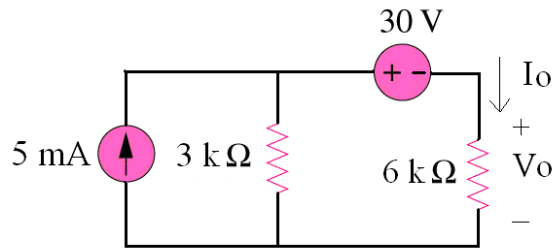3. For the following circuit use the concept of superposition,




- Calculate the voltage, V_o , due to the 5mA current source acting alone. ($10V$)
- Calculate the voltage, V_o , due to the 30V voltage source acting alone. ($-20V$)
- Using the solutions to parts a and b, calculate the total voltage, V_o . ($-10V$)

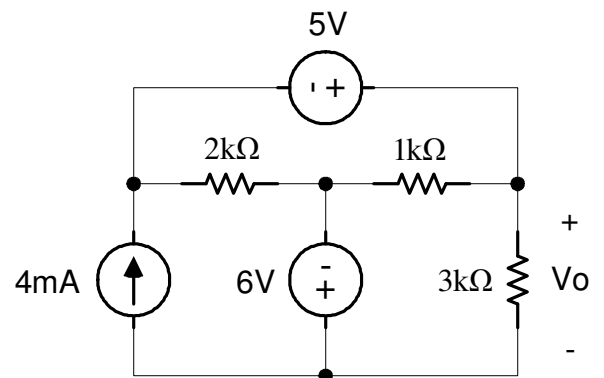
4. Using the concept of superposition to find V_o .



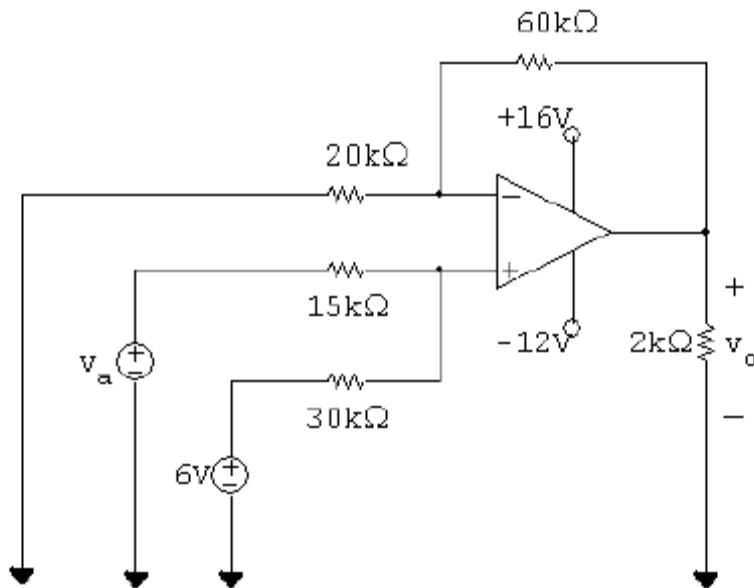5. Find the range of values for the voltage v_a such that the output voltage v_o does not saturate and the op amp remains in its linear region of operation



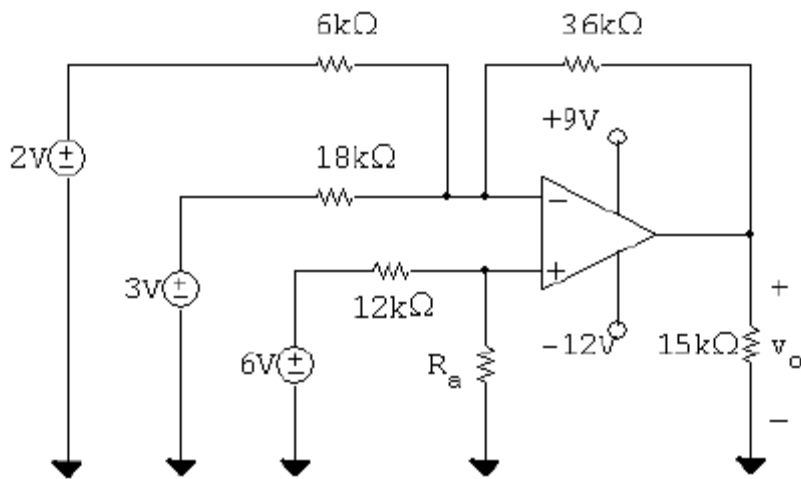6. Find the range of values for the resistor R_a such that the output voltage v_o does not saturate and the op amp remains in its linear region of operation



7. Find V_{o1} and V_{o2} .



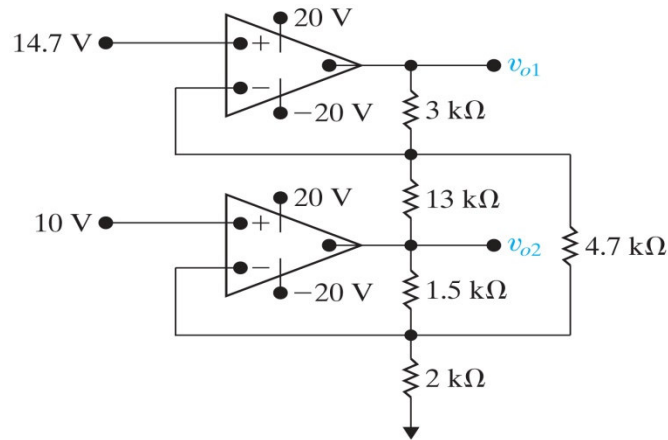


Figure: 05-18-306P5.39
Copyright © 2008 Pearson Prentice Hall, Inc.

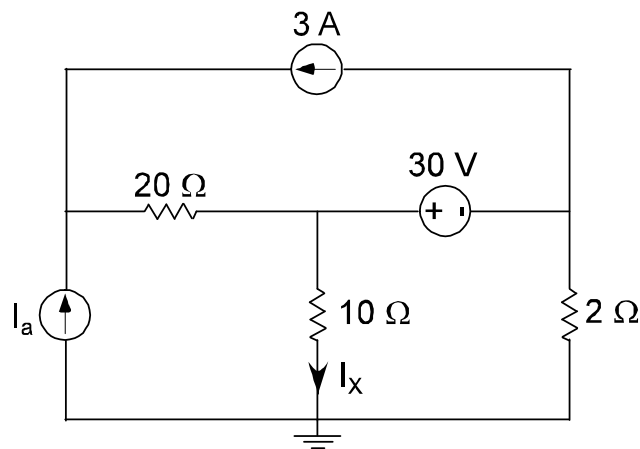
8. Use superposition to determine the value of I_a that will make $I_x = 4.5$ A. What percentage of the 3 A source flows in I_x ?



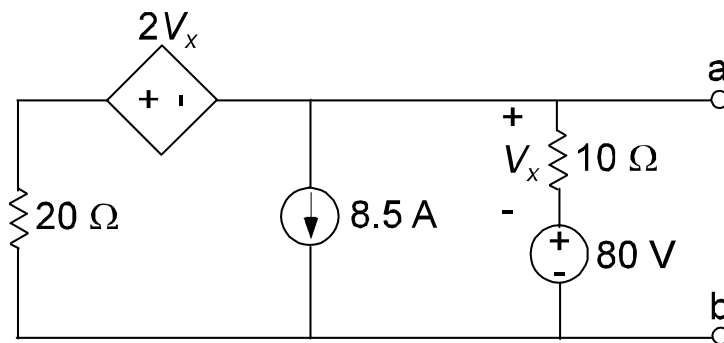9. Determine the maximum power that can be drawn out of the terminals a—b.



10. Determine V_0 and I_x .

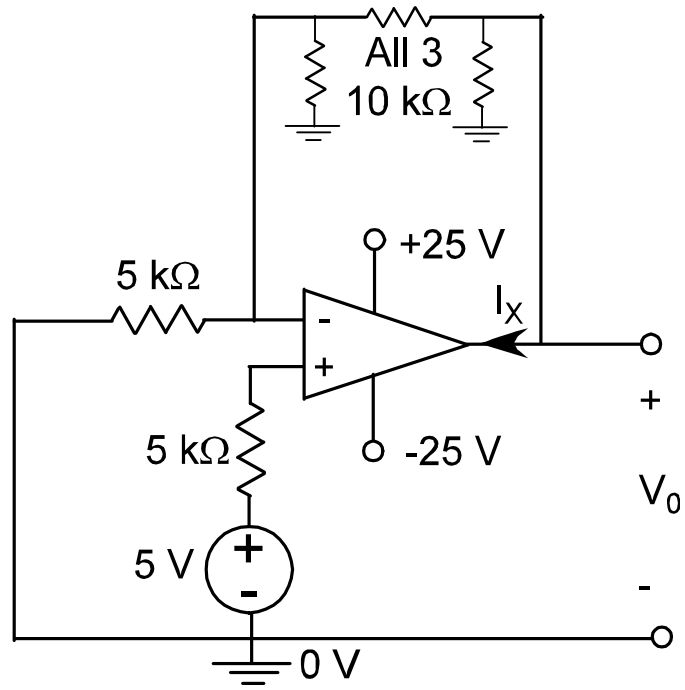

11. Ditto.

