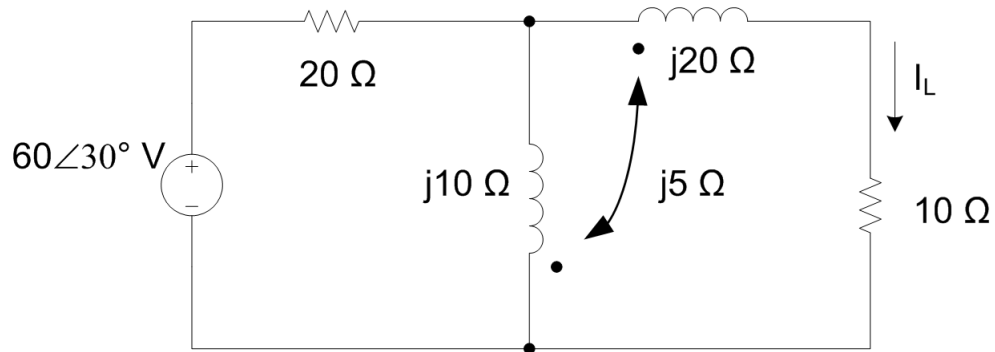


ECE204—AC Circuits


Review for Final Exam [w/ answers](#)

1. For the following circuit, find the current I_L in phasor form.




(Ans: $I_S = 2.74\angle 17.5^\circ \text{ A}$; $I_L = 1.00\angle 31.6^\circ \text{ A}$)

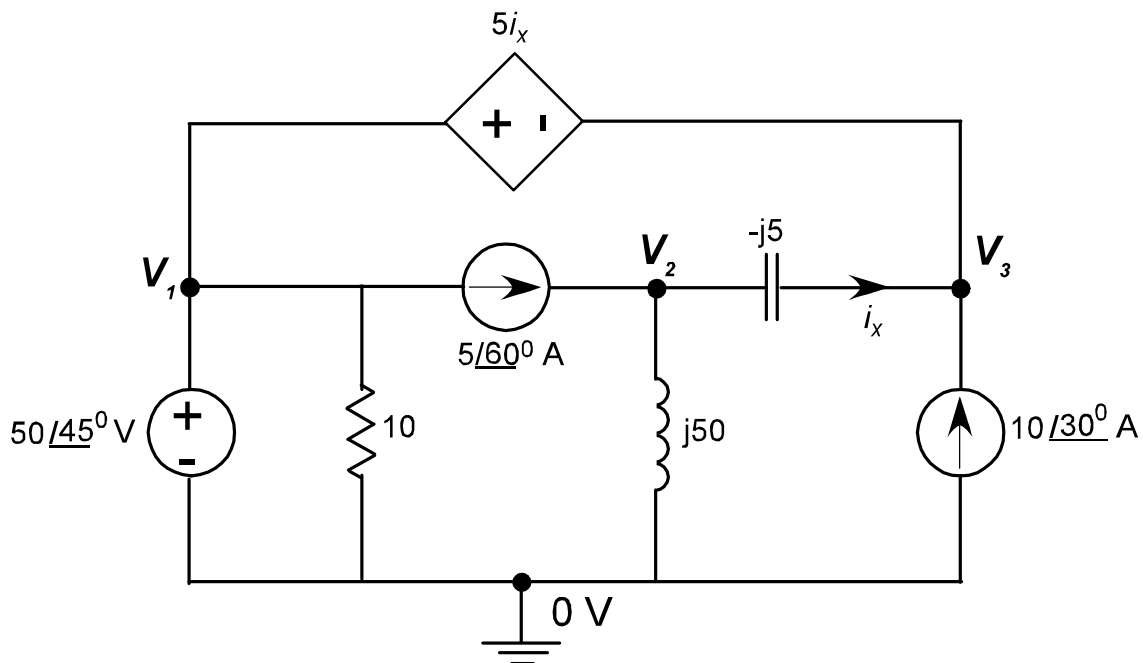2. Apply nodal analysis to the following circuit and determine the phasor voltages V_1 , V_2 and V_3 . Confirm your result using mesh analysis.




(Ans: $V_1 = 50\angle 45^\circ \text{ V}$; $V_2 = 49.17\angle -4.8^\circ \text{ V}$; $V_3 = 24.11\angle 21.4^\circ \text{ V}$; $I_x = 5.9\angle 64.1^\circ$)

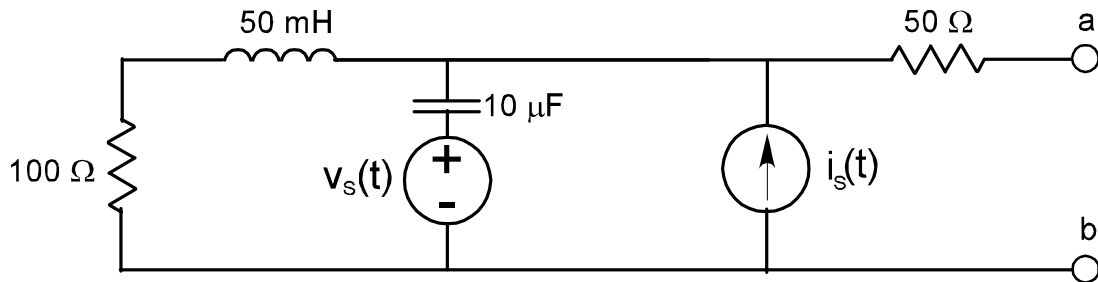3. Determine the Thevenin & Norton Equivalents at terminals a—b. Where the sources are given by:
 $v_s(t) = \sqrt{2} \times 500 \cos(2000t + 90^\circ)$ V and $i_s(t) = \sqrt{2} \times 5 \cos(2000t - 90^\circ)$ A.



(Ans: $V_{TH}=1000\angle 135^\circ$ V; $I_N=10.8\angle 175.6^\circ$ A; $Z_{TH}=70-60j\Omega$)

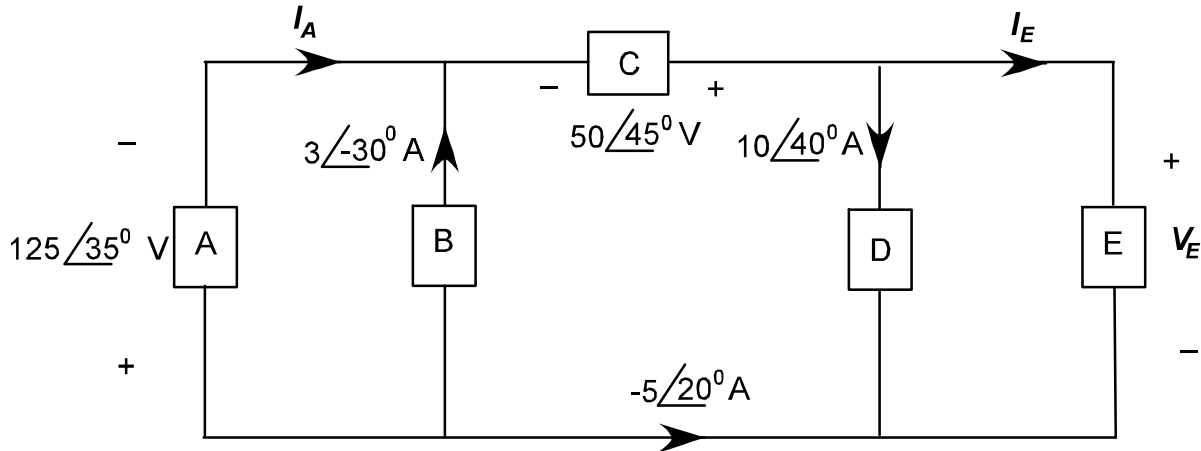
4. Determine the complex power dissipated by each element and the power factor at each element.



($S_A=479.5\angle -21.8^\circ$ VA, $S_B=375\angle 65^\circ$ VA, $S_C=250\angle -155^\circ$ VA, $S_D = 762.5\angle 168.5^\circ$ VA, $S_E= 424.8\angle -29.4^\circ$ VA, check that power balances)

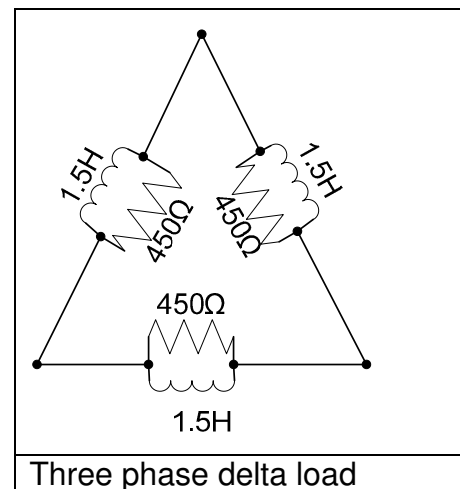5. Three loads A, B & C are supplied at 12.47 kV, 60 Hz, from an ideal three-phase source. Load A is 1.8 MVA at 0.75 lag, load B is 585 kW at 0.9 lead, and load C is three delta-connected 450 Ω/ph resistors in parallel with three 1.5 H/ph inductors. Determine:
- The complex power drawn from the source
 - The value of capacitance (μ F/ph) that has to be placed in parallel with the loads to make the overall power factor 0.925 lag.

ANS: $S_s=990.6+j577.4$ kVA/phase; $C = 8.72\mu$ F/phase



6. A three-phase load is fed from a 60 Hz supply via three parallel feeders each with impedance $0.1 + j0.25 \Omega/\text{phase}$. The load is 9 MVA, 0.864 pf **lag**. The voltage at the load is 4.16 kV. Determine:
- Magnitude of the supply voltage (V_s)
 - Percent Voltage Regulation (VR)
 - Real power drawn from the supply
 - Real power lost in the feeder
 - Efficiency of transmission

ANS: $|V_s| = 4.31\text{kV}$ (line-line); VR = 3.7%; $\eta=98\%$

7. A factory is supplied at 34.5 kV from an ideal 3ϕ , 60 Hz supply. It draws a continuous load of 30 MW with a pf of 0.6 lag. Determine:
- The capacitance ($\mu\text{F}/\text{phase}$) of a Y-connected bank that will improve the pf to 0.95 lag.
 - The capacitance ($\mu\text{F}/\text{phase}$) if a Δ -connected bank were used.
 - The annual saving in demand charge, if the monthly demand charge is \$12.00/kVA.
 - The payback time in months if capacitors cost \$90/kVAR to purchase and install and interest is ignored.

ANS: $C_Y = 67.2\mu\text{F}$; $C_\Delta = 22.4\mu\text{F}$, Savings \$2.65 Million; payback = 53 weeks

8. The following data has been acquired from a transformer rated at 15 kVA, 2300/230 V, 60 Hz.

	Voltage	Current	Power
Open-circuit test	$V_{oc} = 2300 \text{ V}$	$I_{oc} = 0.21 \text{ A}$	$P_{oc} = 50 \text{ W}$
Short-circuit test	$V_{sc} = 47 \text{ V}$	$I_{sc} = 6.0 \text{ A}$	$P_{sc} = 160 \text{ W}$

- Find the equivalent circuit impedances and draw the circuit labeling all known values
- If the transformer is supplying its rated current to a load at 230V and 0.8 pf, lagging, then determine the input voltage of the transformer, the voltage regulation, and the efficiency of the transformer.

ANS: $R_c = 106.5 \text{ k}\Omega$; $X_m = 11.01 \text{ k}\Omega$; $R = 4.45 \Omega$; $X = 6.45 \Omega$, $V_p = 2348.5 \text{ V}$; VR = 2.1 %, $\eta = 98.03\%$. (For high voltage side testing)