

**Homework Set #19****DUE Monday, April 30, 2012**1. Problem 11.10 (9.10 in abridged version) ( $V_{AN} = 262.79\angle-2.17^\circ\text{V}$ )

$$[a] \mathbf{I}_{aA} = \frac{277\angle 0^\circ}{80 + j60} = 2.77\angle -36.87^\circ \text{ A (rms)}$$

$$\mathbf{I}_{bB} = \frac{277\angle -120^\circ}{80 + j60} = 2.77\angle -156.87^\circ \text{ A (rms)}$$

$$\mathbf{I}_{cC} = \frac{277\angle 120^\circ}{80 + j60} = 2.77\angle 83.13^\circ \text{ A (rms)}$$

$$\mathbf{I}_o = \mathbf{I}_{aA} + \mathbf{I}_{bB} + \mathbf{I}_{cC} = 0$$

$$[b] \mathbf{V}_{AN} = (78 + j54)\mathbf{I}_{aA} = 262.79\angle -2.17^\circ \text{ V (rms)}$$


$$[c] \mathbf{V}_{AB} = \mathbf{V}_{AN} - \mathbf{V}_{BN}$$

$$\mathbf{V}_{BN} = (77 + j56)\mathbf{I}_{bB} = 263.73\angle -120.84^\circ \text{ V (rms)}$$


$$\mathbf{V}_{AB} = 262.79\angle -2.17^\circ - 263.73\angle -120.84^\circ = 452.89\angle 28.55^\circ \text{ V (rms)}$$

[d] Unbalanced — see conditions for a balanced circuit on p. 504 of the text!

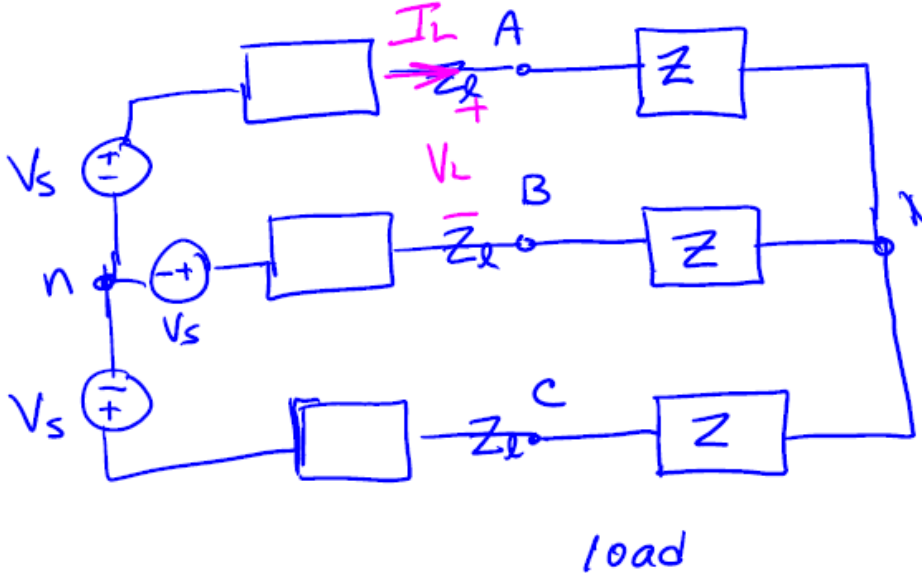2. A three-phase, 50 kVA, 600V, 60Hz generator operates at rated terminal voltage and supplies a **line current** of 48 A at a 0.8 lagging power factor to a balanced three-phase load.
- Determine the real, reactive, and apparent power taken by the load.
  - Determine the impedance ( $\Omega/\text{ph}$ ) of the load:
    - if it is wye-connected,
    - if it is delta-connected.



Generator power

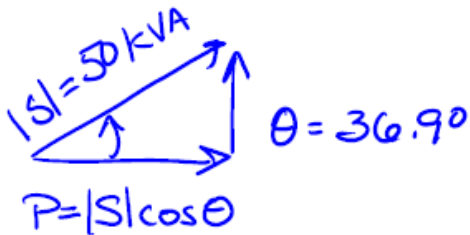

$$P = (50 \text{ k})(0.8) = 40 \text{ kW}$$

$$Q = \sqrt{50^2 - 40^2} = 30 \text{ kVAR}$$

$$|S| = 50 \text{ kVA}$$

$$Z = \frac{V_\phi}{I_\phi}$$

For wye-connection:

$$V_L = 600 \angle 0^\circ \text{ V} \Rightarrow V_{AN} = \frac{600}{\sqrt{3}} \angle 0^\circ \text{ V}$$

$$I_L = 48 \angle -36.9^\circ \text{ A} \Rightarrow I_A = 48 \angle -36.9^\circ \text{ A}$$

$$Z = \frac{V_{AN}}{I_A} = \frac{600/\sqrt{3}}{48 \angle -36.9^\circ}$$


$$Z = 7.217 \angle 36.9^\circ \Omega/\text{ph}$$

For delta-connection:  $Z_\Delta = 3 \times Z_Y$

$$Z_\Delta = 21.65 \angle 36.9^\circ \Omega/\text{ph}$$

3. Problem 11.11 (9.11 in abridged version).

Make a sketch of the a-phase:

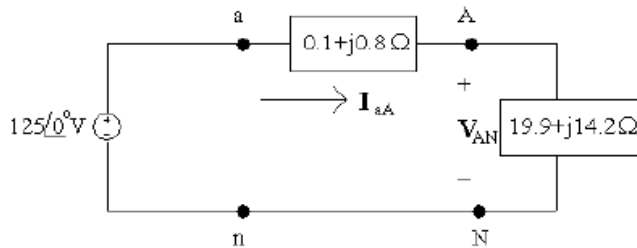

[a] Find the a-phase line current from the a-phase circuit:

$$\begin{aligned} \mathbf{I}_{aA} &= \frac{125\angle 0^\circ}{0.1 + j0.8 + 19.9 + j14.2} = \frac{125\angle 0^\circ}{20 + j15} \\ &= 4 - j3 = 5\angle -36.87^\circ \text{ A (rms)} \end{aligned}$$

Find the other line currents using the acb phase sequence:

$$\mathbf{I}_{bB} = 5\angle -36.87^\circ + 120^\circ = 5\angle 83.13^\circ \text{ A (rms)}$$

$$\mathbf{I}_{cC} = 5\angle -36.87^\circ - 120^\circ = 5\angle -156.87^\circ \text{ A (rms)}$$

[b] The phase voltage at the source is  $\mathbf{V}_{an} = 125\angle 0^\circ$  V. Use Fig. 11.9(b) to find the line voltage,  $\mathbf{V}_{ab}$ , from the phase voltage:

$$\mathbf{V}_{ab} = \mathbf{V}_{an}(\sqrt{3}\angle -30^\circ) = 216.51\angle -30^\circ \text{ V (rms)}$$

Find the other line voltages using the acb phase sequence:

$$\mathbf{V}_{bc} = 216.51\angle -30^\circ + 120^\circ = 216.51\angle 90^\circ \text{ V (rms)}$$

$$\mathbf{V}_{ca} = 216.51\angle -30^\circ - 120^\circ = 216.51\angle -150^\circ \text{ V (rms)}$$

[c] The phase voltage at the load in the a-phase is  $\mathbf{V}_{AN}$ . Calculate its value using  $\mathbf{I}_{aA}$  and the load impedance:

$$\mathbf{V}_{AN} = \mathbf{I}_{aA} Z_L = (4 - j3)(19.9 + j14.2) = 122.2 - j2.9 = 122.23\angle -1.36^\circ \text{ V (rms)}$$

Find the phase voltage at the load for the b- and c-phases using the acb sequence:

$$\mathbf{V}_{BN} = 122.23\angle -1.36^\circ + 120^\circ = 122.23\angle 118.64^\circ \text{ V (rms)}$$

$$\mathbf{V}_{CN} = 122.23\angle -1.36^\circ - 120^\circ = 122.23\angle -121.36^\circ \text{ V (rms)}$$

[d] The line voltage at the load in the a-phase is  $\mathbf{V}_{AB}$ . Find this line voltage from the phase voltage at the load in the a-phase,  $\mathbf{V}_{AN}$ , using Fig. 11.9(b):


$$\mathbf{V}_{AB} = \mathbf{V}_{AN}(\sqrt{3}\angle -30^\circ) = 211.72\angle -31.36^\circ \text{ V (rms)}$$

Find the line voltage at the load for the b- and c-phases using the acb sequence:

$$\mathbf{V}_{BC} = 211.72\angle -31.36^\circ + 120^\circ = 211.72\angle 88.64^\circ \text{ V (rms)}$$

$$\mathbf{V}_{CA} = 211.72\angle -31.36^\circ - 120^\circ = 211.72\angle -151.36^\circ \text{ V (rms)}$$

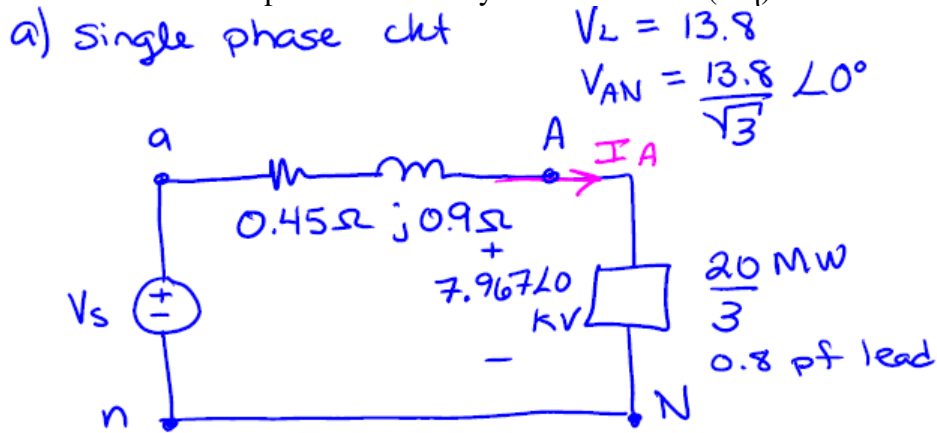4. A 3 $\phi$  load, supplied with 13.8kV at the load end, absorbs 20MW at 0.8 pf leading. The feeder impedance is  $0.45 + j0.9 \Omega/\phi$  (Ohms per phase).
- Draw the single-phase equivalent circuit.
  - Find the line current.
  - What is the percent voltage regulation (%VR)?
  - Is the value obtained in part (c) usually acceptable for general industrial power systems?
  - What is the percent efficiency of transmission (% $\eta$ )?



b)  $S = VI^*$     $P = VI \cos \theta$

$$I = \frac{P}{V \cos \theta} = \frac{P}{V \text{ pf}} = \frac{20 (10^6)}{(0.8)(7.967 \angle 10^\circ)(10^3)}$$

$$I = 1046 \angle 36.9^\circ \text{ A}$$

c)  $V_s = I(0.45 + j0.9) + 7.967 \angle 10^\circ$

$$V_s = 7848 \angle 7.6^\circ \text{ V}$$

$$VR = \frac{V_s - V_{\text{Load}}}{V_{\text{Load}}} = \frac{7848 - 7967}{7967}$$

$$VR = -1.5\%$$

acceptable if magnitude of VR < 5%  
 neg VR if pf is leading

$$e) S_s = V_s I^*$$

$$S_s = 8.21 \angle 29.3^\circ = 7.159 - j4.015 \text{ MVA/ph}$$

$$P_s = 7.159 \text{ MW/ph}$$

$$P_{\text{Load}} = 6.667 \text{ MW/ph}$$

$$\eta = \frac{6.667}{7.159} \times 100\%$$

$$\eta = 93.12\%$$