

**Homework Set #1****Textbook:** Chapter 6.1-6.2**Coverage:** Capacitance and self inductance**DUE Thursday, March 8, 2012**

For problems 3 and 4, you must do the calculus by hand, but you can use a calculator for the arithmetic.

1. Problem 6.1 on page 204 (*answers in back of book*)

$$0 \leq t \leq 2 \text{ s} :$$

$$i_L = \frac{10^3}{2.5} \int_0^t 3 \times 10^{-3} e^{-4x} dx + 1 = 1.2 \frac{e^{-4x}}{-4} \Big|_0^t + 1$$


$$= -0.3e^{-4t} + 1.3 \text{ A}, \quad 0 \leq t \leq 2 \text{ s}$$

$$i_L(2) = -0.3e^{-8} + 1.3 = 1.3 \text{ A}$$

$$t \geq 2 \text{ s} :$$

$$i_L = \frac{10^3}{2.5} \int_2^t -3 \times 10^{-3} e^{-4(x-2)} dx + 1.3 = -1.2 \frac{e^{-4(x-2)}}{-4} \Big|_2^t + 1.3$$
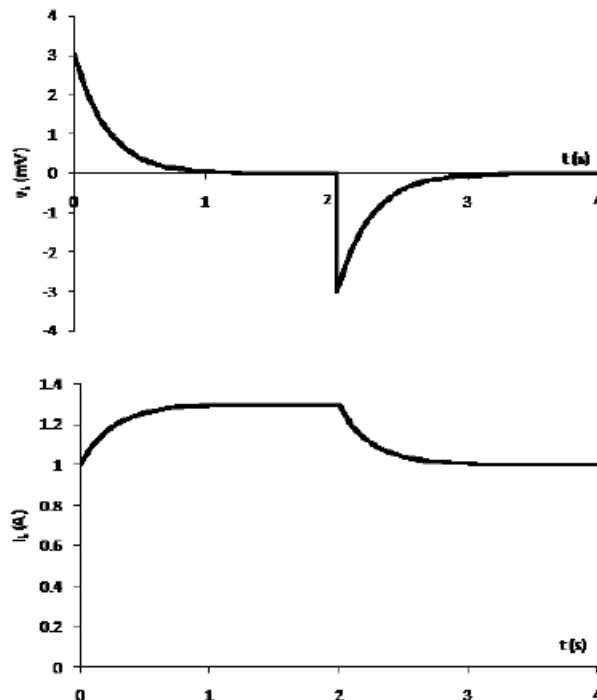
$$= 0.3e^{-4(t-2)} + 1 \text{ A}, \quad t \geq 2 \text{ s}$$




2. Problem 6.17 on page 206 (*answers in back of book*)



$$i_C = C(dv/dt)$$

$$0 < t < 0.5 : \quad i_C = 20 \times 10^{-6}(60)t = 1.2t \text{ mA}$$
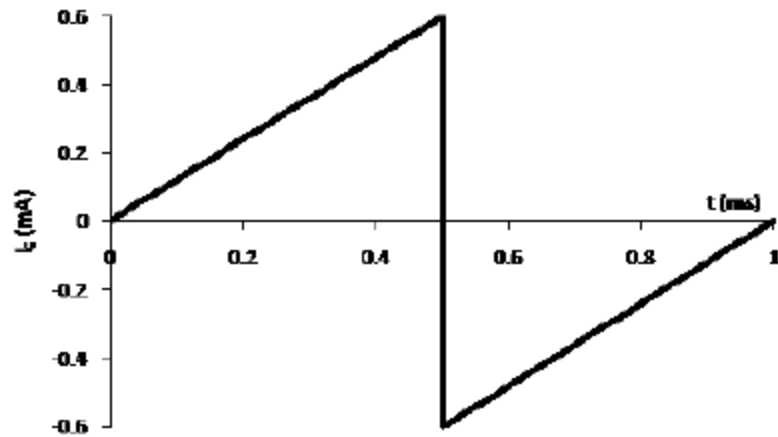
$$0.5 < t < 1 : \quad i_C = 20 \times 10^{-6}(60)(t - 1) = 1.2(t - 1) \text{ mA}$$



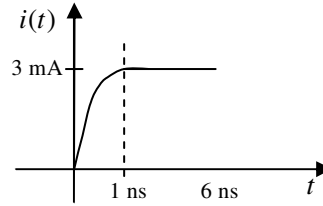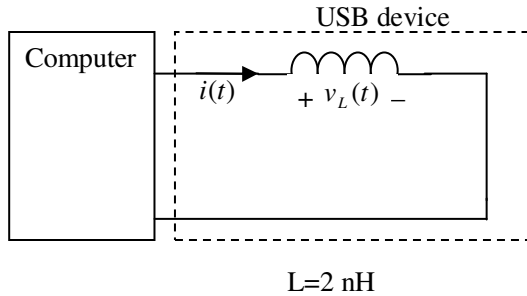3. A computer communicates over wires (such as a USB cable) by sending very short pulses. The device at the far end of the cable (such as a memory stick) senses the pulses with electronics which have inductance and capacitance. They can be modeled with the appropriate valued device as shown below.



$$i(t) = \begin{cases} 0 & t \leq 0 \text{ ns} \\ 3(1 - e^{-4 \times 10^9 t}) \text{ mA} & 0 \text{ ns} \leq t < 1 \text{ ns} \\ 3 \text{ mA} & 1 \text{ ns} \leq t < 6 \text{ ns} \end{cases}$$

- (a) Find the voltage  $v_L(t)$  for  $0 \text{ ns} < t \leq 1 \text{ ns}$  and plot your results.  
 (b) Find the power absorbed by the inductor at  $t = 0.5 \text{ ns}$ .  
 (c) Find the energy stored in the inductor at  $t = 0.5 \text{ ns}$ .

Solution:

For an inductor labeled with passive sign convention,  
 $v = L \frac{di}{dt}$ . Since we know  $i(t)$ , we just need to take a derivative.

$$v_L(t) = (2 \times 10^{-9}) \frac{d}{dt} \left[ \underset{\substack{\uparrow \\ \text{work in Amps}}}{0.003} (1 - e^{-4E+9t}) \right]$$

$$\text{we need } \frac{d}{dt} \left[ \underset{\substack{\downarrow \\ \text{deriv. of const} \\ = 0}}{0.003} - \underset{\substack{\downarrow \\ \frac{d}{dt} e^u = e^u \frac{du}{dt}}}{0.003 e^{-4E+9t}} \right]$$

$$\text{here, } \frac{du}{dt} \text{ is } -4E+9$$

So the result is

$$-0.003 e^{-4E+9t} \left( \underset{\substack{\uparrow \\ e^u}}{e^u} \right) \left( \underset{\substack{\downarrow \\ \frac{du}{dt}}}{-4E+9} \right)$$

$$\text{So, } \frac{d}{dt} \left[ 0.003 - 0.003 e^{-4E+9t} \right]$$

$$= (-0.003)(-4E+9) e^{-4E+9t} = (+12E6) e^{-4E+9t}$$


and

$$v_L(t) = (2E-9)(12E+6) e^{-4E+9t} \text{ V}$$

$$v_L(t) = (0.024) e^{-4E+9t} \text{ V} \quad 0 < t < 1\text{ns}$$

Since an exponential starts at 0 with a value of 1 and decays to zero in about 4 time constants,

the plot should be

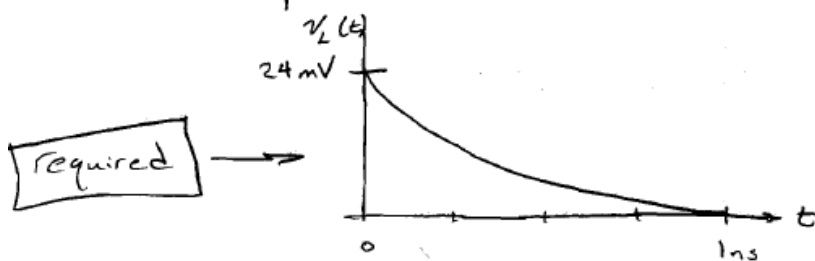

$$\left( e^{-t/\tau} \text{ where } \tau \text{ is the time constant gives } \tau = \frac{1}{4E+9} = \frac{1}{4} \text{ ns} \right)$$

b)  $p(t) = v(t) i(t)$  (+ is absorbed for passive labeling)

$$v(0.5\text{ns}) = 0.024 \left( e^{-4E+9(0.5E-9)} \right)$$

$$= 0.024 e^{-2} = 0.003248 \text{ V} = 3.248 \text{ mV}$$

$$i(t) = 0.003 \left( 1 - e^{-4E+9(0.5E-9)} \right)$$

$$= 0.003 \left( 1 - e^{-2} \right) = 0.003 (0.8647)$$


$$= 0.002594 \text{ A} = 2.594 \text{ mA}$$

$$p(0.5\text{ns}) = 8.425 \mu\text{W}$$

c)  $W = \frac{1}{2} L i^2 = \frac{1}{2} (2E-9) (2.594E-3)^2$


$$W = 6.729E-15 \text{ J} \quad \text{femtoJoules!}$$

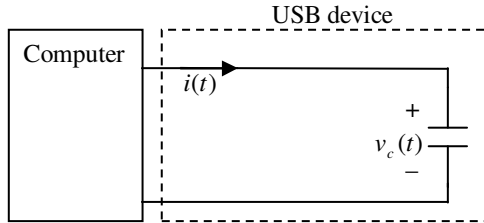4. A computer communicates over wires (such as a USB cable) by sending very short pulses. The device at the far end of the cable (such as a memory stick) senses the pulses with electronics which have inductance and capacitance. They can be modeled with the appropriate valued device as shown below.



$$C = 5 \text{ pF}$$

$$v_c(0) = 0 \text{ V}$$

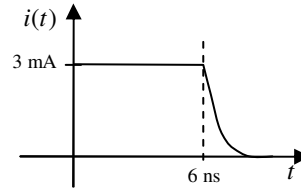

$$i(t) = \begin{cases} 3 \text{ mA} & 0 \text{ ns} \leq t < 6 \text{ ns} \\ 3e^{-4 \times 10^9(t - 6 \times 10^{-9})} \text{ mA} & 6 \text{ ns} \leq t < 7 \text{ ns} \\ 0 \text{ mA} & t \geq 7 \text{ ns} \end{cases}$$

- (a) Find the voltage  $v_c(t)$  for  $0 \text{ ns} < t < 7 \text{ ns}$  and plot your results.  
 (b) Find the power absorbed by the capacitor at  $t = 6.5 \text{ ns}$ .  
 (c) Find the energy stored in the capacitor at  $t = 2 \text{ ns}$ .

Solution:  $v_c(t) = \frac{1}{C} \int_0^t i(\tau) d\tau + v_c(0)$

for  $0 \leq t < 6 \text{ ns}$ ,  $i(t) = 3 \text{ mA}$ , so

$$\int_0^t (3 \times 10^{-3}) d\tau = (3 \times 10^{-3})t$$

$$\text{and } v_c(t) = \frac{1}{5 \times 10^{-12}} (3 \times 10^{-3})t + 0 \text{ V}$$

$$v_c(t) = 600 \times 10^6 t \text{ V}$$

$$\text{at } t = 6 \text{ ns}, v_c(t) = 600 \times 10^6 (6 \times 10^{-9}) = 3.6 \text{ V}$$

$$\text{from } 6 \text{ ns} \leq t < 7 \text{ ns}, i(t) = 3 e^{-4 \times 10^9(t - 6 \times 10^{-9})} \text{ V} \quad \checkmark$$

$$v_c(t) = \frac{1}{C} \int_{6 \text{ ns}}^t i(\tau) d\tau + v_c(6 \text{ ns})$$

here  $\int e^u du = e^u$  we need  $du = -4 \times 10^9$

$$\text{so } \int \frac{(3 \times 10^{-3}) e^{-4 \times 10^9(t - 6 \times 10^{-9})}}{(-4 \times 10^9)} (-4 \times 10^9) dt$$

$$= -750 \times 10^{-15} e^{-4 \times 10^9(t - 6 \times 10^{-9})} du$$


$$\text{So, } v_c(t) = \frac{1}{5E-12} \left( (-750E-15) e^{-4E9(t-6E-9)} - [(-750E-15) e^{-4E9(6E-9-6E-9)}] \right) + v_c(6\text{ns})$$

$$v_c(t) = \frac{1}{5E-12} \left( 750E-15 (1 - e^{-4E9(t-6E-9)}) \right) + 3.6 \text{ V}$$

$$v_c(t) = 0.15 (1 - e^{-4E9(t-6E-9)}) + 3.6 \text{ V}$$

for  $6\text{ns} \leq t < 7\text{ns}$

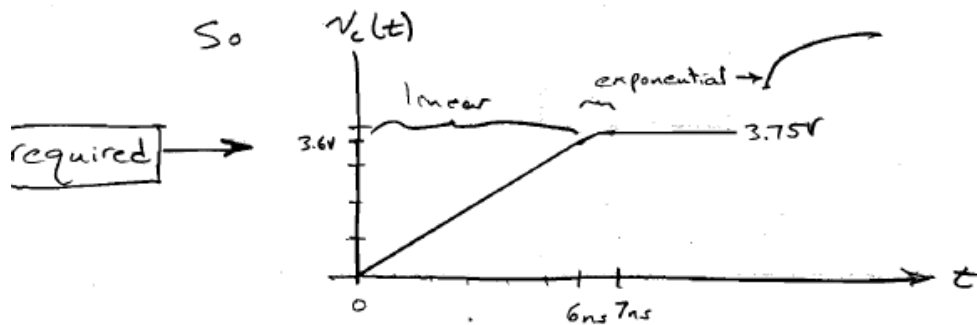So, the voltage increase linearly from 0 to 6ns, and then increases with an exponential decay from 6ns to 7ns. Again, the time constant is  $\tau$  ns.



b) the power absorbed by the capacitor at  $t_1 = 6.5\text{ns}$  is given by  $p_{\text{abs}}(t_1) = v(t_1) i(t_1)$ .

$$v(t_1) = 0.15 (1 - e^{-4E9(0.5E-9)}) + 3.6 \text{ V} = 3.723 \text{ V}$$

$$i(t_1) = (3E-3) (e^{-4E9(0.5E-9)}) = 406 \mu\text{A}$$

$$p(t_1) = 1.514 \text{ mW}$$

$$\text{c) } W = \frac{1}{2} C v^2 = \frac{1}{2} (5E-12) (600E6 (2E-9))^2$$

$$= 3.6E-12 = \boxed{3.6 \text{ pJ}}$$