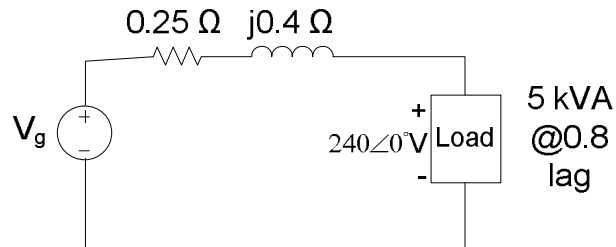


**Homework Set #26****DUE Thursday, May 17, 2012**

1. Assume that power is transmitted to a load at 240V without using a transformer as shown in the circuit below. Find the real power lost in the feeder and the efficiency of the system.




$$|I| = \frac{S}{V} = \frac{5 \times 10^3}{240} = 20.83 \text{ A}$$

The power lost in the feeder is:  $P_L = I^2 R = 20.83^2 \times 0.25 = 108.5 \text{ W}$

The efficiency is:  $\eta = \frac{5 \times 10^3 \times 0.8}{5 \times 10^3 \times 0.8 + 108.5} = 97.4 \%$

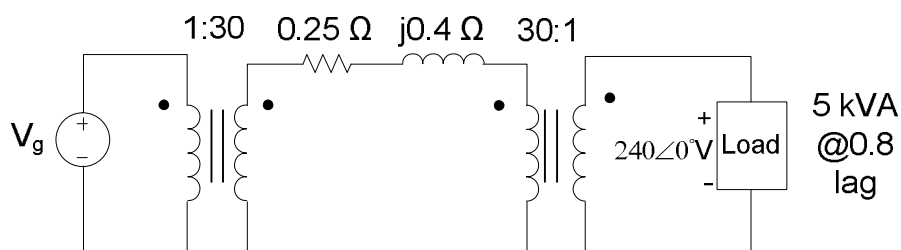2. Suppose that the power was delivered to the load but a step-up and step-down transformer was used to reduce the current in the line. Find the real power lost in the feeder and the efficiency when a 30:1 transformer is used as shown in the circuit below. If power costs 6cents/kW how much money can you save in one year?



Because the load power and load voltage are unchanged the load current  $I$  is unchanged and remains at 20.83 A, but the feeder current  $I_F$  is reduced because it is in the high voltage part of the circuit.

$$I_F = 0.0333 \times I = 0.694 \text{ A}$$

The power lost in the feeder is:  $P_L = I_F^2 R = 0.694^2 \times 0.25 = 0.12 \text{ W}$

The efficiency is:  $\eta = \frac{5 \times 10^3 \times 0.8}{5 \times 10^3 \times 0.8 + 0.12} = 100 \%$

The cost of the losses is:  $\$L = 0.108 \times 8760 \times 0.06 = \$57/\text{yr}$

3. Now consider the effect of a non-ideal transformer used in both the step-up and step-down transformers. Assume the transformers used have the following equivalent circuit parameters, referred to the high voltage side:  $R = 15 \Omega$ ,  $X = 50 \Omega$ ,  $R_c = 150 \text{ k}\Omega$ ,  $X_m = 100 \text{ k}\Omega$ . Compute the real power lost in the system (include both coil loss and core loss along with the loss in the line) and the overall efficiency of the system.