

Homework Set #1



Textbook: Chapter 6.1-2

Coverage: Capacitance and Self Inductance

DUE Tuesday September 5, 2017 – Start of Class

You must do the calculus and sketching by hand, but you can use a calculator/Maple to check.

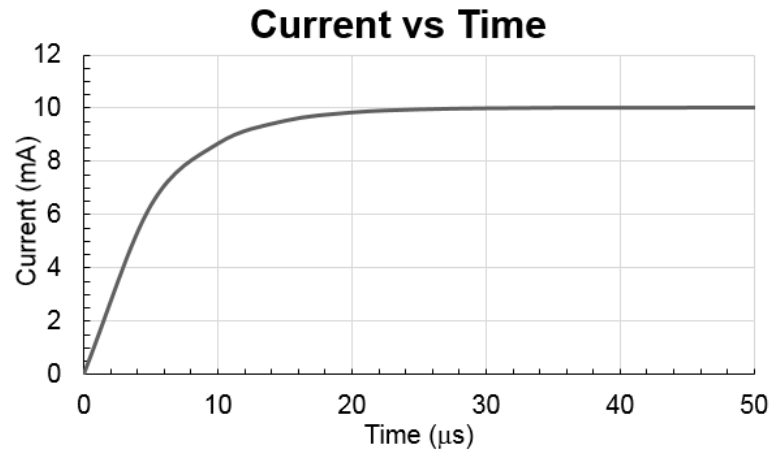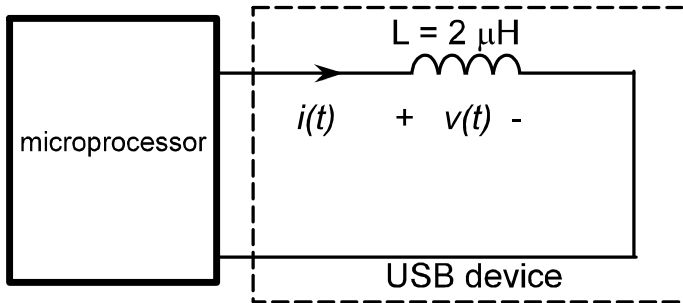1. A microprocessor communicates over wires (such as a USB cable) by sending very short pulses. The device at the far end of the cable (such as a memory stick) senses the pulses with electronics that has inductance and negligible capacitance. The appropriate model is shown below.



$$i(t) = \begin{cases} 0 & t < 0 \mu\text{s} \\ 10(1 - e^{-20000t}) \text{ mA} & 0 < t < 40 \mu\text{s} \\ 10 \text{ mA} & t > 40 \mu\text{s} \end{cases}$$

- a) Find the voltage $v_L(t)$ for $0 \mu\text{s} < t \leq 40 \mu\text{s}$ and sketch your results.
- b) Find the power absorbed by the inductor at $t = 10 \mu\text{s}$. (*slightly over $4.5 \mu\text{W}$*)
- c) Find the energy stored in the inductor at $t = 10 \mu\text{s}$. (*slightly under 75 pJ*)

2. Problem 6.2 *Answers in back of book*
3. Problem 6.16 *sketch in back of book*
4. Problem 6.21 *Answers in back of book*