

ECE204 AC Circuits


Midterm Exam 2 10/19/2010

NAME: _____ KEY _____

- **NO PARTIAL CREDIT WILL BE GIVEN** without a full explanation of the procedure followed to arrive at your solution. Put a box around your solution. **DON'T FORGET UNITS AND CONDITIONS ON VALIDITY.**
- One 8 ½ x11 inch formula sheets (both sides) may be used. Laptops may not be used. Cellphones must be turned-off.
- Time allowed : 50 min.
- You may use both sides of the paper for your answer. Please use the back of the previous page.
- Present all *phasor* quantities in *polar* form with the angle in degrees and state magnitudes to 3 significant figures.


Question #	Possible Points	Awarded Points
1	25	
2	25	
3	25	
4	25	
Total	100	

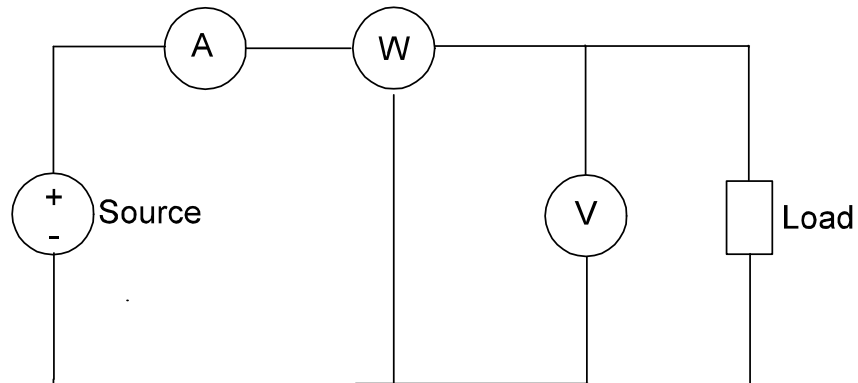1. In the circuit shown below the voltmeter reads 300 V, the ammeter reads 25 A, and the wattmeter reads 6 kW. The load is a resistor and capacitor in **parallel**. Determine:
- Real Power
 - Apparent Power
 - Reactive Power
 - Power Factor
 - Load Components (R & C) if the frequency is 1 kHz




6 kW 7.5 kVA -4.5kVAR 0.8 lead

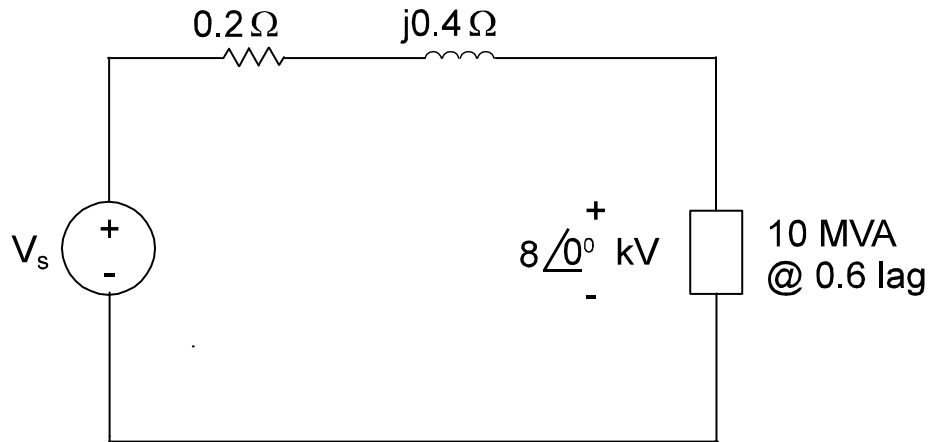2. The following figure shows a distribution feeder whose impedance is $0.2 + j0.4 \Omega$ that supplies a load of 10 MVA, 0.6 lagging pf, at 8 kV. Determine:
- Magnitude of the supply voltage (V_s)
 - Percent Voltage Regulation (VR)
 - Real power lost in the feeder



8.551 kV . 6.88% . 312.5 kW .

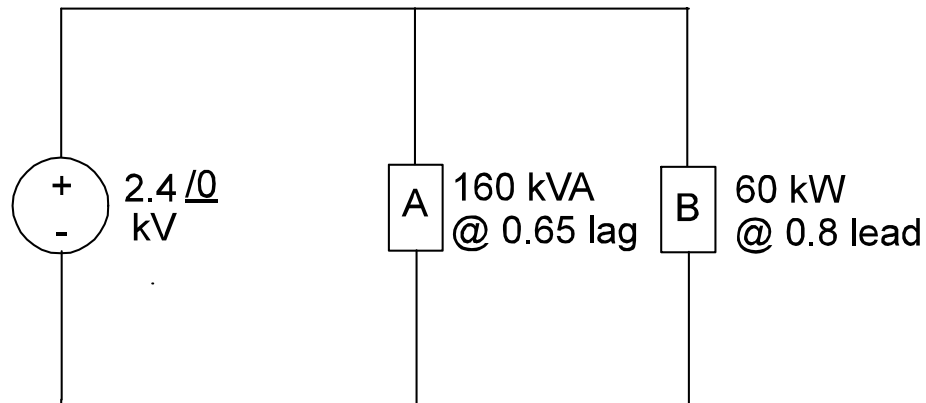3. Two loads A & B are supplied at 2.4 kV, 60 Hz, from an ideal source, as shown below. Load A is 160 kVA at 0.65 lag, and load B is 60 kW at 0.8 lead. Determine:
- The complex power drawn from the source
 - The additional reactive power needed to make the overall pf 0.95 lag
 - The value of capacitive reactance that will produce the reactive power in part (b)
 - The value of capacitance (μF) that has to be placed in parallel with the load to achieve the results of (b) and (c)



$$181 \angle 25^\circ \text{ kVA} \quad 22.69 \text{ kVAR} \quad 253.9 \Omega \quad C = \frac{1}{377 \times 253.9} = 10.45 \mu\text{F}$$

4. A 12.8 kV three-phase supply feeds a balanced delta-connected load consisting of $Z = 46\angle 30^\circ \Omega/\text{ph}$. Determine:
- the line and phase voltages and currents, and
 - the real, reactive and apparent power supplied to the loads
 - the power factor of the load.

$$\mathbf{V}_{ab} = 12.8\angle 0^\circ \quad \mathbf{V}_{bc} = 12.8\angle 240^\circ \quad \mathbf{V}_{ca} = 12.8\angle 120^\circ$$

$$\mathbf{I}_{ab} = 278.3\angle -30^\circ \text{ A}, \quad \mathbf{I}_{bc} = 278.3\angle 210^\circ \text{ A}, \quad \mathbf{I}_{ca} = 278.3\angle 90^\circ \text{ A}.$$

$$\mathbf{I}_a = \mathbf{I}_a = 482\angle -60^\circ \text{ A}, \quad \mathbf{I}_b = 482\angle 180^\circ \text{ A}, \quad \mathbf{I}_c = 482\angle 60^\circ \text{ A}.$$

9.254 MW 5.343 MVAR 10.69 MVA 0.866 lag .