
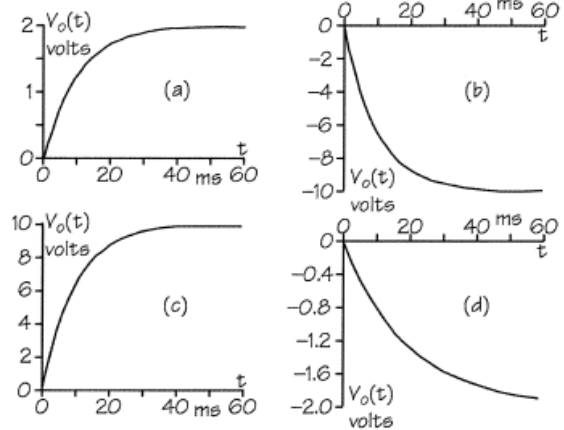


# ECE207 ELEMENTS OF ELECTRICAL ENGINEERING


## Homework Set 8 – Solutions

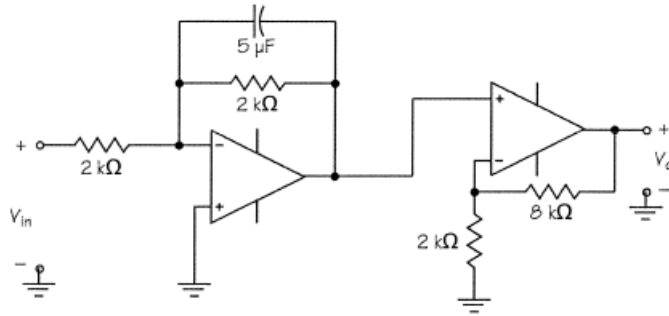8-1 Which of the four responses shown best approximates the output voltage  $V_o(t)$  for  $0 < t < 60$  ms when  $V_{in}$  is a step with an amplitude of 2 volts. Fully justify your answer.



The op-amp on the left is a LPF with a dc gain of unity (inverted). The op-amp on the right is a non-inverting amplifier with a gain of 5. Therefore, the steady-state output will be 10 V and will be inverted, so (b) is the response.

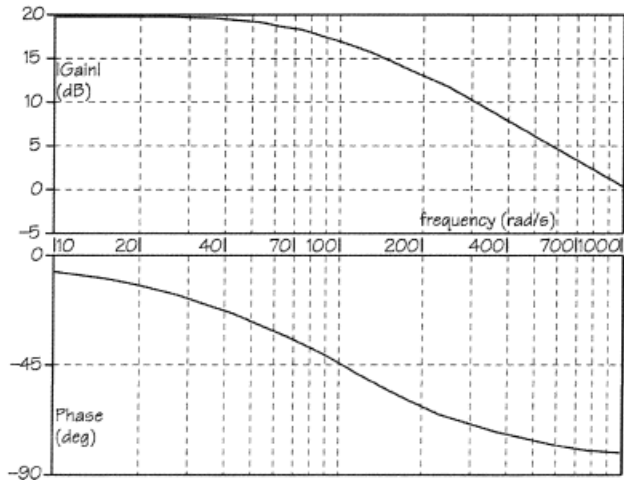8-2 The frequency response of a system is shown below. Which of the time functions shown is the best fit for the system's unit step response? Fully justify your answer.



- a)  $10(1 - e^{-100t})$
- b)  $1 - e^{-100t}$
- c)  $20(1 - e^{-100t})$
- d)  $20e^{-100t}$
- e) none of the above.

The system is 1<sup>st</sup> order because it has a slope of -20 dB/dec. The 3 dB point occurs at 100 rad/s and the LF gain is 20 dB or  $|H_{dc}| = 10$ . This means the transfer function is:

$$H(s) = \frac{10}{1 + 0.01s}, \text{ which gives } \tau = 0.01.$$


This gives a unit step response of:  $10(1 - e^{-100t})$ , which is item (a).

8-3 Data taken for a certain circuit are shown at the bottom of the page as a Bode plot of the magnitude and phase of the voltage transfer function  $H(s) = V_o(s) / V_i(s)$ .

a) If the input to this circuit is  $v_i(t) = 6.0 \cos(20,000t + 50^\circ)$  V, find the output  $v_o(t)$  in the sinusoidal steady state.

b) If the observed output voltage  $v_o(t)$  has an RMS value of 100 mV at a frequency of 60 Hz, what is the RMS value of the input voltage? [Clue: Note Hz!] [Clue<sup>2</sup>: 225 mV.]

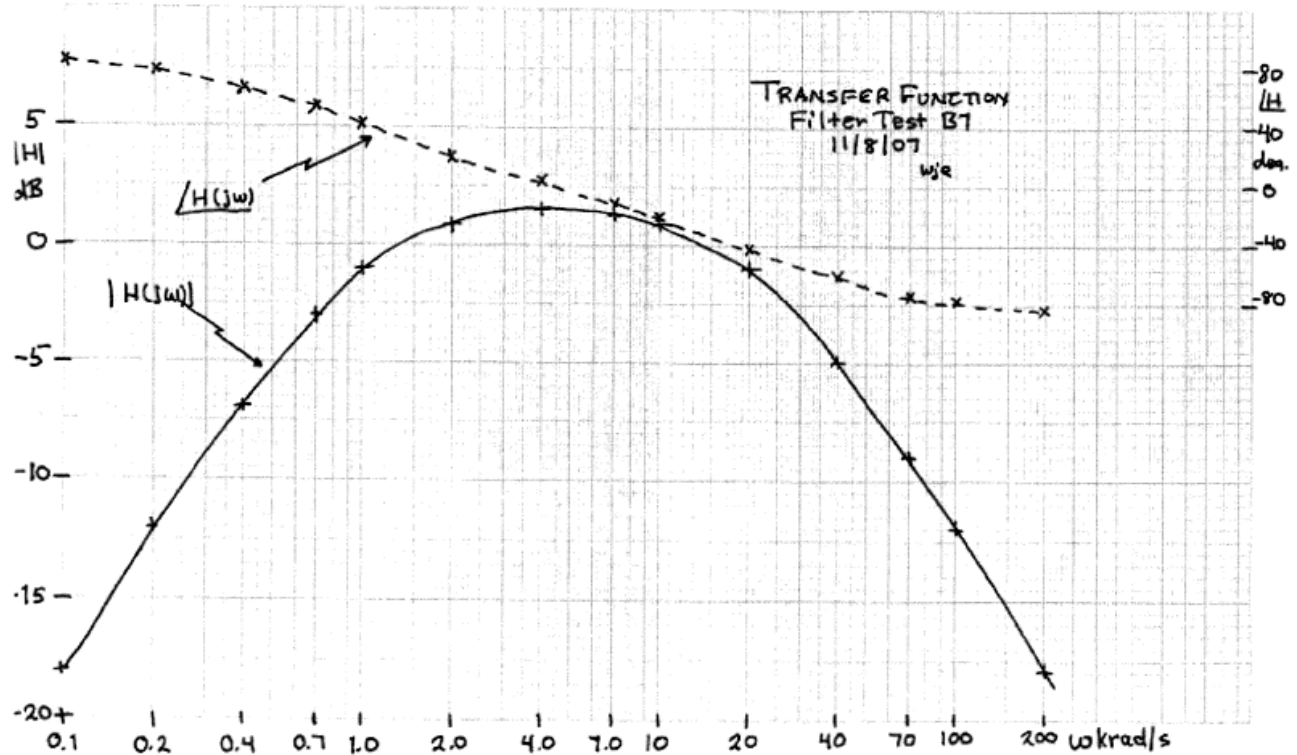c) Determine the transfer function  $H(s)$  represented by this Bode plot. Present your result for  $H(s)$  in the standard form where each term of the denominator is in the form  $(s/a + 1)$ .



a)

The gain at 20 krad/s is -1 dB or  $|H(20k)| = 10^{-1/20} = 0.8913$ , with a phase shift of  $-40^\circ$ .

$$V_i = 6/50 \text{ and } H(20k) = 0.8913/-40 \text{ so } V_o = 6 \times 0.8913/50 - 40 = 5.348/10$$

$$\boxed{V_o(t) = 5.38 \cos(20000t + 10^\circ)}$$

b) The gain at 377 rad/s is -7.0 dB or  $|H(377)| = 10^{-7.0/20} = 0.4467$

$$|V_i| = \frac{100}{0.4467} = \boxed{224 \text{ mV}}$$

c) The LF slope of +20 dB/dec means we have an "s" in the numerator. The two break points are both poles, so the form of  $H(s)$  is:

$$H(s) = \frac{K_b s}{(1 + s/p_1)(1 + s/p_2)}$$

Where  $p_1 = 10^3$  rad/s,  $p_2 = 20 \times 10^3$  rad/s and  $K_b$  is the gain at  $\omega = 1$  rad/s.

Since the gain at  $\omega = 100$  rad/s is -17.5 dB and the slope is 20 dB/dec,  $|H(1)| = -57.5$  dB and  $K_b = 10^{-57.5/20} = 1.334 \times 10^{-3}$ , which leads to:

$$H(s) = \frac{1.334 \times 10^{-3} s}{(1 + 10^{-3} s)(1 + 50 \times 10^{-6} s)}$$