
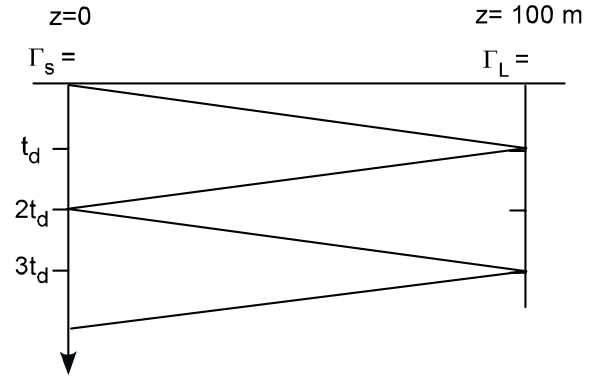


1. Given the system shown below,

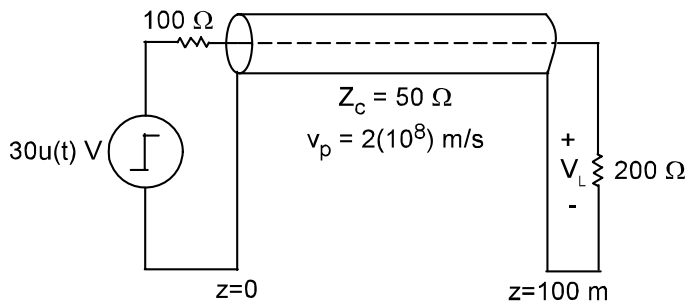

- i) Complete and label the bounce diagram through $3t_d$. (9 pts)


- ii) Determine $V_L(50 \text{ m}, 1 \mu\text{s})$ (4 pts)

- iii) Determine V_L in steady-state. (4 pts)

- iv) During the transient, will the voltage, V_L , overshoot its steady-state value? *Why or why not?* (4 pts)

- v) Show how to modify the system, with one resistor, that will cause the transient solution to end in exactly $2t_d$. *In the diagram above, place the resistance and show its value.*
 With this resistance in place, what would be the steady-state load voltage? (4 pts)

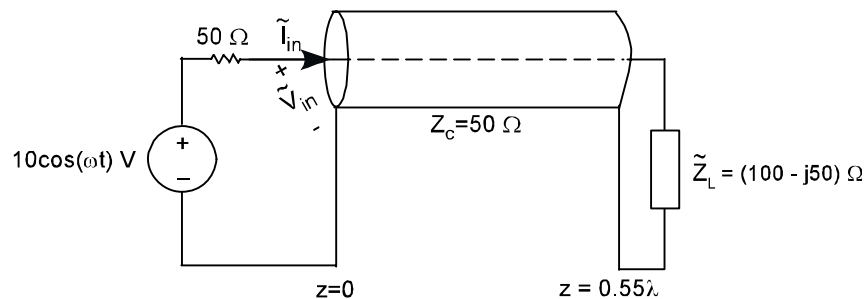3. The system shown below involves a lossless transmission line.



- i) Determine the impedance, \tilde{Z}_{in} , and the reflection coefficient, $\tilde{\Gamma}_{in}$, at the input of the transmission line. (10 pts)

- ii) Find the phasor voltage, \tilde{V}_{in} , and the phasor current, \tilde{I}_{in} , at the input of the transmission line. (8 pts.)

- iii) What is the average power input to the transmission line? (5 pts)

- iv) What is the average power absorbed by the load? (2 pts)

4. Mark **each** True/False as either **T** or **F**. (2½ pts each)

___ The input impedance for very long lossy transmission lines (“long” implying that $2\alpha d$ grows large) will be approximately Z_c no matter what load impedance is connected to the line.

___ Given that $Z_c = 100 \Omega$ and $\epsilon = 100 \text{ pF/m}$, it can be shown that $v_p = 10^8 \text{ m/s}$.

9 pts.

a)

b)

c)

d

Z_c

load

d

Z_c

load

d

Z_c

load

Hints: For the **loads** in a), b), and c), possibilities are R , parallel RC , or series RL .


You should be able to determine the resistance of all resistances.

___ Consider two lossy lines of lengths, $d_1 = \lambda$ and $d_2 = 10\lambda$. Both lines have $Z_c = 50\Omega$ and have identical \mathcal{L} , \mathcal{C} , \mathcal{R} , and \mathcal{G} . Each line is terminated with $R_L = 100\Omega$. At the input, the reflection coefficient for the shorter line will be smaller in magnitude than that of the longer line.


Why or why not? _____

___ A 1.75λ long lossless transmission line is short-circuited at the load end. For this transmission line, the input impedance and the VSWR are both infinite.

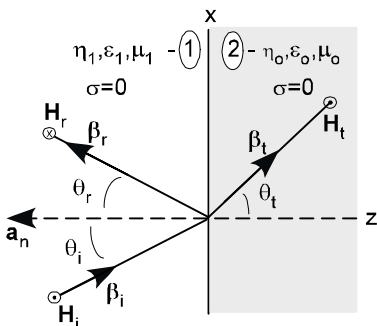___ $\tilde{H}_i = 10e^{-j\beta z} \mathbf{a}_x \text{ A/m}$ is incident on a PEC. The reflected magnetic vector is $\tilde{H}_r = 10e^{j\beta z} \mathbf{a}_x \text{ A/m}$.



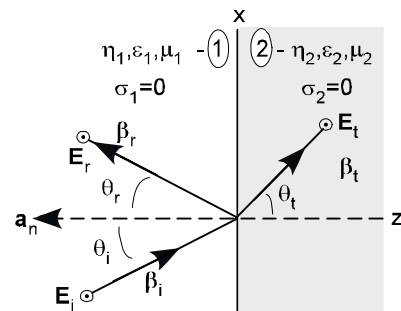___ Given that region 2 is free space, the above diagram is possible. **Why or why not?** _____



___ The result of a refraction experiment is shown above. Given this result, it is not possible for an incident wave in region 1 to be totally reflected.

Answers

1. ii) 16 V, iii) 20 V, iv) No. v) place 100 Ω resistor in parallel to 100 Ω source resistance to obtain match, 24 V
2. i) $\theta_t = 25.7^\circ$ ii) No, iii) 0.526, iv) 0.998
3. i) $0.446 \angle -63.5^\circ$ ($50 - j50$) Ω , ii) $0.0894 \angle 26.6^\circ$ A, $6.325 \angle -18.4^\circ$ V, iii) 0.2 W, iv) 0.2 W
4. T, T, (300 m, 200 Ω , open), (400 m, 50 Ω , RC with $R = 50$ Ω), (400 m, 25 Ω , 25 Ω), F, T, T, T, F