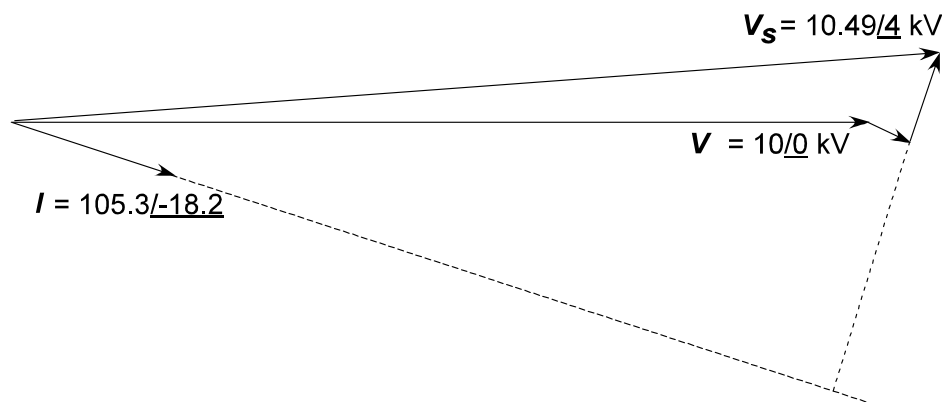


ECE370 POWER & ENERGY SYSTEMS

Homework Set 2

- 2.1 A **single-phase** source has a terminal voltage $V = 720/\underline{-40}^\circ$ V. It supplies a current of $I = 30/\underline{-10}^\circ$ A to an electrical load.
- Is the load lagging or leading?
 - Find the complex power supplied by the source.
 - Determine the real power and state whether the source is delivering or absorbing.
 - Determine the reactive power and state whether the source is delivering to the load or absorbing from the load.
 - Determine the impedance of the load and state whether it is inductive or capacitive.

- 2.2 A three-phase distribution feeder whose impedance is $2 + j8 \Omega$ supplies a load of 1000 kW/ph at 0.95 lag, 10kV (phase), 60 Hz.
- Determine the supply voltage and current and show that the phasor diagram is:



- Re-draw the phasor diagram (not necessarily to scale, but use a straight-edge) if the pf is 0.95 **lead** and the current magnitude stays constant at the value in part (a). Be sure to mark the values of the parameters that are indicated above.

- 2.3 A 3ϕ , 800 kVA, 2.4 kV, 60 Hz generator operates at rated terminal voltage and supplies rated current at a 0.8 **leading** power factor to a balanced 3ϕ load.
- Determine the real, reactive, and apparent power.
 - Determine the impedance per phase of the load if it is wye-connected.
 - Determine the impedance per phase of the load if it is delta-connected.

- 2.4 A 3ϕ load consists of a 150 hp motor operating at a power factor of 0.85 lagging with 93¼% efficiency. It is fed from a 440 V, 60 Hz supply. In parallel with this load is a 3ϕ capacitor bank that draws 50 kVAR. Find:
- Current in the load, the current in the capacitor bank, and total line current.
 - Resultant power factor.
- (1 hp = 746 W)

- 2.5 A three-phase motor load draws 30.4 kVAR with a pf of 0.65 lag, 230 V, 60 Hz. A capacitor bank is placed across the terminals to make the combined power factor 0.95 lagging.
- Determine the required kVAR rating of the capacitor bank.
 - Determine the line current before and after the capacitors are added.

- 2.6 Complete the Concept Quiz at the end of Chapter 2 in the course notes. Assume the systems are balanced and have positive sequence.

