

ECE370 POWER & ENERGY SYSTEMS

Homework Set 2 – Solutions

2.1 A **single-phase** source has a terminal voltage $V = 720\angle -40^\circ$ V. It supplies a current of $I = 30\angle -10^\circ$ A to an electrical load.

- a) Is the load lagging or leading?
- b) Find the complex power supplied by the source.
- c) Determine the real power and state whether the source is delivering or absorbing.
- d) Determine the reactive power and state whether the source is delivering to the load or absorbing from the load.
- e) Determine the impedance of the load and state whether it is inductive or capacitive.

a) $V = 720\angle -40^\circ$ and $I = 30\angle -10^\circ$ $\therefore \theta = -40 + 10 = -30^\circ$

i.e. current is 30° **ahead** of the voltage \therefore the load is **leading**


b) $S = 720\angle -40 \times 30\angle +10 = 21.6\angle -30 = 18.7 - j10.8$ kVA

c) $P = 18.7$ kW (delivered to load because it is positive)

d) $Q = 10.8$ kVAR (absorbed from load because it is negative)

e) $Z = \frac{V}{I} = \frac{720\angle -40}{30\angle -10} = 24\angle -30 \Omega = 20.79 - j12 \Omega$, this is **capacitive**

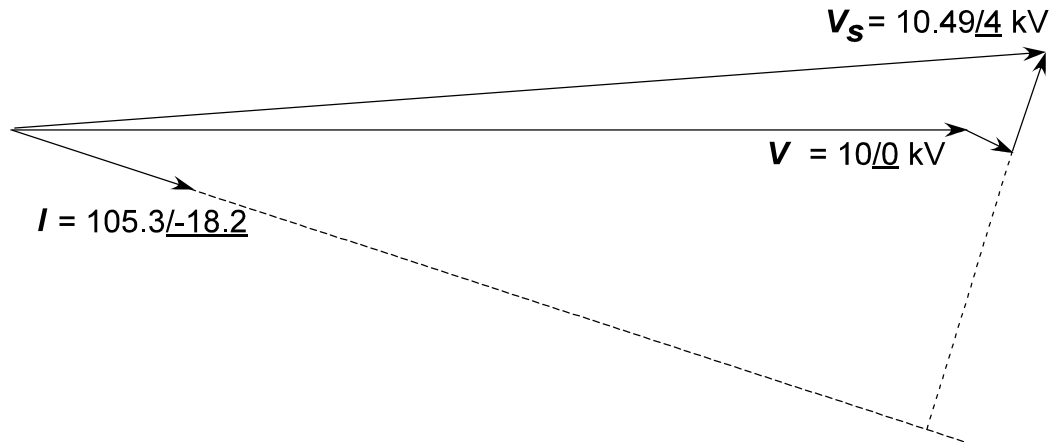- 2.2 A three-phase distribution feeder whose impedance is $2 + j8 \Omega$ supplies a load of 1000 kW/ph at 0.95 **lag**, 10kV (phase), 60 Hz.
- a) Determine the supply voltage and current and show that the phasor diagram is:




- b) Re-draw the phasor diagram (not necessarily to scale, but use a straight-edge) if the pf is 0.95 **lead** and the current magnitude stays constant at the value in part (a). Be sure to mark the values of all the parameters that are indicated above.

$I = 105.3 \angle +18.2$ A because the current is now leading.

and: $V_s = (2 + j8) \times 105.3 \angle +18.2 + 10 \times 10^3 \angle 0 = \boxed{9975 \angle 5 \text{ V}}$

The phasor diagram (not to scale) is:

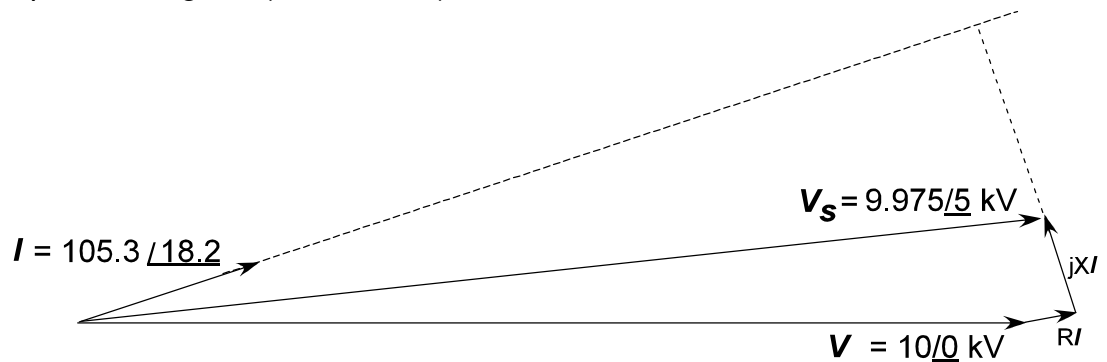

- 2.3 A 3 ϕ , 800 kVA, 2.4 kV, 60 Hz generator operates at rated terminal voltage and supplies rated current at a 0.8 **leading** power factor to a balanced 3 ϕ load.
- Determine the real, reactive, and apparent power.
 - Determine the impedance per phase of the load if it is wye-connected.
 - Determine the impedance per phase of the load if it is delta-connected.

a) $S = 800 \text{ kVA}$ (given) $\mathbf{S} = 800/\underline{\cos^{-1}0.8} = 800/\underline{-36.9^\circ} \text{ kVA} = 266\frac{2}{3}\angle-36.9 \text{ kVA/ph}$

$$P = 800\cos(-36.9) = 640 \text{ kW}$$

$$Q = 800\sin(-36.9) = -480 \text{ kVAR}$$

b) $V_\phi = \frac{2.4 \times 10^3 \angle 0}{\sqrt{3}} = 1386 \angle 0 \text{ V}$ $I_\phi = \frac{S_\phi^*}{V_\phi} = \frac{266.7 \times 10^3 \angle 36.9}{1386 \angle 0} = 192.5/\underline{36.9} \text{ A}$

$$\mathbf{Z}_Y = \frac{V_\phi}{I_\phi} \quad \text{so } |Z_Y| = \frac{1386}{192.5} = 7.2 \text{ } \Omega/\text{ph} \quad \text{and} \quad \boxed{\mathbf{Z}_Y = 7.2/\underline{-36.9} = 5.76 - j4.32 \text{ } \Omega/\text{ph}}$$

c) $\mathbf{Z}_\Delta = 3\mathbf{Z}_Y$ \therefore $\boxed{\mathbf{Z}_\Delta = 21.6/\underline{-36.9} = 17.28 - j12.96 \text{ } \Omega/\text{ph}}$

- 2.4 A 3ϕ load consists of a 150 hp motor operating at a power factor of 0.85 lagging with 93 $\frac{1}{4}$ % efficiency. It is fed from a 440 V, 60 Hz supply. In parallel with this load is a 3ϕ capacitor bank that draws 50 kVAR. Find:
- Current in the load, the current in the capacitor bank, and total line current.
 - Resultant power factor.
- (1 hp = 746 W)

a) $P_{\text{mech}} = 150 \times 746 = 111.9 \text{ kW}$ so $P_{\text{elec}} = \frac{P_{\text{mech}}}{\eta} = \frac{111.9}{0.9325} = 120 \text{ kW}$

$$P_L = 120 \text{ kW}, V_L = 440 \text{ V}, \text{PF}_L = 0.85 \text{ lagging}$$

$$Q_c = 50 \text{ kVAR}$$

$$\mathbf{I}_L = \frac{120,000 \angle -\cos^{-1} 0.85}{\sqrt{3} (440)(0.85)} = 185.2 \angle -31.8^\circ \text{ A}$$

$$\mathbf{I}_c = \frac{50,000 \angle 90^\circ}{\sqrt{3} (440)} = 65.6 \angle 90^\circ \text{ A}$$

$$\mathbf{I}_T = \mathbf{I}_L + \mathbf{I}_c = 185.2 \angle -31.8^\circ + 65.6 \angle 90^\circ = 160.6 \angle -11.49^\circ$$

b) $\text{PF} = \cos(11.49^\circ) = 0.98 \text{ lagging}$

- 2.5 A three-phase motor load draws 30.4 kVAR with a pf of 0.65 lag, 230 V, 60 Hz. A capacitor bank is placed across the terminals to make the combined power factor 0.95 lagging.
- Determine the required kVAR rating of the capacitor bank.
 - Determine the line current before and after the capacitors are added.

$$\text{pf} = 0.65 \text{ lag} \quad \therefore \quad \text{rf} = 0.7599 \quad \text{and} \quad S_M = \frac{Q}{\text{rf}} = \frac{30.4}{0.7599} = 40 \text{ kVA}$$

$$S_M = 40 \text{ kVA}, \quad V_M = 230 \text{ V}, \quad \text{PF}_M = 0.65 \text{ lagging}$$

$$P_M = 40 (0.65) = 26 \text{ kW}$$

$$\theta_M = \cos^{-1} 0.65 = 49.46^\circ$$

$$Q_M = P_M \tan \theta_M = 26 \tan 49.46^\circ = 30.4 \text{ kVAR}$$

$$\text{PF}_{\text{new}} = 0.95$$

$$\theta_{\text{new}} = \cos^{-1} 0.95 = 18.19^\circ$$

$$Q_{\text{new}} = P_M \tan \theta_{\text{new}} = 8.54 \text{ kVAR} = Q_M + Q_C$$


$$\therefore Q_C = Q_{\text{new}} - Q_M = 8.54 - 30.4 = -21.86 \text{ kVAR}$$

$$I_{\text{before}} = \frac{40,000}{\sqrt{3} (230)} \angle -\cos^{-1} 0.65 = 100 \angle -49.46^\circ$$

$$I_{\text{after}} = \frac{26,000}{\sqrt{3} (230) (0.95)} \angle -\cos^{-1} 0.95 = 68.7 \angle -18.19^\circ$$

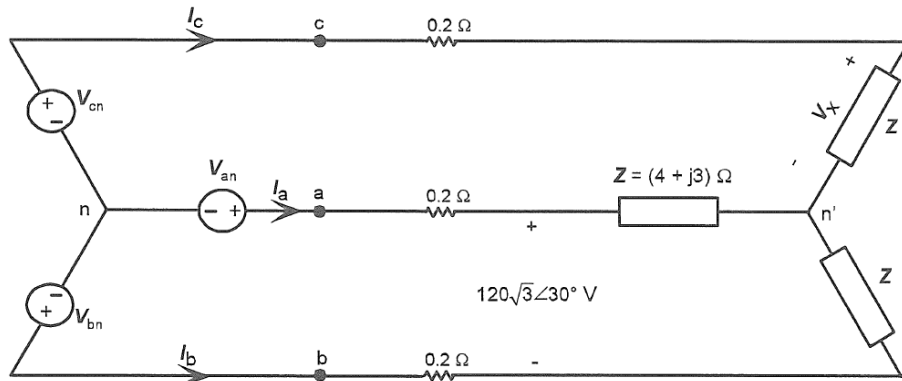
2.6 Complete the Concept Quiz at the end of Chapter 2 in the course notes. Assume the systems are balanced and have positive sequence.

The diagram below is used for the next five questions.



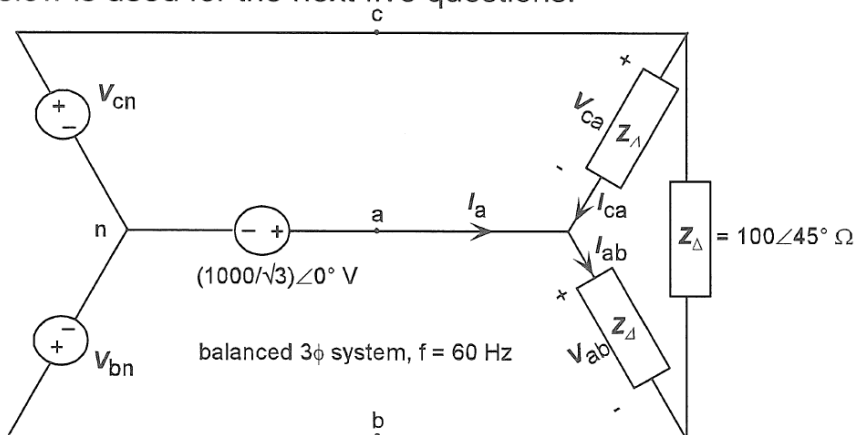- 1) **T/F** The magnitude of I_a is $24\sqrt{3}$ A **F** ($= 24A$)
- 2) **T/F** The power delivered to the load is 2304 W. **F** ($= 3 \times 2304W$)
- 3) **T/F** $\% \eta = \left(\frac{4000}{42} \right) \%$ **T**
- 4) **T/F** $V_x = 120 \angle 120^\circ$ V **T**
- 5) **T/F** The power factor of the load is 0.8 leading. **F** ($= 0.8 \text{ lag}$)

The diagram below is used for the next five questions.



- 6) **T/F** The instantaneous power delivered to the 3 ϕ load is independent of time. **T**
- 7) **T/F** $V_{bn} = (1000/\sqrt{3}) \angle -120^\circ$ V and $V_{ab} = 1000 \angle 30^\circ$ V **T**
- 8) **T/F** $I_{ab} = 10 \angle -45^\circ$ A **F** ($= 10 \angle -15$)
- 9) **T/F** $v_{ca}(t) = 1000\sqrt{2} \cos(2\pi 60t + 150^\circ)$ V **T**
- 10) **T/F** $P_{3\phi} = 10 \cos 45^\circ$ KW **F** ($= \sqrt{3} 10 \cos 45^\circ \text{ kW}$)