

ECE370 POWER & ENERGY SYSTEMS

Homework Set 7

- 7.1 A three-phase induction motor is supplied with power from a 60-Hz source. At full load the motor speed is 1728 rpm, and at no load the speed is nearly 1800 rpm. At full-load conditions, determine the following:
- a) Number of poles
 - b) Slip
 - c) Frequency of the rotor voltages
 - d) Speed of the rotor field with respect to the rotor
 - e) Speed of the rotor field with respect to the stator
 - f) Speed of the rotor field with respect to the stator field
- 7.2 A three-phase, 440-V, 60-Hz, wye-connected induction motor takes a stator current of 50 A at 0.8 power factor while running at its rated speed of 855 rpm. The stator loss is 2500 W, and the rotational losses are 3200 W. Calculate the efficiency of the motor.
- 7.3 A three-phase, 480 V, 60 Hz, wye-connected induction motor draws a **reactive power** of 18 kVAR at 0.8 lag pf and runs at 1158 rpm. The stator losses are 500 W and the rotational losses are 350 W. Determine:
- a) Rotor copper loss.
 - b) Shaft output torque and horsepower.
 - c) Efficiency.
 - d) Input current magnitude.

- 7.4 The following test results were obtained for a three-phase, 400 hp, 2.4 kV, eight-pole, wye-connected induction motor.
- a) Determine the exact equivalent circuit.

Test performed	Voltage (V)	Current (A)	Power (kW)
No-load	2400	9.3	29.1
Locked-rotor (performed at 15 Hz)	112.6	100	7.5
Rotational loss	-	-	19
DC (measured between phases a – b)	80	400	-

- b) **Estimate** the efficiency when rated load is supplied.

- 7.5 The equivalent circuit parameters of a three-phase, Y-connected induction motor are, $R_1 = 0.06 \Omega$, $R_2' = 0.14 \Omega$, $X_1 = X_2' = 1.17 \Omega$, $R_c = 585 \Omega$, $X_m = 58.5 \Omega$. The nameplate states: 1.247 kV, 60 Hz, 1176 rpm, with rotational losses of 6644 W. Determine:

- Magnitude of rated input current.
- Rated power factor.
- Rated shaft horsepower.
- Rated output torque.
- Rated efficiency.
- Starting current.
- Starting pf.