

ECE370 POWER & ENERGY SYSTEMS

Homework Sets 9 & 10, plus the Final Review – WOW!!

- 9.1 A three-phase, 440 V, six-pole, 60 Hz, wye-connected induction motor takes 18 kVAR at 0.8 lag pf and runs at a slip of 3.5%. The stator losses are 500 W and the rotational losses are 350 W. Determine:
- Rotor copper loss.
 - Shaft output torque and horsepower.
 - Efficiency.

- 9.2 The following test results were obtained for a three-phase, 100 hp, 440 V, eight-pole, wye-connected induction motor.
- Determine the exact equivalent circuit.

Test performed	Voltage (V)	Current (A)	Power (W)
No-load	440	38	3800
Locked-rotor (performed at 15 Hz)	80	110	4800
Rotational loss	-	-	1800
DC (measured between phases a – b)	8	50	-

- Estimate** the efficiency when rated load is supplied.

- 9.3 A three-phase, four-pole, 60 Hz induction machine is rated at 7.98 hp, 208 V, and 1755 rpm. The parameters of the equivalent circuit of the motor are:

$$\begin{array}{lll}
 R_1 = 0.15 \, \Omega & R_2 = 0.15 \, \Omega & R_c \text{ can be neglected} \\
 X_1 = 0.4 \, \Omega & X_2 = 0.25 \, \Omega & X_m = 30 \, \Omega
 \end{array}$$

The rotational losses are 500 W. For rated load calculate:

- Line current and power factor.
- Output torque.
- Efficiency of the motor.
- Starting current and torque.

- 9.4 A three-phase, 440 V, 60 Hz, four-pole, wound-rotor induction motor has a stator impedance of $1.0 + j 1.6 \Omega/\text{ph}$. The rotor impedance referred to the stator is $0.8 + j 1.4 \Omega/\text{ph}$. Core-loss resistance can be neglected and magnetizing reactance is $30\Omega/\text{ph}$. Determine:
- The maximum torque developed by the motor and the speed at which it occurs if no additional external rotor resistance is applied.
 - Additional external resistance needed to make T_{max} occur at start-up, if the actual rotor resistance is measured through the slip-rings as $0.4 \Omega/\text{phase}$.
- 9.5 A three-phase induction motor is rated: 480 V, 25 hp, 3450 rpm. It is used to drive a compressor rated: 30 hp, 3600 rpm. The power input of the compressor is proportional to speed³ (speed cubed). Determine the hp output of the motor and its speed in rpm.
- 9.6 A bank of three identical single-phase transformers is to be used to transform a 34.5 kV three-phase supply down to 12.47 kV. Each transformer is rated 12 MVA, 34.5 kV to 7.2 kV.
- Draw a diagram showing how each transformer should be connected. Be sure to mark the polarity of each winding.
 - What is the MVA rating of the three-phase bank?
 - What are the primary and secondary rated line currents?
- 9.7 A 1200 V dc shunt motor is rated at 500 hp, 3000 rpm. It has an armature resistance of 0.17Ω and a total field circuit resistance of 120Ω . It draws a current of 350 A from the supply when delivering rated load. Ignore magnetic saturation and determine:
- Rated output torque.
 - Rated developed torque.
 - Rated efficiency.
 - Rotational losses at rated speed.
 - Line current when the load is changed, causing the speed to become 3067 rpm. (Field resistance is unaltered.)
 - Developed torque for the conditions in part (e).
 - Horsepower output for the conditions in (e) if the rotational losses are proportional to speed².

- 9.8 A 600 V dc series motor is rated at 250 hp, 2000 rpm. It has an armature resistance of 0.1Ω and a field resistance of 0.05Ω . It draws a current of 360 A from the supply when delivering rated load. Ignore magnetic saturation and determine:
- Rated output torque.
 - Rated developed torque.
 - Rated efficiency.
 - Rotational losses at rated speed.
 - Speed when the load is changed, causing the line current to drop to 180 A.
 - Developed torque for the conditions in part (e).
 - Horsepower output for the conditions in (e) if the rotational losses are proportional to speed².
 - Efficiency for the conditions in part (e).
- 9.9
- A solar energy system consists of eight panels that are 15% efficient and each one is 2 m by 1.5 m. At noon, the zenith angle is 20° , the transmittance of gasses is 73%, the water vapor absorption is 8%, and the transmittance of aerosol is 85%. Calculate:
 - Power density
 - Solar efficiency
 - Power output of the system.
 - The solar power density at the site in part (a) is: $\rho = 0.7e^{-(t-12)^2/18} \text{ kW/m}^2$.
 - What is the daily energy produced?
 - What is the power output of the array at 3:00 p.m.?
- 9.10 The induction machine in problem 9.3 is used as a generator that is driven by a wind turbine with a blade length of 10 m and fixed TSR of 0.75. It is required to produce power when wind speed is above 3 m/s, which corresponds to a generator slip of 0.4% ($s = -0.004$). Calculate the necessary gear ratio and the real and reactive power at the rated slip of 2.5% ($s = -0.025$).