

ECE470 POWER SYSTEMS I

Homework Set 1


1. Using 100 MVA and 115 kV as base values, express 138 kV, 50 MVA, 251 A, and 52.9 Ω in per-unit.
2. The per-unit impedance of an electric load is 1.5. The base power is 750 kVA, and the base voltage is 13.8 kV.
 - a) Find the per-unit impedance of the load if 1500 kVA and 27.6 kV are selected as base values.
 - b) Find the ohmic value of the impedance.
3. A 750 MVA, 25 kV ac generator has a synchronous reactance of 1.5 per unit. The generator is connected to a circuit for which the specified bases are 100 MVA, 500 kV. Find:
 - a) The per-unit value of the generator synchronous reactance on the specified bases.
 - b) The ohmic value of the synchronous reactance.
4. A single-phase source is connected to an electrical load. The load draws a 0.6 pu current at 1.10 pu voltage while taking a real power of 0.4 pu at a lagging power factor. Choose a base voltage of 8 kV and a base current of 125 A. Calculate the following:
 - a) Real power in kW.
 - b) Reactive power in kVAR.
 - c) Power factor.
 - d) The ohmic values of the resistance and the reactance of the load (assume series).

5.

The single-line diagram of a 3 ϕ power system is shown below. The system data, on equipment rating bases are:

Generator 1:	20 MVA,	13.8 kV,	$X_s'' = 0.2$ pu
Generator 2:	30 MVA,	18 kV,	$X_s'' = 0.2$ pu
Generator 3:	30 MVA,	20 kV,	$X_s'' = 0.2$ pu
Transformer T_1 :	25 MVA,	13.8/220 kV,	$X = 10\%$
Transformer T_2 : (3x1 ϕ)	10 MVA,	18/127 kV,	$X = 10\%$
Transformer T_3 :	35 MVA,	22/220 kV,	$X = 10\%$
Line L1	80 Ω , 220 kV		
Line L2	100 Ω , 220 kV		

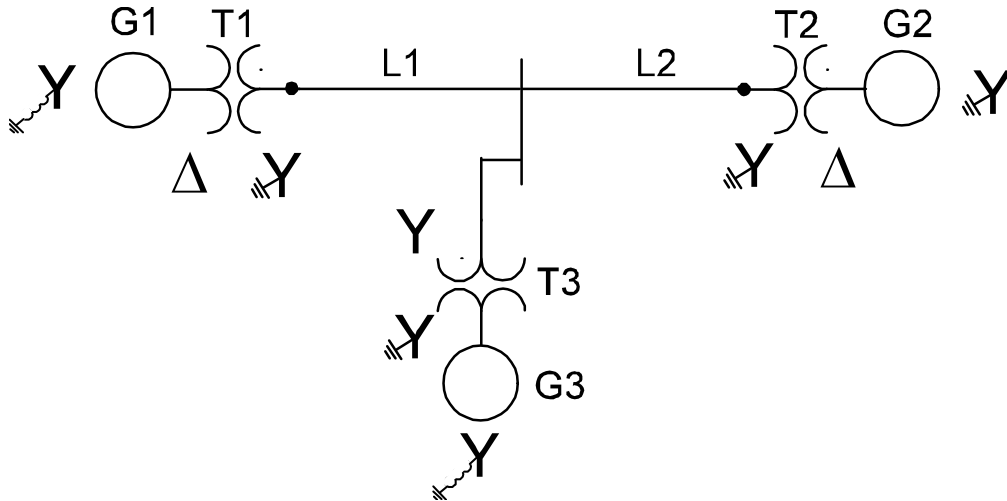Using 50 MVA, 13.8 kV base in the circuit of generator 1, draw the impedance diagram with all reactances marked in pu.



6.

The single-line diagram of a 3 ϕ power system is shown below. The system data, on equipment rating bases are:

G1	18 kV	20 MVA	$X = 0.2$
G2	18 kV	20 MVA	$X = 0.2$
G3	13.8 kV	30 MVA	$X = 0.2$
3 ϕ Y – Y Trans.	20/138 kV	20 MVA	$X = 10\%$
3 ϕ Y – Δ Trans.	13.8/138 kV	15 MVA	$X = 10\%$
L1-2	138 kV		$X = 40 \Omega$
L1-3	138 kV		$X = 20 \Omega$
L2-3	138 kV		$X = 20 \Omega$

Draw the impedance diagram using 50 MVA, 138 kV base in the zone of each line.

