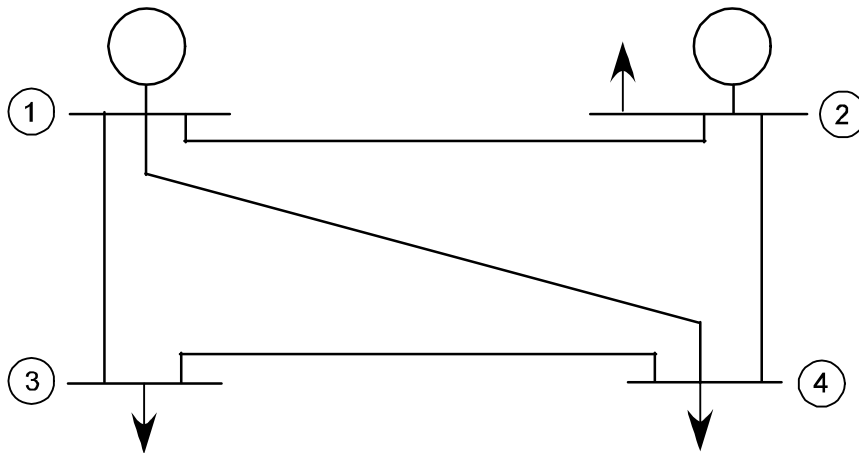


ECE470 POWER SYSTEMS I

Homework Set 7

Complete the Load Flow lab work, plus the following questions.

1.
 - a) Load Flow analysis was performed on the system shown below and the results are presented in tables 1 & 2. Determine:
 - i) the current (A or kA) received at bus 3 from bus 4,
 - ii) the current (A or kA) flowing out of generator 2, and
 - iii) the power factor of generator 1.
 - b) Another load flow was run with one line removed for maintenance; the results are shown in table 3. If losses cost \$80/MWh and the outage lasts for ten weeks, how much is the increase in losses costing the utility? (Assume the loads are constant).
 - c) It was decided to install capacitors at bus 4 during the outage. The results of a load flow are shown in table 4. Determine:
 - i) The MVAR rating of the capacitor bank.
 - ii) The capacitance/phase for wye-connected capacitors.
 - iii) The saving in cost of losses achieved by installing the capacitors for the outage period.



$$V_B = 500 \text{ kV}$$

$$S_B = 500 \text{ MVA}$$

Table 1

BUS#	MAG pu	ANGLE degrees	PG pu	QG pu	PL pu	QL pu
1	1.050	0.000	2.050	1.950	0.400	0.300
2	1.050	2.040	1.500	0.550	1.200	0.800
3	0.985	-2.213	0.000	0.000	1.000	0.600
4	0.975	-3.141	0.000	0.000	0.800	0.500
TOTAL			3.550	2.500	3.400	2.200

Table 2

LINE #	BUS TO	BUS	P	Q	S
1	1	2	0.797	1.047	1.316
	2	1	-0.705	-0.636	0.950
2	1	3	0.695	0.892	1.131
	3	1	-0.601	-0.219	0.640
3	1	4	0.554	0.014	0.554
	4	1	-0.334	0.080	0.343
4	2	4	1.005	0.386	1.077
	4	2	-0.761	-0.865	1.152
5	3	4	-0.399	-0.381	0.552
	4	3	0.295	0.285	0.410


Table 3

BUS#	MAG pu	ANGLE degrees	PG pu	QG pu	PL pu	QL pu
1	1.050	0.000	2.180	1.823	0.400	0.300
2	1.050	-4.797	1.500	0.880	1.200	0.800
3	0.933	-8.945	0.000	0.000	1.000	0.600
4	0.953	-6.193	0.000	0.000	0.800	0.500
TOTAL			3.680	2.703	3.400	2.200

Table 4

BUS#	MAG pu	ANGLE degrees	PG pu	QG pu	PL pu	QL pu
1	1.050	0.000	2.000	1.770	0.400	0.300
2	1.050	-3.775	1.500	0.670	1.200	0.800
3	0.964	-13.073	0.000	0.000	1.000	0.600
4	0.980	-16.862	0.000	0.311	0.800	0.500
TOTAL			3.500	2.751	3.400	2.200

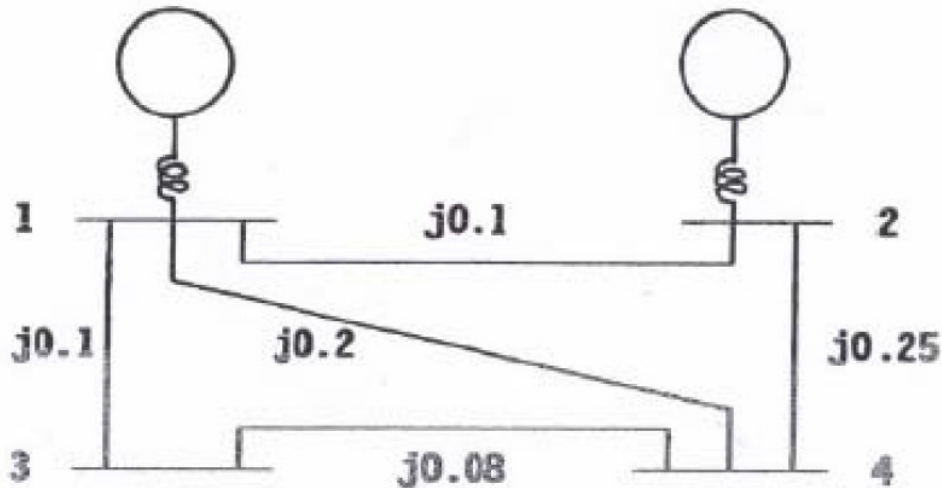2. The impedances in the system below are in pu on a base of 200 MVA, 115 kV. Both generators have 0.5 pu sub-transient reactance. Ignoring the effect of any loads, use the $[Y_{bus}]$ matrix derived in last week's HW to determine:
- the nominal balanced 3 ϕ fault level at each bus, and
 - the current flowing from bus 1 to bus 4 when bus 4 is faulted.



3. The impedances in the system below are in pu on a base of 100 MVA, 230 kV, both loads are rated at $S = 0.5$ pu, zpf (i.e., they are 0.5 pu when their voltages are 1 pu). The excitation voltage at generator 1 is 276 kV and at generator 2 it is 253 kV. Both generators have 0.5 pu synchronous reactance as shown. Ignoring the effect of any loads:
- use the $[Y_{bus}]$ matrix derived in last week's HW to determine the nominal balanced 3 ϕ fault level at bus 3 and the currents flowing from busses 1 and 4; and
 - remove the capacitor bank at bus 3 and repeat part (a).

