

ECE471 INDUSTRIAL POWER SYSTEMS Homework Set 3

From chapter 6 of the course text, turn in problems 4 and 5.

- 6.4. Refer to Figure 6.2(a). The transformer is 1000 kVA, its impedance is 5.75%, the primary feeder impedance is 0.75%, and the secondary voltage is 480Y/277 V. Calculate the short-circuit current on the secondary of the transformer under three-phase bolted fault conditions.

$$Z_s = 0.0075 + 0.0575 = 0.0650 \text{ p.u.}$$

$$I_{sc} = \frac{1.0}{0.0650} = 15.38 \text{ p.u.}$$

$$I_s \text{ (of transformer)} = \frac{1000 \times 1000}{1.732 \times 480} = 1203 \text{ A}$$

$$I_{sc} = 1203 \times 15.38 = 18,500 \text{ A symm.}$$

- 6.5. Repeat Problem 4, except the transformer is 1500 kVA, its impedance is 5.0%, and the primary feeder impedance is 0.5%.

$$Z_s = 0.005 + 0.050 = 0.055 \text{ p.u.}$$

$$I_{sc} = \frac{1.0}{0.055} = 18.18 \text{ p.u.}$$

$$I_s \text{ (of transformer)} = \frac{1500 \times 1000}{1.732 \times 480} = 1804 \text{ A}$$

$$I_{sc} = 1804 \times 18.18 = 32,800 \text{ A symm.}$$

From chapter 16 of the course text, turn in problems 2 and 3.

16.2. Power is supplied over a primary feeder to a 13,800-208Y/120 V, 500 kVA unit substation. The impedance of the transformer is 5.0%. The utility system short-circuit capability is 150,000 kVA. Assume 50% of the load is motors. Calculate the available short-circuit current at the main secondary bus of the substation.

$$I_s \text{ (of transformer)} = \frac{500 \times 1000}{1.732 \times 208} = 1388 \text{ A}$$

$$Z_U = \frac{500}{150,000} = 0.0033 \text{ p.u.}$$

$$Z_{UT} = 0.050 + 0.0033 = 0.0533 \text{ p.u.}$$

$$I_T = \frac{1.0}{0.0533} = 18.76 \text{ p.u.} = 18.76 \times 1388 = 26,038 \text{ A}$$

$$\text{Motor load is 50\%; } \Sigma I_M = 4 \times (0.5 \times 1388) = 2776 \text{ A}$$
$$I_{SC} = 26,038 + 2776 \approx 28,800 \text{ A sym.}$$

16.3. Repeat Problem 2, except the secondary voltage is 480Y/277 V and motor load is 100%.

$$I_s \text{ (of transformer)} = \frac{500 \times 1000}{1.732 \times 480} = 601 \text{ A}$$

From problem 2; Z_{UT} is 0.0533 p.u. and $I_T = 18.76$ p.u.


$$I_T = 18.76 \times 601 = 11,275 \text{ A}$$

Motor load is 100%; $\Sigma I_M = 4 \times 601 = 2404 \text{ A}$

$$I_{SC} = 11,275 + 2404 \approx 13,700 \text{ A sym.}$$

Point out the much lower level of available fault current for the 480 volt system as compared to that in Problem 2 for the 208 volt system. This is another very important consideration in selecting the highest possible secondary voltage for distributing the power within a building.

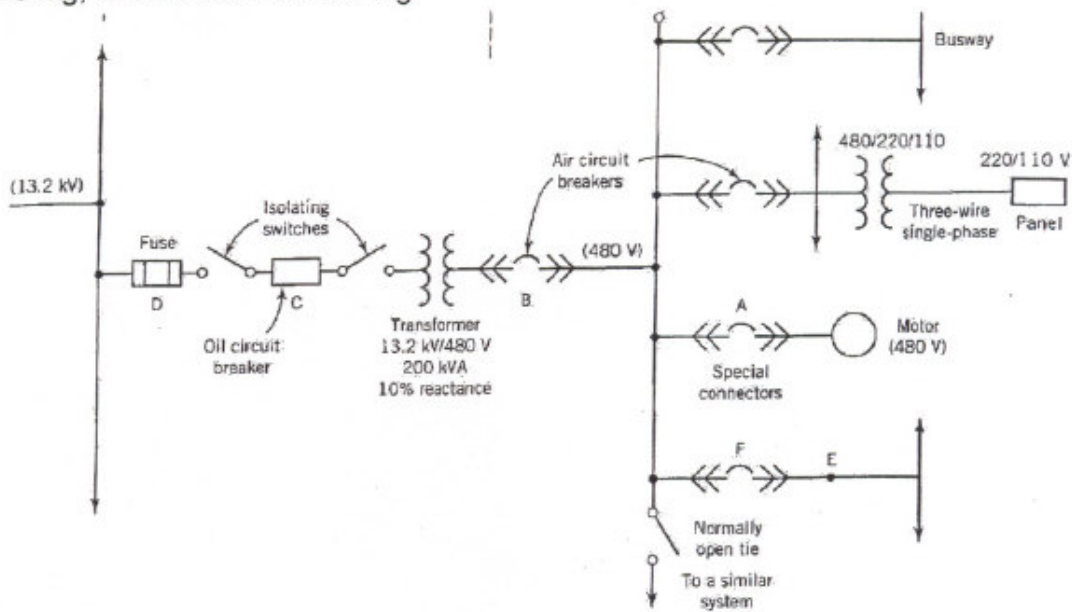The next problems refer to the following diagram, in which the four load groups on the right-hand side take respectively: 34 kVA @ 0.84 lag, 20 kVA @ 0.97 lag, 60 kVA (motor) @ 0.78 lag, and 38 kVA @ 0.89 lag.



1.

What is the current and power factor at the 13.2 kV supply?

Collect the loads together:-

$$L1: 34 \angle 32.9^\circ = 28.56 + j18.45 \text{ kVA}$$

$$L2: 20 \angle 14^\circ = 19.40 + j4.86 \text{ kVA}$$

$$L3: 60 \angle 38.7^\circ = 46.80 + j37.55 \text{ kVA}$$

$$L4: 38 \angle 27.1^\circ = 33.82 + j17.33 \text{ kVA}$$

$$\underline{128.58 + j78.18 \text{ kVA} = 150.5 \angle 31.3}$$

$$\text{At the supply: } \tilde{I} = \left(\frac{56}{V_{\phi}} \right)^* = \frac{150.5 \times 10^3 \angle -31.3}{\frac{13.2 \times 10^3}{\sqrt{3}}}$$

$$\boxed{\tilde{I} = 6.58 \angle -31.3 \text{ A}}$$

$$\boxed{\text{pf} = \cos(31.3) = 0.854 \text{ lag}}$$


2.
What is the pu loading on the main 200 kVA transformer?

The base rating is 200 kVA and the load is 150.5 kVA

$$\therefore S_{pu} = \frac{150.5}{200} = \boxed{0.752 \text{ pu}}$$

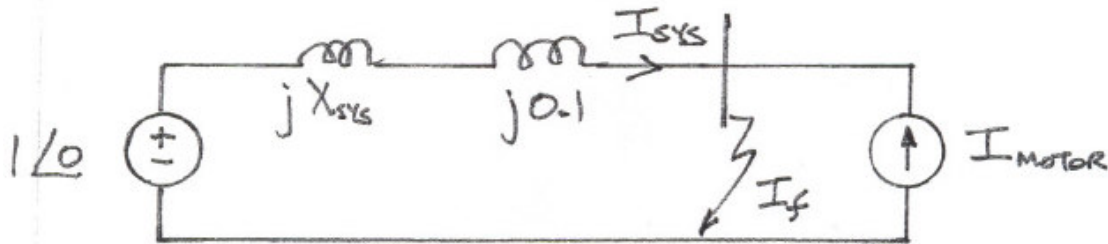3.
If the three-phase fault level at the 13.2 kV bus is 26.4 kA, what will be the fault level at the 480 V bus?

Only the motor and utility contribute to the fault, so the 1 ϕ equivalent is:



$$\text{On } 13.2 \text{ kV side } I_{BP} = \frac{200 \times 10^3}{\sqrt{3} \times 13.2 \times 10^3} = 8.75 \text{ A}$$

$$\therefore \text{Fault level @ utility} = \frac{26.4 \times 10^3}{8.75} = 3018 \text{ pu}$$

$$\therefore X_{sys} = \frac{1}{3018} = 0.0003 \text{ pu}$$

$$I_{sys} = \frac{1}{0.0003} = 9.967 \text{ pu on } 480 \text{ V side}$$

$$I_{BS} = \frac{200 \times 10^3}{\sqrt{3} \times 480} = 240.6 \text{ A} \quad \therefore I_{sys} = 2398 \text{ A}$$

$$\text{Motor FLA} = \frac{60 \times 10^3}{\sqrt{3} \times 480} = 72.2 \quad \therefore I_{motor} = 288.7 \text{ A}$$

$$\boxed{I_f = 2686 \text{ A}}$$