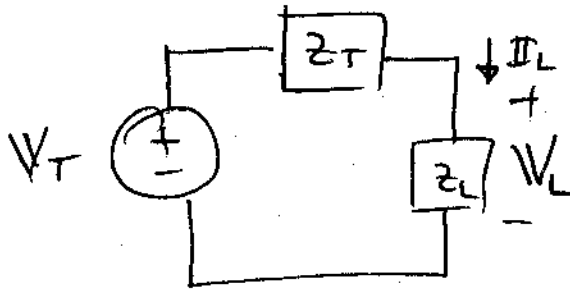


Max power in AC steady state:

$$I_L = \frac{V_T}{Z_T + Z_T^*} = \frac{V_T}{2 \operatorname{Re}\{Z_T\}}$$

$$V_L = \frac{Z_T^*}{Z_T^* + Z_T} V_T = \frac{Z_T^*}{2 \operatorname{Re}\{Z_T\}} V_T$$

$$\text{Set } Z_L = Z_T^*$$

(NOTE: V_L , I_L are RMS quantities)

$$S_{\max} = V_L I_L^* = \left[\frac{Z_T^*}{2 \operatorname{Re}\{Z_T\}} V_T \right] \cdot \left[\frac{V_T}{2 \operatorname{Re}\{Z_T\}} \right]^*$$


$$S_{\max} = \frac{Z_T^* |V_T|^2}{4 \operatorname{Re}\{Z_T\}^2} = \frac{(\operatorname{Re}\{Z_T\} - j \operatorname{Im}\{Z_T\}) |V_T|^2}{4 \operatorname{Re}\{Z_T\}^2}$$

$$P_{\max} = \operatorname{Re}\{S_{\max}\}$$

$$= \frac{\operatorname{Re}\{Z_T\} |V_T|^2}{4 \operatorname{Re}\{Z_T\}^2}$$

$$P_{\max} = \frac{\overset{\text{RMS}}{|V_T|^2}}{4 \operatorname{Re}\{Z_T\}} = \frac{\overset{\text{peak}}{|V_T|^2}}{4 \operatorname{Re}\{Z_T\}} = \frac{\overset{\text{peak}}{|V_T|^2}}{8 \operatorname{Re}\{Z_T\}}$$

* In general:

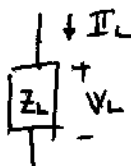


$$P = |V_L| \cdot |I_L| \cos \theta$$

RMS

phase of voltage waveform
minus
phase of current waveform
(phase difference)

OVER

Max power (easier way!)

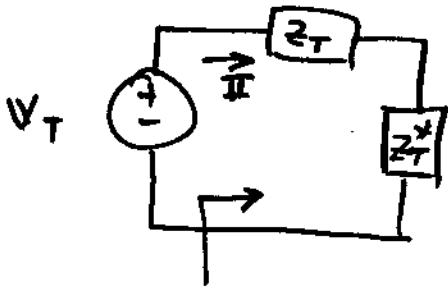

- ① Find impedance seen by source ($= 2\text{Re}\{z_T\}$)
- ② Observe that $\frac{1}{2}$ the power delivered by V_T makes it to the load
- ③ Write expression for power delivered by V_T & \div by 2:

$$S_{\max} = \frac{V_T I^*}{2} = \frac{V_T}{2} \left(\frac{V_T}{2\text{Re}\{z_T\}} \right)^*$$

$$\Rightarrow S_{\max} = \frac{|V_T|^2}{4\text{Re}\{z_T\}}$$

↑
this is always a pure real #,
so it must be P_{\max}

$$\Rightarrow P_{\max} = \frac{|V_{\text{TRMS}}|^2}{4\text{Re}\{z_T\}}$$