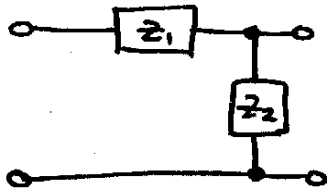



s-Domain Tinker Toys

* NOTE: $H(s) = \frac{V_{out}(s)}{V_{in}(s)}$ = transfer function
(zero-state frequency response)


Step 1: Choose a network:



$$H(s) = \frac{z_2}{z_1 + z_2}$$

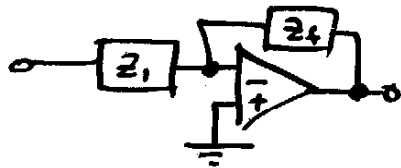

$$H(s) = -\frac{z_f}{z_1}$$

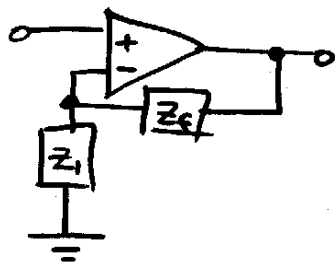


$$H(s) = 1 + \frac{z_f}{z_1} = \frac{z_1 + z_f}{z_1}$$

This method is easiest for designing circuits with inductors

Step 2: Choose appropriate impedance elements:




$$z = R$$

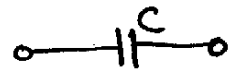

$$z = \frac{1}{C s}$$




$$z = L s$$

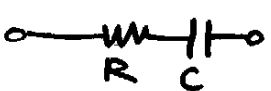


$$z = R + \frac{1}{C s}$$



$$z = R + L s$$

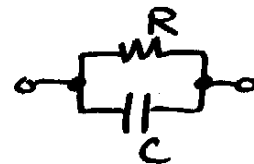
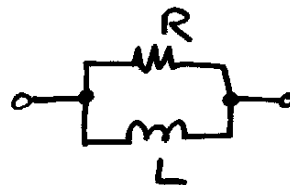
$$z = \frac{1}{\frac{1}{R} + Cs} = \frac{1}{Cs + 1/R} = \frac{1/C}{s + 1/RC}$$




$$z = \frac{1}{\frac{1}{R} + \frac{1}{Ls}} = \frac{R L s}{s + R/L}$$

(OVER →)




Best method for capacitors \Rightarrow work with admittances:


Step 1 : Choose a network:

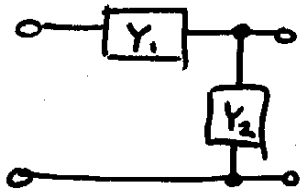
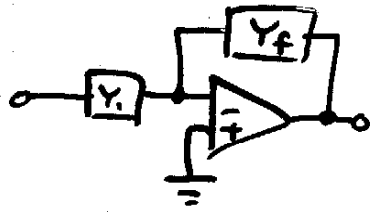
$$H(s) = \frac{\frac{1}{Y_2}}{\frac{1}{Y_1} + \frac{1}{Y_2}} = \frac{\frac{1}{Y_2}}{\frac{Y_2 + Y_1}{Y_1 Y_2}} = \frac{Y_1}{Y_1 + Y_2}$$



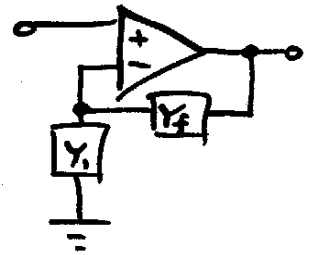
$$H(s) = -\frac{\frac{1}{Y_f}}{\frac{1}{Y_1}} = -\frac{Y_1}{Y_f}$$




$$H(s) = 1 + \frac{\frac{1}{Y_f}}{\frac{1}{Y_1}} = 1 + \frac{Y_1}{Y_f} = \frac{Y_f + Y_1}{Y_f}$$

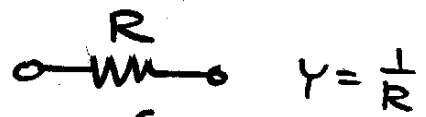Step 2 : Choose appropriate admittance elements:



$$Y = \frac{1}{R}$$

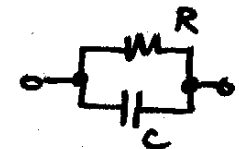


$$Y = \frac{1}{R} + Cs$$




$$Y = Cs$$



$$Y = \frac{1}{R} + \frac{1}{Ls}$$

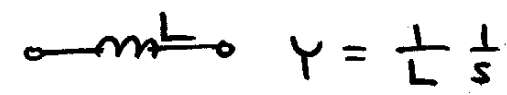


$$Y = \frac{1}{Ls}$$

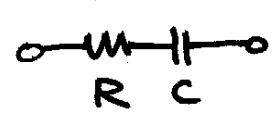

$$Y = \frac{1}{R + \frac{1}{Cs}} = \frac{Cs}{RCs + 1} = \frac{1}{R} \frac{s}{s + \frac{1}{RC}}$$

} dual of parallel RL

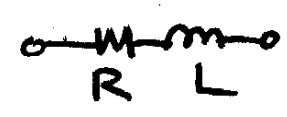

$$Y = \frac{1}{R + Ls} = \frac{1/L}{s + R/L}$$

} dual of parallel RC

