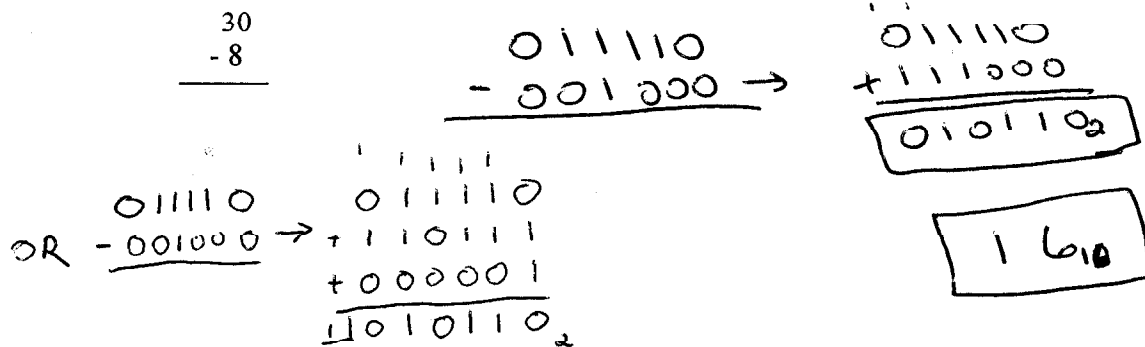


# Homework 1 - ECE Review

## Problem 1


Perform the following arithmetic using 6 bit 2's complement numbers. Provide the answer in binary and hexadecimal form.




## Problem 2

Design a 4-bit arithmetic block that performs the following functions. You may only use muxes, NOR gates, and 4 full adders. Assume all inputs are 4-bit binary numbers in 2's complement form.

$S_1 S_0$	function
0 0	A+B
0 1	A-B
1 0	A+1
1 1	A-1

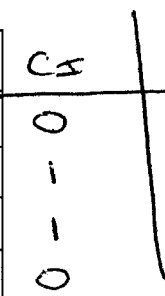

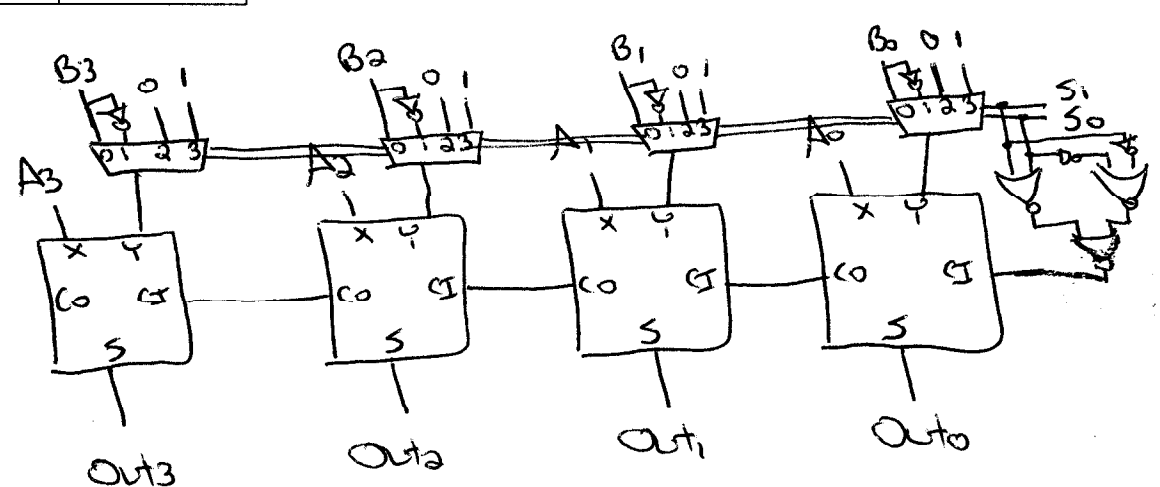
$$C_S = (S_1 + S_0)(\bar{S}_1 + \bar{S}_0) = \overline{(S_1 + S_0)(\bar{S}_1 + \bar{S}_0)}$$




To get an inverter with NOR:

A	B	A+B	$\overline{A+B}$
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

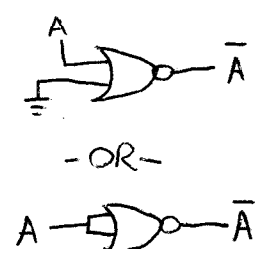



alternatively:

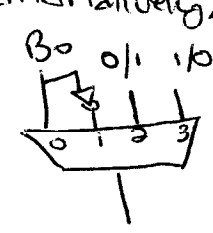

$C_S$
0
1
1
0
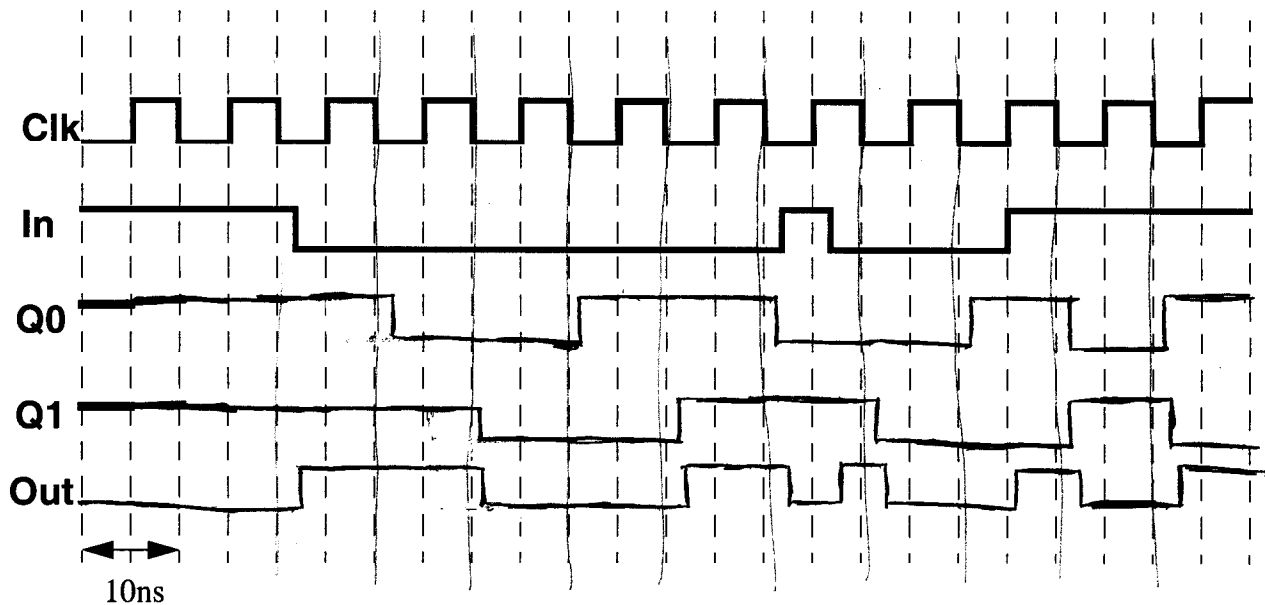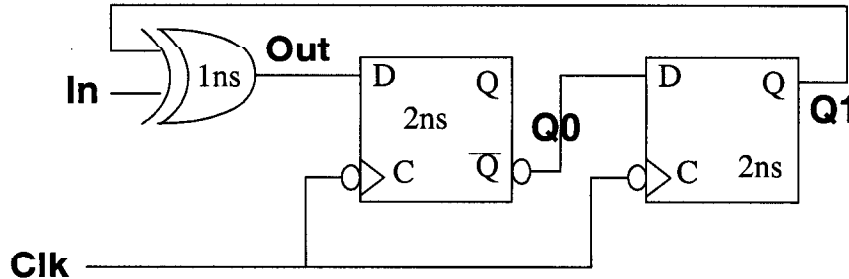
### Problem 3

Complete the timing diagram for the following circuit. Assume that the flip-flops have a 2ns delay each and that the XOR gate has a 1ns delay. Both flip-flops are negative edge triggered. Q0 and Q1 are initially high. Assume there are no set-up or hold violations.



### Problem 4

An electronic lock is controlled by a keypad that has three buttons labelled **A**, **B**, and **R**. The keypad is restricted such that, at most, one key can be pressed at a time, and that each keypress generates an input signal that lasts for only one clock cycle. A state machine takes the keypresses as input, and its output is either lock (**L**) or unlock (**U**). If the correct sequence of keys is typed and followed by an **R**, the state machine generates an unlock (**U**) signal and then resets. At any other time the output should be locked (**L**). If an incorrect sequence of keys is pressed the lock becomes inactive until the reset (**R**) key is pressed, at which point the lock resets (with no unlock signal).

(a) Create state diagram for a MOORE machine that will test for the correct key sequence is BBA. Label your inputs A, B, R, and O (for no key pressed). Label your output L or U. Label your states

with words such as "reset" and "inactive," or with partial key sequences such as "BBA." Make sure that all possible transitions exist.

(b) How many flip-flops are necessary to implement this state machine if the outputs are one-hot encoded? Explain your answer. *need 1 F.F. for each state*

*⇒ need 6 F.F.*

(c) How many flip-flops are necessary to implement this state machine if the states are binary encoded? Explain your answer. *need 6 states,  $2^3 = 8 \Rightarrow$  need 3 flip-flops*  
*000, 001, 010, 011, 100, 101 } 6 states*


(d) Show how the state diagram would change for a Meely implementation? *See next page*


(e) How many flip-flops are necessary to implement the Meely state machine if the states are one-hot encoded? Explain your answer. *need 5 F.F. because have 5 states*

(f) How many flip-flops are necessary to implement the Meely state machine if the states are binary encoded? Explain your answer. *still need 3 flip-flops to encode 5 states: 000, 001, 010, 011, 100*

(g) Under what circumstances would a designer choose the Moore implementation? The Meely implementation? *see next page*

A)

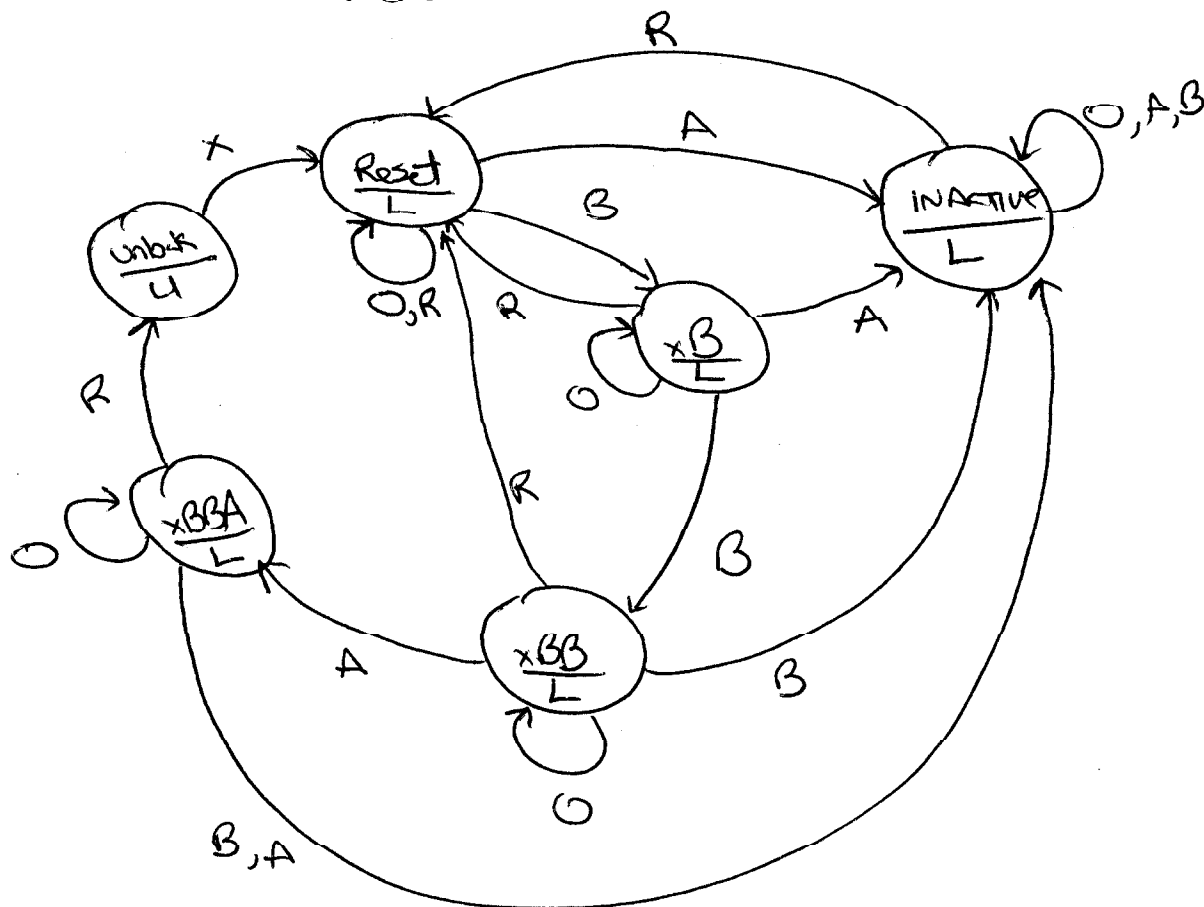

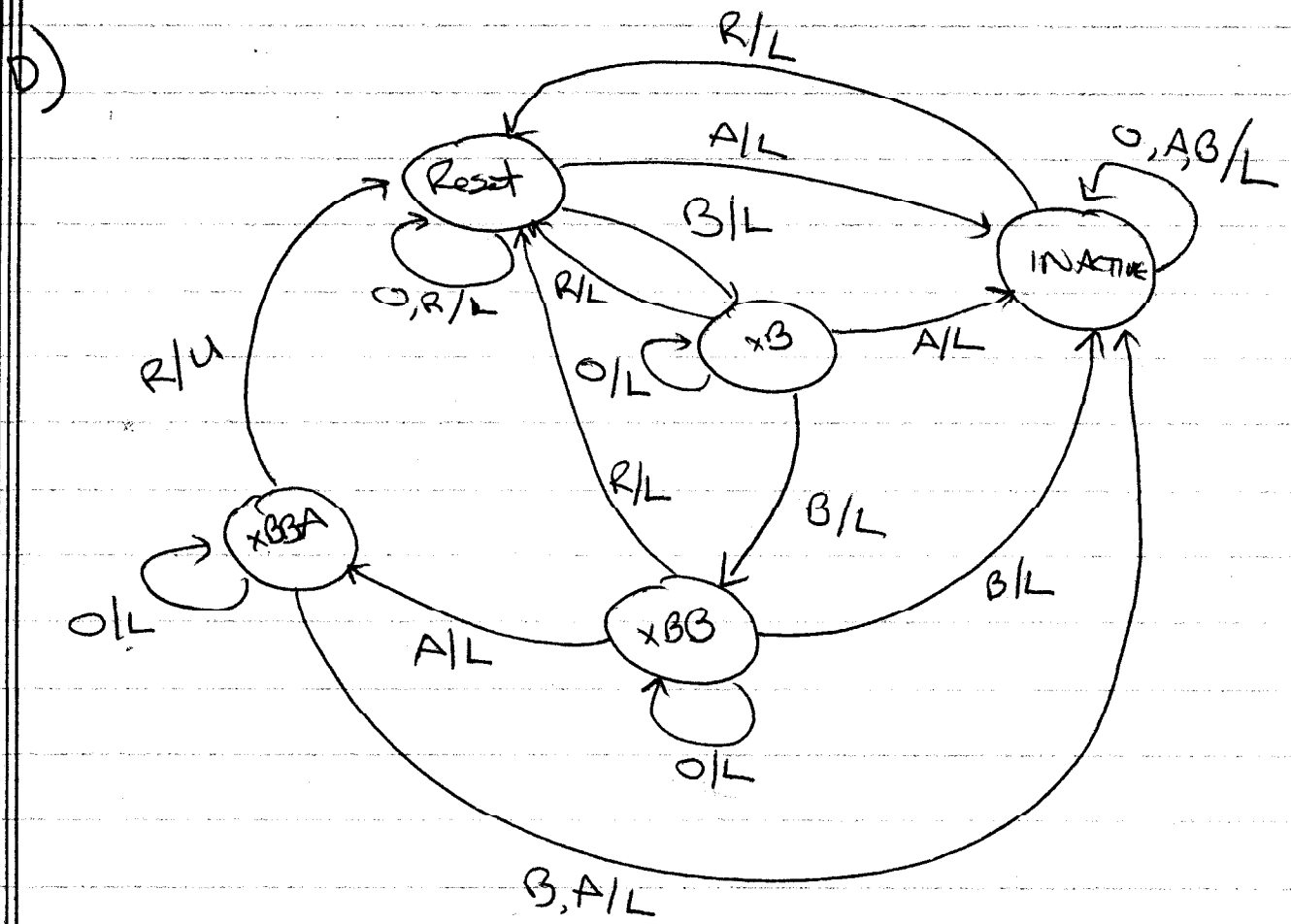

G) Moore implementation is always necessary if you are concerned about the output changing if the inputs changes (i.e., output change not tied to the clock)

⇒ if going to another system that is clocked, not necessary

Mealy implementation is # of G.F. is a serious concern and you are using one-hot encoding.