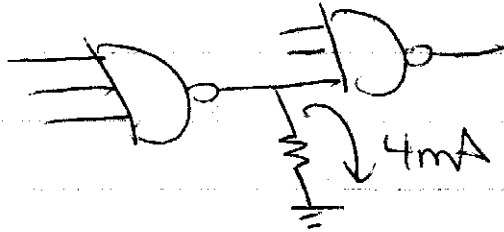


# Homework 5 Solutions

Problem 1:

a)



high state  $NM = V_{OH} - V_{IH}$

$V_{OH}$  will source 4mA,

so from data sheet,

worst case  $V_{OH} \stackrel{V_{OH}}{\text{at}} 4\text{mA load @ } 4.5\text{V supply}$   
 $= \text{~~3.7V~~ } 3.7\text{V}$

$$V_{IH} = 3.15\text{V}$$

$$\text{high state } NM = 3.7 - 3.15 = 0.55\text{V}$$

low state  $NM = V_{IL} - V_{OL}$

when  $V_{out} = 0$ , no  $I$  sourced, so


$$V_{OL} = 0\text{V}$$

$$V_{IL} = 1.35$$

$$\text{low state } NM = 1.35 - 0 = 1.35\text{V}$$

b) assuming gate is sinking  
 or sourcing 4mA,  
 worst case  $V_{OL} = 0.4V$   
 worst case  $V_{OH} = 3.7V$

3-input NAND gate looks like:

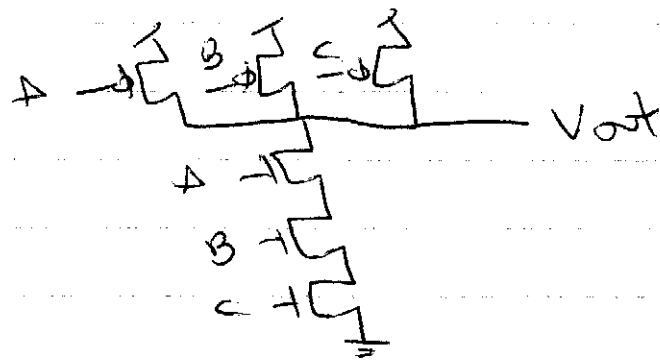


If  $R_{dsN} = R_{dsP} = 10\Omega$  as we  
 have previously assumed,  
 $V_{OH} > V_{DD} - V_{OH}$  because  
 $R_{dsN}$ 's are in series

however, as shown above,  
 $V_{OL} = 0.4 < V_{DD} - V_{OH} = 0.8V$

Therefore,  $R_{dsN} < R_{dsP}$

Problem 2:

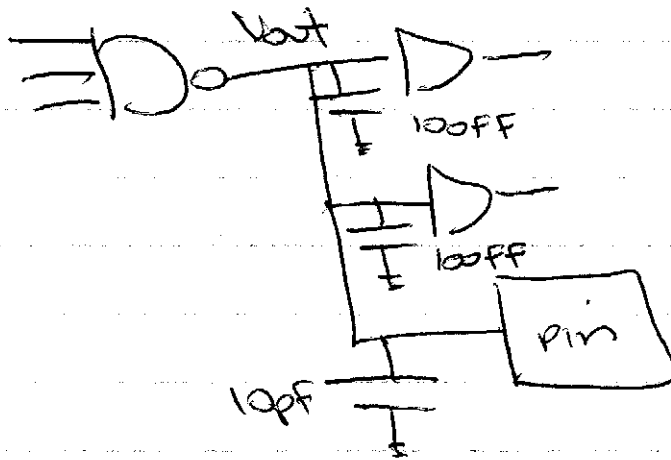

Fall time assumes  $V_{out}$  starts at  $V_{DD}$  & falls to zero  
 $\Rightarrow$  NFEET network discharges equivalent cap at  $V_{out}$

$$t_{fall} \approx 2.2 RC$$

$$C = 100fF + 100fF + 10pF$$

$$R = (10\Omega) \cdot 3$$

$\underbrace{\hspace{2cm}}_{\substack{\text{3 NFEETs in series}}}$

$$t_{fall} \approx 2.2 (30\Omega) (10.2fF)$$

$$t_{fall} \approx 673.2 \text{ psec}$$

### Problem 3

$$P_T = (C_L + C_{p0}) \cdot V_{op}^2 \cdot f$$

same device, only dropping  $V_{op}$ , so  $C_L$  &  $C_{p0}$  &  $f$  are the same for both calc.

$$P_{T6} = (6)^2 [(C_L + C_{p0}) f]$$


$$P_{T2V} = (2)^2 [(C_L + C_{p0}) f]$$

$$\% \text{ diff} = \frac{(36 - 4) [(C_L + C_{p0}) f]}{36 [(C_L + C_{p0}) f]} \times 100$$

$$= 88.89\% \text{ savings}$$

# Problem 4

A)

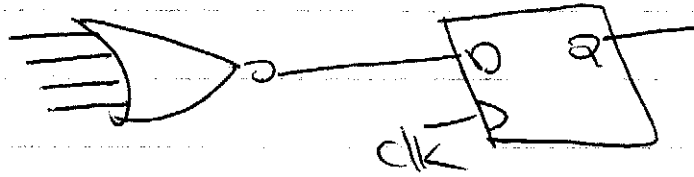

$$V_{IL} = 0.8V \quad V_{IH} = 2.2V$$



purely capacitive load so

$$V_{OH} = V_{DD} = 3.3V$$

$$V_{OL} = 0V$$

high state  $NM = V_{OH} - V_{IH} = 3.3 - 2.2 = 1.1V$   
 low state  $NM = V_{IL} - V_{OL} = 0.8 - 0 = 0.8V$


B)

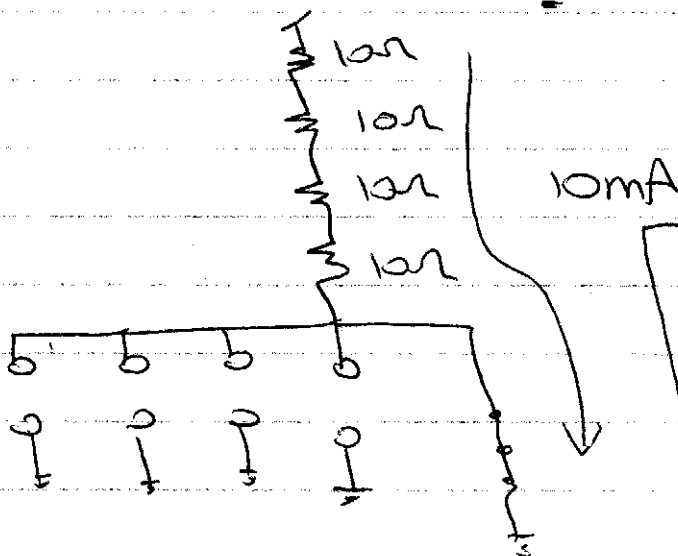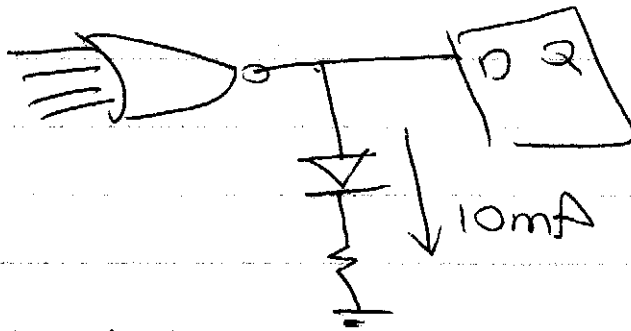

$$V_{OH} = V_{DD} - (10mA)(400\Omega) = 2.9$$

high state  $NM = 2.9 - 2.2 = 0.7V$   
 low state  $NM$  doesn't change  
 $= 0.8V$

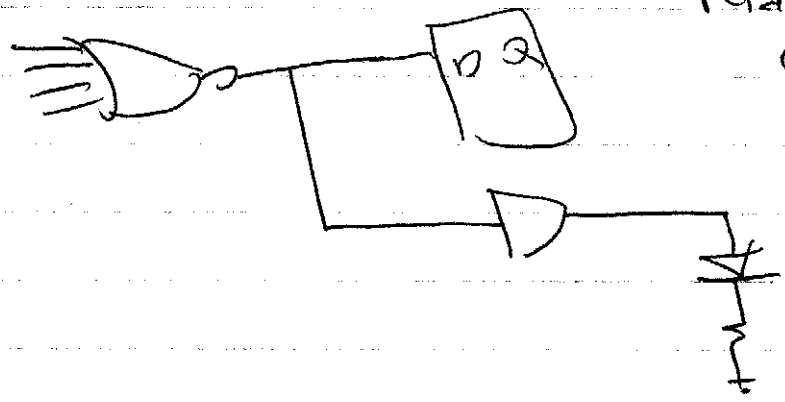c) NAND would see buffer instead of LED, so it would retain its capacitive load.



As a consequence, the high state NM would be improved (equal to part (a)).