



Homework 1


First Order Circuits

Reading: Chapter 1 and 2 of Course Notes

Complete the following problems on engineering paper using the problem solving format and submit the assignment at the beginning of class.

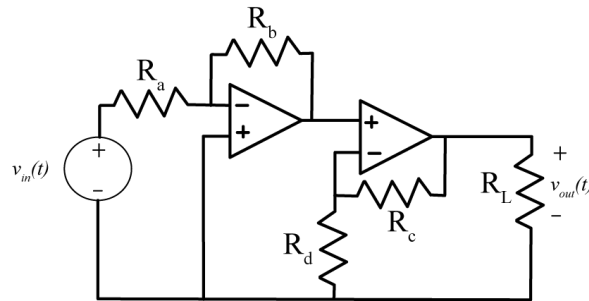
1. Chapter 2, Problem 2.1 from the Course Notes
2. Chapter 2, Problem 2.3 from the Course Notes
3. Assume the following two operational amplifiers are ideal, show that

$$v_{out}(t) = \left(-\frac{R_b R_c + R_d}{R_a R_d} \right) v_{in}(t)$$




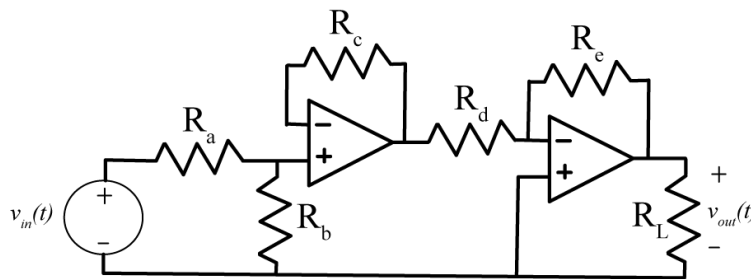4. Assume the following two operational amplifiers are ideal, show that

$$v_{out}(t) = \left(-\frac{R_e R_b}{R_d R_a + R_b} \right) v_{in}(t)$$



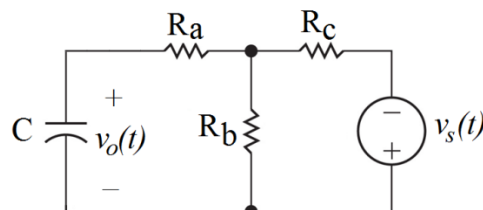5. For the following circuit, if $v_s(t)$ is the input and $v_o(t)$ is the output,






- Derive the governing differential equation and write it in standard form.
- Determine the static gain and time constant from the equation in part (a).
- Determine the time constant by using the Thevenin equivalent resistance across the capacitor.
- Determine the static gain by determine the DC voltage across the capacitor.
- Assume $R_a = 8 \text{ k}\Omega$, $R_b = 160 \text{ k}\Omega$, $R_c = 40 \text{ k}\Omega$ and $C = 0.25 \text{ }\mu\text{F}$, what is the static gain and the time constant for the circuit?

Scrambled answers: 10 ms, -0.8, 40 k Ω

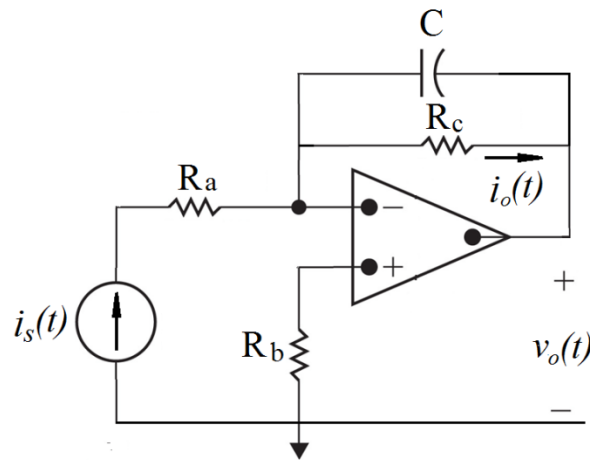6. Assume the following operational amplifier is ideal,



- If the output is $i_o(t)$, derive the governing differential equation and write it in standard form.
- Determine the static gain and time constant from the equation in part (a).
- If the output is $v_o(t)$, derive the governing differential equation and write it in standard form.
- Determine the static gain and time constant from the equation in part (c).
- Assume $C = 500 \text{ nF}$, $R_a = 50 \text{ k}\Omega$, $R_b = 20 \text{ k}\Omega$, $R_c = 150 \text{ k}\Omega$, if the output is $v_o(t)$, what is the static gain and time constant of the circuit?

Scrambled answers: 75 ms, -150k, 1