

PHYSICS III  
Dr. Joenathan – Winter 2001

Homework VIII  
Chapter 27  
27-11, 15, 25, 43, 55, 63

27-11.

$$\frac{1}{R_3} = \frac{1}{R} + \frac{1}{R} + \frac{1}{R} = 3/R$$

$$R_3 = R/3$$

$$R_2 = \frac{R^2}{2R} = \frac{R}{2}$$

$$R_{AB} = R + \frac{R}{2} + \frac{R}{3} + \frac{R}{2} + R = 3.33R$$

27-15.

$$R_{tot} = 15.0 \Omega$$

$$I_1 = \frac{\mathcal{E}}{R_{tot}} = \frac{12.0V}{15.0\Omega} = 0.800A$$

$$\Delta V_1 = I_1 R_1 = (0.800A)(9.00\Omega) = 7.20V$$

$$\Delta V_2 = \Delta V_P = I_1 R_P = I_1 \left( \frac{(R_3 + R_4)(R_2)}{R_2 + R_3 + R_4} \right) = 2.40V$$

$$I_{34} = \frac{\Delta V_P}{R_3 + R_4} = \frac{2.40V}{6.00\Omega} = 0.400A$$

$$\Delta V_3 = I_{34} R_3 = (0.400A)(4.00\Omega) = 1.60V$$

$$\Delta V_4 = I_{34} R_4 = \Delta V_P - \Delta V_3 = 2.40V - 1.60V = 0.800V$$

$$\Delta V_5 = I_1 R_5 = (0.800A)(3.00\Omega) = 2.40V$$

27-25.

$$\varepsilon_1 - I_1 R_1 - \varepsilon_3 - I_2 R_3 + \varepsilon_2 - I_1 R_2 = 0$$

$$\varepsilon_2 + I_3 R_4 - I_2 R_3 = 0$$

At junction near positive terminal of  $\varepsilon_2$ :  $-I_1 + I_2 + I_3 = 0$

$$I_1(R_1 + R_2) + I_2 R_3 = \varepsilon_1 + \varepsilon_2 - \varepsilon_3$$

$$(14.0 \times 10^3 \Omega) I_1 + (2.00 \times 10^3 \Omega) I_2 = 8.00 \text{ V}$$

$$I_2 R_3 - I_3 R_4 = \varepsilon_2$$

$$(2.00 \times 10^3 \Omega) I_2 - (4.00 \times 10^3 \Omega) I_3 = 4.00 \text{ V}$$

$$I_1 = 4.35 \times 10^{-4} \text{ A}$$

$$I_2 = 9.57 \times 10^{-4} \text{ A}$$

$$I_3 = -5.22 \times 10^{-4} \text{ A} \quad (I_3 \text{ is } 5.22 \times 10^{-4} \text{ A but in the direction opposite to that shown.})$$

$$P_4 = I_3^2 R_4 = (5.22 \times 10^{-4} \text{ A})^2 (4.00 \times 10^3 \Omega)$$

$$= 1.09 \times 10^{-3} \text{ W}$$

$$P \varepsilon_2 = \varepsilon_2 I_2 = (4.00 \text{ V})(9.57 \times 10^{-4} \text{ A})$$

$$= 3.83 \times 10^{-3} \text{ W}$$

$$\Delta V_1 = I_1 R_1 = (4.35 \times 10^{-4} \text{ A})(6.00 \times 10^3 \Omega)$$

$$= 2.61 \text{ V}$$

27-43.

(a)

$$q = C\varepsilon(1 - e^{-t/R'C}); R' = R + 1.00M \Omega$$

$$e^{-t/R'C} = 1 - \frac{q}{C\varepsilon} = 1 - \frac{8.00 \times 10^{-3} C}{(20.0 \times 10^{-6} F)(500. V)} = 0.200$$

$$t = -R'C \ln(0.200)$$

$$R' = -\frac{t}{C \ln(0.200)} = -\frac{160. s}{(20.0 \times 10^{-6} F) \ln(0.200)}$$

$$= 4.97 \times 10^6 \Omega$$

$$R = R' - 1.00 \times 10^6 \Omega = 3.97 \times 10^6 \Omega$$

(b)

$$\frac{q}{C} = \Delta V = \varepsilon e^{-t/R'C}$$

$$= (500. V) \left( e^{\frac{-120. s}{(4.97 \times 10^6 \Omega)(20.0 \times 10^{-6} F)}} \right)$$

$$= 119. V$$

27-63.

$$\varepsilon_1 - I_1 R_1 - \varepsilon_2 + I_3 R_3 - \varepsilon_3 = 0$$

$$\varepsilon_3 - I_3 R_3 - I_2 R_2 + \varepsilon_4 - I_2 R_4 = 0$$

At junction on negative side of  $\varepsilon_2$ ;  $I_1 - I_2 + I_3 = 0$

$$I_1 R_1 - I_3 R_3 = \varepsilon_1 - \varepsilon_2 - \varepsilon_3$$

$$(20.0\Omega)I_1 - (8.00\Omega)I_3 = 4.00V$$

$$I_3R_3 + I_2R_2 + I_2R_4 = \varepsilon_3 + \varepsilon_4$$

$$(10.0\Omega)I_2 + (8.00\Omega)I_3 = 10.0V$$

$$I_1 = 0.345A$$

$$I_2 = 0.709A$$

$$I_3 = 0.364A$$