

$$7.2) \quad V_m = 1.3 \text{ V} \quad V_{DD} = 3 \text{ V} \quad V_{Tn} = 0.6 \quad |V_{Tp}| = 0.82 \\ k'_n = 110 \mu\text{A/V}^2 \quad \mu_n = 2.2 \mu\text{p}$$

$$\frac{\beta_n}{\beta_p} = \left(\frac{V_m - V_{DD} + |V_{Tp}|}{V_{Tn} - V_m} \right)^2 = \left(\frac{1.3 - 3 + 0.82}{0.6 - 1.3} \right)^2 = \boxed{1.58}$$

$$\frac{\beta_n}{\beta_p} = \frac{\mu_n C_{ox} \left(\frac{W}{L}\right)_n}{\mu_p C_{ox} \left(\frac{W}{L}\right)_p} = 2.2 \frac{\left(\frac{W}{L}\right)_n}{\left(\frac{W}{L}\right)_p} = 1.58$$

$$\boxed{1.39 \cdot \left(\frac{W}{L}\right)_n = \left(\frac{W}{L}\right)_p}$$

prob 7.3 from text

$$\beta_n = 2.1 \text{ mA/V}^2$$

$$V_{TN} = 0.6 \text{ V}$$

$$V_{DD} = 5 \text{ V}$$

$$C_{FET} = 74 \text{ fF}$$

$$\beta_p = 1.8 \text{ mA/V}^2$$

$$V_{TP} = -0.7 \text{ V}$$

(a) Find V_{th} (or V_M)

$$V_{th} = \frac{V_{DD} - |V_{TP}| + \sqrt{\frac{\beta_n}{\beta_p}} V_{TN}}{1 + \sqrt{\frac{\beta_n}{\beta_p}}} = \frac{5 \text{ V} - 0.7 + 1.08 \cdot 0.6}{1 + 1.08}$$

$$V_{th} = 2.38 \text{ V}$$

(b) Find R_n & R_p

$$R_n = \frac{1}{\beta_n (V_{DD} - V_{TN})} = 108.2 \text{ } \Omega$$


$$R_p = \frac{1}{\beta_p (V_{DD} - |V_{TP}|)} = 129.2 \text{ } \Omega$$

$$(c) t_{HL} \approx 2.2 \tau_n = 2.2 R_n C_{FET} = 17.6 \text{ ps}$$

$$t_{LH} \approx 2.2 \tau_p = 2.2 R_p C_{FET} = 21.03 \text{ ps}$$

$$(d) t_{HL} = 2.2 R_n (C_{FET} + C_L) = 44.9 \text{ ps}$$
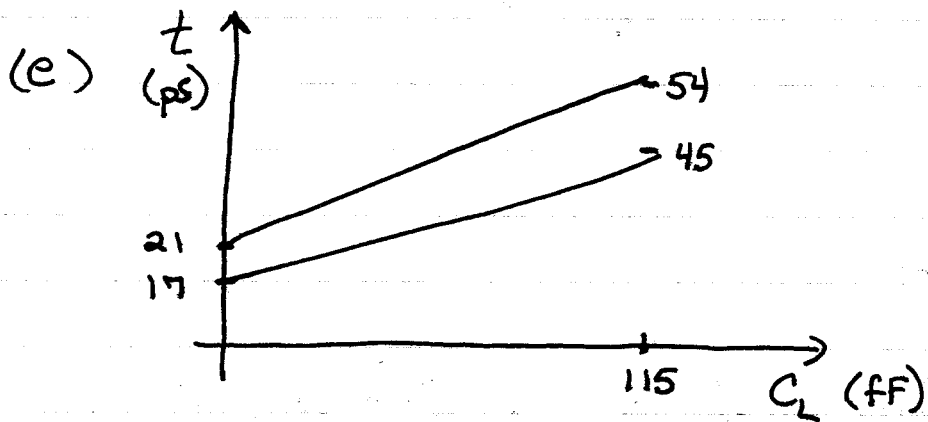
$$t_{LH} = 2.2 R_p (C_{FET} + C_L) = 54.1 \text{ ps}$$



$$\alpha_n = 2.2 R_n = 237 \Omega$$

$$\alpha_p = 2.2 R_p = 286 \Omega$$

Problem 3

$$t_{ox} = 150 \times 10^{-10} \text{ m}$$

$$V_{DD} = 3 \text{ V}$$

$$\mu_n = 580 \frac{\text{cm}^2}{\text{V}\cdot\text{s}}$$

$$V_{T0n} = 0.75 \text{ V}$$

$$\left(\frac{W}{L}\right)_n = 12$$

$$\mu_p = 235 \frac{\text{cm}^2}{\text{V}\cdot\text{s}}$$

$$V_{T0p} = -0.8 \text{ V}$$

$$\left(\frac{W}{L}\right)_p = 12$$

$$C_{ox} = \frac{\epsilon_{ox}}{t_{ox}} = \frac{(3.9)(8.854 \times 10^{-14})}{150 \times 10^{-8} \text{ cm}} =$$

$$2.3 \text{ fF}/\mu\text{m}^2$$

$$\beta_n = \mu_n C_{ox} \left(\frac{W}{L}\right)_n = \left(580 \frac{\text{cm}^2}{\text{V}\cdot\text{s}}\right) \left(\frac{100 \times 10^6 \mu\text{m}^2}{1 \text{ cm}^2}\right) \left(2.3 \frac{\text{fF}}{\mu\text{m}^2}\right) (12) = 1.6 \frac{\text{mA}}{\text{V}^2}$$

$$\beta_p = \mu_p C_{ox} \left(\frac{W}{L}\right)_p = \left(235 \frac{\text{cm}^2}{\text{V}\cdot\text{s}}\right) \left(\frac{100 \times 10^6 \mu\text{m}^2}{1 \text{ cm}^2}\right) \left(2.3 \frac{\text{fF}}{\mu\text{m}^2}\right) (12) = 648 \frac{\mu\text{A}}{\text{V}^2}$$

$$(a) V_{TH} = \frac{V_{DD} - |V_{TP}| + \sqrt{\frac{\beta_n}{\beta_p}} V_{TN}}{1 + \sqrt{\frac{\beta_n}{\beta_p}}} = \boxed{1.31 \text{ V}}$$

(b) FIND V_{IL} & V_{IH}

$$V_{IL}: \frac{\beta_n}{2} (V_{IL} - V_{TN})^2 = \frac{\beta_p}{2} [2(V_{DD} - V_{IL} - |V_{TP}|)(V_{DD} - V_{OUT}) - (V_{DD} - V_{OUT})^2]$$

$$V_{IL} \left(1 + \frac{\beta_n}{\beta_p}\right) = 2V_{OUT} - |V_{TP}| + \frac{\beta_n}{\beta_p} V_{TN}$$

Use Maple to solve simultaneously


$$\boxed{V_{IL} = 1.09 \text{ V}}$$

$$V_{IH}: \frac{\beta_n}{2} (2(V_{IH} - V_{TN})(V_{OUT}) - V_{OUT}^2) = \frac{\beta_p}{2} (V_{DD} - V_{IH} - |V_{TP}|)^2$$

$$V_{IH} \left(1 + \frac{\beta_p}{\beta_n}\right) = 2V_{OUT} + V_{TN} + \frac{\beta_p}{\beta_n} (V_{DD} - |V_{TP}|)$$

Use Maple

$$\boxed{V_{IH} = 1.44 \text{ V}}$$

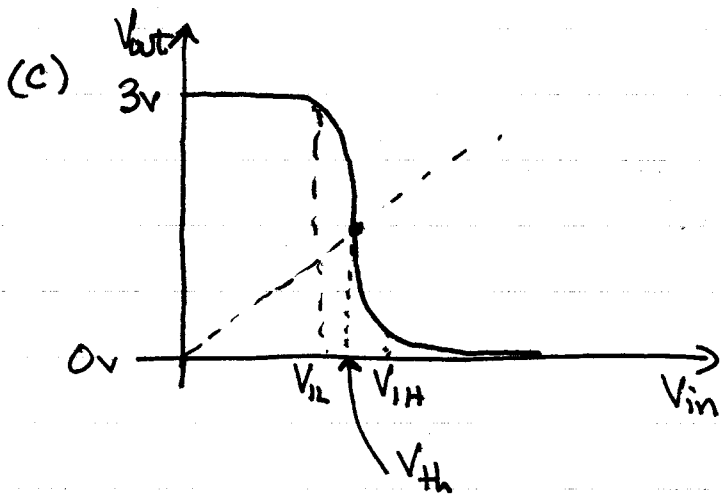

$$V_{IL} = 1.09V$$

$$V_{th} = 1.31V$$

$$V_{IH} = 1.44V$$

(D) Assuming $C_{out} = 140 \text{ fF}$

$$t_{HL} = 2.2 R_m C_{out} = \frac{2.2 (140 \times 10^{-15})}{(1.6 \times 10^{-3})(2.25)} = \boxed{86 \text{ ps}}$$

$$t_{LH} = 2.2 R_p C_{out} = \frac{2.2 (140 \times 10^{-15})}{(648 \times 10^{-6})(2.2)} = \boxed{216 \text{ ps}}$$


$$7.8) \frac{1}{2.2} \beta_p = \beta_n$$

$$V_m = \frac{V_{DD} - |V_{TP}| + 2 \sqrt{\frac{\beta_n}{\beta_p}} V_{TN}}{1 + 2 \sqrt{\frac{\beta_n}{\beta_p}}}$$

$$\frac{\beta_n}{\beta_p} = \frac{1}{2.2} \quad \sqrt{\frac{\beta_n}{\beta_p}} = 0.674$$

$$V_m = \frac{3.3 - 0.8 + 2(0.674)0.65}{1 + 2(0.674)} = \boxed{1.43 \text{ V}}$$

7.10

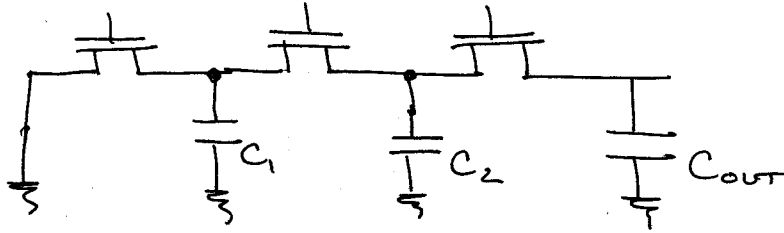

$$C_1 = 36 \text{ fF}$$

$$C_2 = 36 \text{ fF}$$

$$C_{\text{OUT}} = 130 \text{ fF}$$

$$\beta_n = 2.0 \text{ mA/V}^2$$

$$V_{\text{DD}} = 3.3 \text{ V}$$

$$V_{\text{TN}} = 0.7 \text{ V}$$

$$R_n = \frac{1}{\beta_n (V_{\text{DD}} - V_{\text{TN}})} = 192 \text{ } \Omega$$

(a) USING ELMORE

$$\tau = C_{\text{OUT}} (3R_n) + C_2 (2R_n) + C_1 R_n$$

$$= 7.48 \times 10^{-11} \text{ s} + 1.38 \times 10^{-11} \text{ s} + 6.91 \times 10^{-12} \text{ s}$$

$$= 95.53 \text{ ps}$$

$$(b) \tau = C_{\text{OUT}} (3R_n) = 7.48 \times 10^{-11} \text{ s} = 74.8 \text{ ps}$$

$$\% \text{ difference} = \frac{95.53 - 74.8}{95.53} = 22\%$$