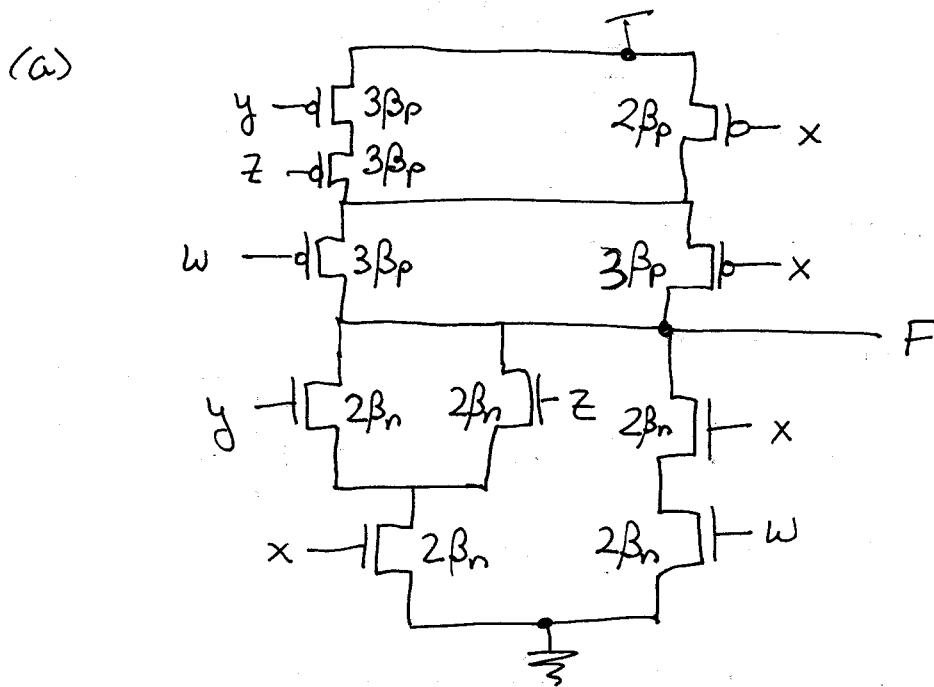


7.12)  $F = \overline{x \cdot (y + z) + x \cdot w}$



(b) sizes on FETs

(c) Worst Case Path would be

nFETS :  $x y \bar{z} \bar{w}$   
 pFETS :  $\bar{y} \bar{z} \bar{w} x$

$y_p \rightarrow z_p \rightarrow w_p$  : rise  
 $y_n \rightarrow x_n$  : fall

## Problem 2

Estimate Rise & fall time

$$\beta_n = 60 \frac{\mu A}{V^2} \quad \beta_p = 30 \frac{\mu A}{V^2}$$

$$V_{DD} = 5V \quad V_T = 0.7V$$

$$t_r = 2.2 \tau_r = 26.42 \text{ ns}$$

$$t_f = 2.2 \tau_f = 19.67 \text{ ns}$$

$\tau_r$  worst case: transistors pB & pA

$$\tau_r = C_L (R_{pA} + R_{pB}) + C_{N1} R_{pB} = \boxed{12.01 \text{ ns}}$$

$$R_{pA} = \frac{1}{\beta_p(2)(4.3V)} = 3.87 \text{ k}\Omega$$

$$R_{pB} = \frac{1}{\beta_p(1)(4.3V)} = 7.75 \text{ k}\Omega$$

$\tau_f$  worst case: transistors nC, nB, nD


$$R_{nC} = R_{nB} = \frac{1}{\beta_n(1)(4.3V)} = 3.87 \text{ k}\Omega$$

$$R_{nD} = \frac{1}{\beta_n(4)(4.3V)} = 968 \Omega$$

$$\tau_f = C_L (R_{nC} + R_{nB} + R_{nD}) + C_{N2} (R_{nB} + R_{nD}) + C_{N3} R_{nD}$$

$$= \boxed{8.94 \text{ ns}}$$

7.15)

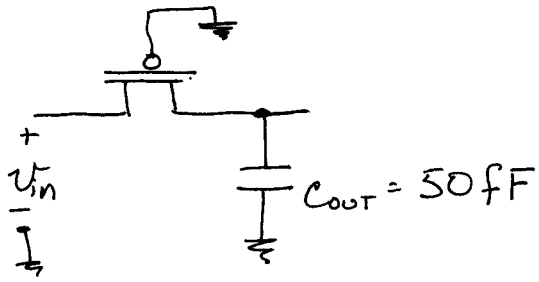

$$\left(\frac{w}{L}\right)_p = 8 \quad k'_p = 60 \frac{\mu\text{A}}{\text{V}^2} \quad V_{DD} = 3.3 \text{ V} \quad |V_{TP}| = 0.8 \text{ V}$$

(a) FIND FALL TIME

$$V_{SG1} = V_{OUT}$$

$$V_{SD} = V_{OUT}$$

$$t_f \approx 18 \tau_p = 18 R_p C_{OUT} = 750 \text{ ps}$$

$$(b) t_r = 2.94 \tau_p = 2.94 R_p C_{OUT} = 123 \text{ ps}$$