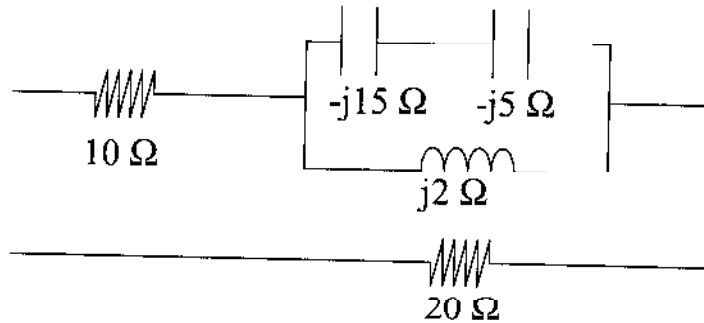


1) Find the equivalent impedance of the following circuit. You may use Maple or a calculator to do your calculations, but **show all of your steps** on paper. (25 pts)




$$1) \quad Z_{Req} = 10\ \Omega + 20\ \Omega + j0 = 30 + j0\ \Omega$$

$$2) \quad Z_{ceq} = -j15\ \Omega - j5\ \Omega = -j20\ \Omega$$

$$3) \quad Z_{Lc} = \frac{Z_{ceq} Z_L}{Z_{ceq} + Z_L} = \frac{(-j20)(j2)}{(-j20) + (j2)} = \frac{-j^2 40}{-j18} = j \frac{20}{9}$$

$$4) \quad Z_{eq} = Z_{Req} + Z_{Lc} = \boxed{30 + j \frac{20}{9}\ \Omega}$$

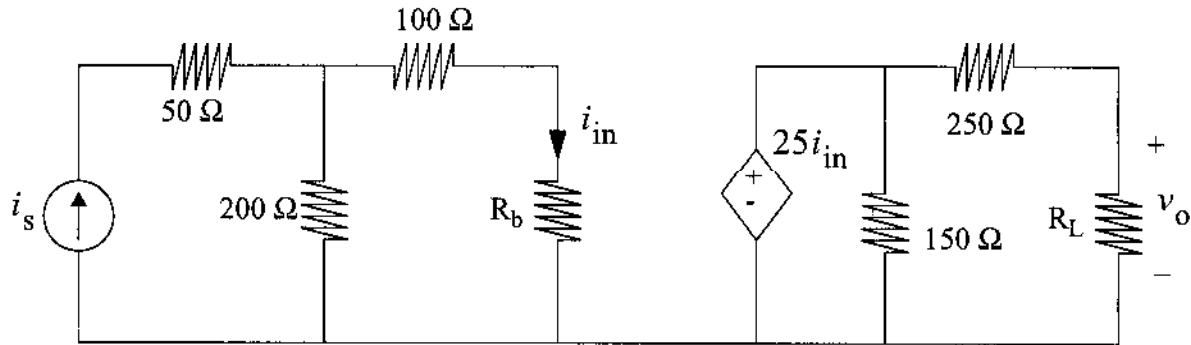2) Use the following diagram for the next set of questions. You are limited to using the four tools: Voltage Divider, Current Divider, Source Transformations, and Ohm's Law. You must show all your work to get full credit.: (25 pts)



A) Determine whether R_b should be maximized or minimized to minimize the amplifier loading of the source. Provide an equation to justify your answer. (9 pts)

Make $i_{in} \approx i_s$

$$i_{in} = i_s \frac{200\ \Omega}{300\ \Omega + R_b}$$

Make R_b as small as possible

B) Determine whether R_L should be maximized or minimized to minimize the loading of the amplifier. Provide an equation to justify your answer. (9 pts)

Make $v_o \approx 25\ \Omega i_{in}$

$$v_o = 25\ \Omega i_{in} \frac{R_L}{R_L + 250\ \Omega}$$


Make R_L as large as possible

C) Assuming that $R_b = 25\ \Omega$ and $R_L = 75\ \Omega$, find the gain $A = \frac{v_o}{i_s}$. (7 pts)

$$A = \frac{v_o}{i_s} = 25\ \Omega \left(\frac{200\ \Omega}{300\ \Omega + R_b} \right) \left(\frac{R_L}{R_L + 250\ \Omega} \right) = 4.19\ \Omega$$

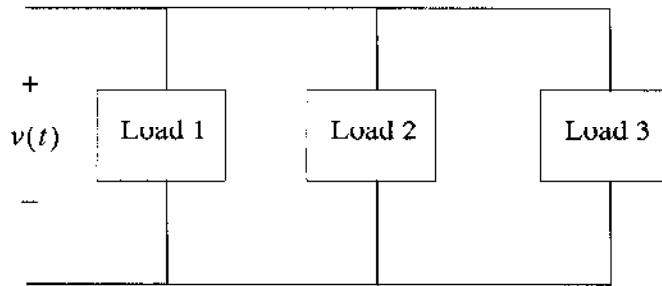3) Use the following diagram for the next series of questions (25 pts)

$$v(t) = 10 \cos\left(120\pi t + \frac{\pi}{6}\right)$$



A) Load 1 is a capacitive load and absorbs 7.5 kW and 2.5 kVARs. What is the complex power absorbed by this load? (6 pts)

$$P = 7.5 \text{ kW}$$

$$Q = 2.5 \text{ kVAR}$$

$$\underline{S} = P + jQ = 7.5 + j2.5 \text{ kVA}$$

B) Load 2 is 10kVA at a 0.28 pf-leading. What is the complex power absorbed by this load? (6pts)

$$|\underline{S}| = 10 \text{ kVA}$$

$$0.28 = -\cos(\theta_s)$$

$$\underline{S} = 10 \angle -73.7^\circ \text{ kVA}$$

$$= 2800 - j9600$$

C) The impedance of Load 3 is $12 + j5 \Omega$. What is the complex power absorbed by this load? (6pts)


$$\underline{Z}_3 = 12 + j5 \Omega$$

$$V_3 = \frac{10}{\sqrt{2}} \angle \frac{\pi}{6} \text{ (RMS)}$$


$$\underline{S} = \frac{V_3 V_3^*}{\underline{Z}_3^*} = 3.84 \angle -22.62^\circ = 3.55 + j1.48$$

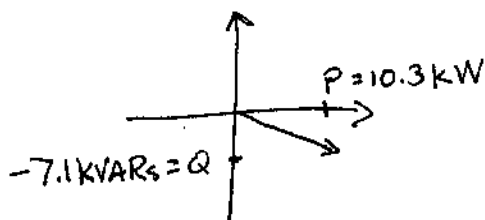D) Draw the power triangle for the combined power absorbed by all three loads. (7 pts)

$$\underline{S}_T = \underline{S}_1 + \underline{S}_2 + \underline{S}_3 = 10.3 - j7.1 \text{ kVA} = P_T + jQ_T$$



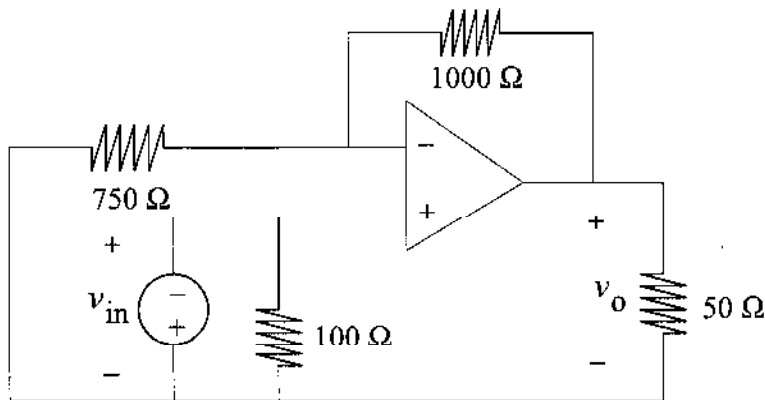4) Find the gain of the op-amp circuit $A = \frac{v_o}{v_{in}}$ (25 pts)



Non-Inverting AMP

$$\text{So } A = \frac{v_o}{v_{in}} = \left(1 + \frac{R_{fb}}{R_i}\right) = \left(1 + \frac{1000}{750}\right)$$
$$= 2.33$$

Because v_{in} is negative

$$v_o = A_v v_{in} \text{ will be negative}$$