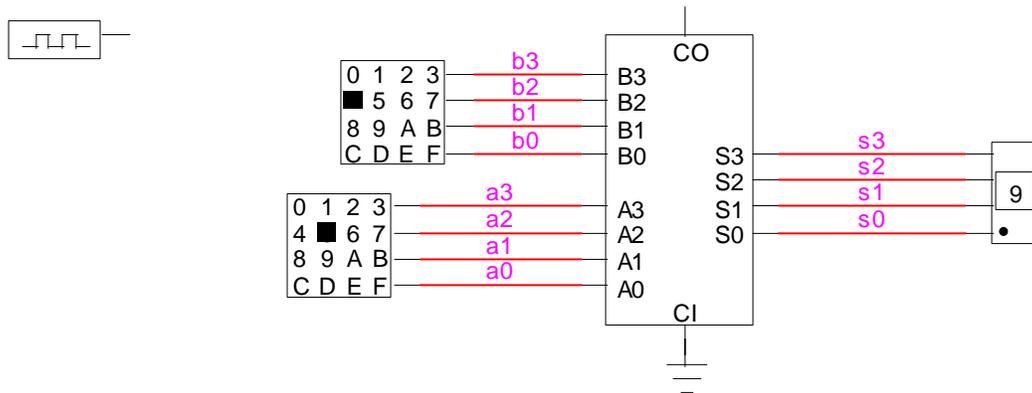
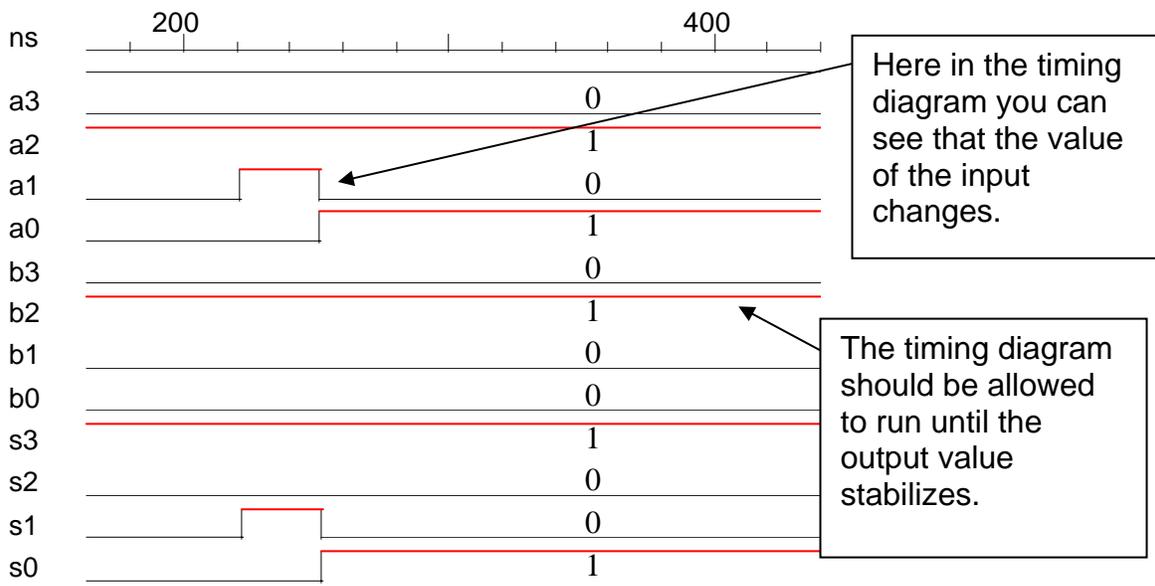


To Create A Non-Sequential Timing Diagram



Setup your circuit using hex keypads. Be sure to label all the input lines (a3 – a0 and b3 – b0) and all the output lines (s3 – s0). (Note: In this circuit, the clock is added in order to produce the timing diagram. If the device you are using requires a clock input then you need not add another clock)



You should annotate one segment of the waveform after the output stabilizes. From this annotation we can read that $0101 + 0100 = 1001$