

1 Find the waveforms of  $F(A,B,C)$  in the following circuits with and without delays.

